

Chapter 17

Power Supplies

Glossary

Bipolar Transistor — A term used to denote the common two junction transistor types (NPN, PNP) as opposed to the field effect families of devices (JFET, MOSFET and so on).

Bleeder — A resistive load across the output or filter of a power supply, intended to quickly discharge stored energy once the supply is turned off.

C-Rate — The charging rate for a battery, expressed as a ratio of the battery's ampere-hour rating.

Circular Mils — A convenient way of expressing the cross-sectional area of a round conductor. The area of the conductor in circular mils is found by squaring its diameter in mils (thousandths of an inch), rather than squaring its radius and multiplying by pi. For example, the diameter of 10-gauge wire is 101.9 mils (0.1019 inch). Its cross-sectional area is 10380 CM, or 0.008155 square inches.

Core Saturation (Magnetic) — That condition whereby the magnetic flux in a transformer or inductor core is more than the core can handle. If the flux is forced beyond this point, the permeability of the core will decrease, and it will approach the permeability of air.

Crowbar — A last-ditch protection circuit included in many power supplies to protect the load equipment against failure of the regulator in the supply. The crowbar senses an overvoltage condition on the supply's output and fires a shorting device (usually an SCR) to directly short-circuit the supply's output and protect the load. This causes very high currents in the power supply, which blow the supply's input-line fuse.

Darlington Transistor — A package

of two transistors in one case, with the collectors tied together, and the emitter of one transistor connected to the base of the other. The effective current gain of the pair is approximately the product of the individual gains of the two devices.

DC-DC Converter — A circuit for changing the voltage of a dc source to ac, transforming it to another level, and then rectifying the output to produce direct current.

Fast Recovery Rectifier — A specially doped rectifier diode designed to minimize the time necessary to halt conduction when the diode is switched from a forward-biased state to a reverse-biased state.

Foldback Current Limiting — A special type of current limiting used in linear power supplies, which reduces the current through the supply's regulator to a low value under short circuited load conditions in order to protect the series pass transistor from excessive power dissipation and possible destruction.

Ground Fault (Circuit) Interrupter (GFI or GFCI) — A safety device installed between the household power mains and equipment where there is a danger of personnel touching an earth ground while operating the equipment. The GFI senses any current flowing directly to ground and immediately switches off all power to the equipment to minimize electrical shock. GFIs are now standard equipment in bathroom and outdoor receptacles.

Input-Output Differential — The voltage drop appearing across the series pass transistor in a linear voltage regulator. This term is usually stated as a minimum val-

ue, which is that voltage necessary to allow the regulator to function and conduct current. A typical figure for this drop in most three-terminal regulator ICs is about 2.5 V. In other words, a regulator that is to provide 12.5 V dc will need a source voltage of at least 15.0 V at all times to maintain regulation.

Inverter — A circuit for producing ac power from a dc source.

Peak Inverse Voltage — The maximum reverse-biased voltage that a semiconductor is rated to handle safely. Exceeding the peak inverse rating can result in junction breakdown and device destruction.

Power Conditioner — Another term for a power supply.

Regulator — A device (such as a Zener diode) or circuitry in a power supply for maintaining a constant output voltage over a range of load currents and input voltages.

Resonant Converter — A form of dc-dc converter characterized by the series pass switch turning on into an effective series-resonant load. This allows a zero current condition at turn-on and turn-off. The resonant converter normally operates at frequencies between 100 kHz and 500 kHz and is very compact in size for its power handling ability.

Ripple — The residual ac left after rectification, filtration and regulation of the input power.

RMS — Root of the Mean of the Squares. Refers to the effective value of an alternating voltage or current, corresponding to the dc voltage or current that would cause the same heating effect.

Secondary Breakdown — A runaway failure condition in a transistor, occurring at higher collector-emitter voltages, where hot spots occur due to (and promoting) localization of the collector current at that region of the chip.

Series Pass Transistor, or Pass Transistor — The transistor(s) that controls the passage of power between the unregulated dc source and the load in a regulator. In a linear regulator, the series pass transistor acts as a controlled resistor to drop the voltage to that needed by the load. In a switch-mode regulator, the series pass transistor switches between its ON and OFF states.

SOAR (Safe Operating Area) — The range of permissible collector current and

collector-emitter voltage combinations where a transistor may be safely operated without danger of device failure.

Spike — An extremely short perturbation on a power line, usually lasting less than a few microseconds.

Surge — A moderate-duration perturbation on a power line, usually lasting for hundreds of milliseconds to several seconds.

Transient — A short perturbation on a power line, usually lasting for microseconds to tens of milliseconds.

Varistor — A surge suppression device used to absorb transients and spikes occurring on the power lines, thereby protecting electronic equipment plugged into that line. Frequently, the term MOV (Metal Oxide

Varistor) is used instead.

Volt-Amperes — The product obtained by multiplying the current times the voltage in an ac circuit without regard for the phase angle between the two. This is also known as the *apparent power* delivered to the load as opposed to the actual or *real power* absorbed by the load, expressed in watts.

Voltage Multiplier — A type of rectifier circuit that is arranged so as to charge a capacitor or capacitors on one half-cycle of the ac input voltage waveform, and then to connect these capacitors in series with the rectified line or other charged capacitors on the alternate half-cycle. The voltage doubler and tripler are commonly used forms of the voltage multiplier.


Alternating-Current Power

Ken Stuart, W3VVN, wrote the text for the theory portion of this chapter.

In most residences, three wires are brought in from the outside electrical-service mains to the house distribution panel. In this three-wire system, one wire is neutral and should be at earth ground. The voltage between the other two wires is 60-Hz alternating current with a potential difference of approximately 240 V RMS. Half of this voltage appears between each of these wires and the neutral, as indicated in Fig 17.1A. In systems of this type, the 120-V household loads are divided at the breaker panel as evenly as possible between the two sides of the power mains. Heavy appliances such as electric stoves, water heaters, central air conditioners and so forth, are designed for 240-V operation and are connected across the two ungrounded wires.

Both ungrounded wires should be fused. A fuse or switch should never be used in the neutral wire, however. Opening the neutral wire does not disconnect the equipment from an active or “hot” line, creating a potential shock hazard between that line and earth ground.

Another word of caution should be given at this point. Since one side of the ac line is grounded to earth, all communications equipment should be reliably connected to the ac-line ground through a heavy ground braid or bus wire of #14 or heavier-gauge wire. This wire must be a separate conductor. You must not use the power-wiring neutral conductor for this safety ground. (A properly wired 120-V outlet with a ground terminal uses one wire for the ac hot connection, one wire for the

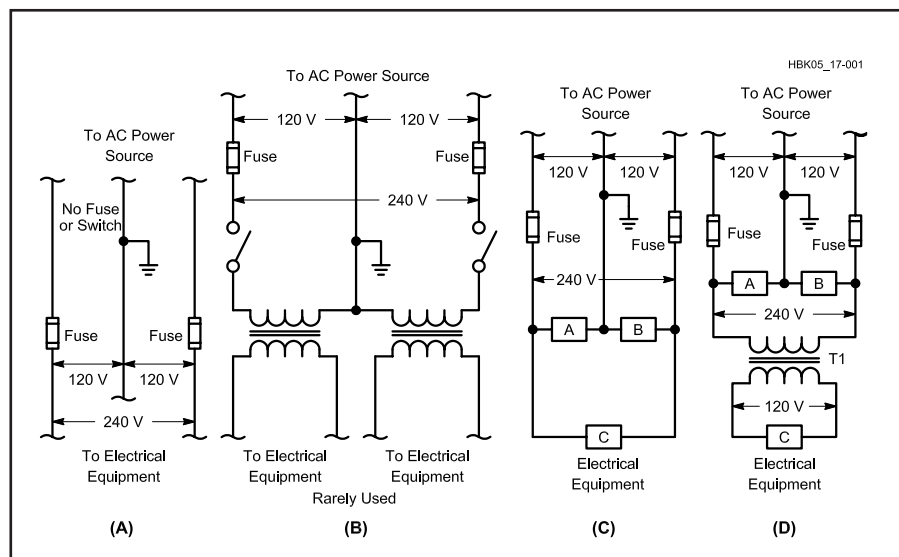

17.1 — Three-wire power-line circuits. At A, normal three-wire-line termination. No fuse should be used in the grounded (neutral) line. The ground symbol is the power company's ground, not yours! Do *not* connect *anything*, including the equipment chassis, to the power neutral wire. At B, the “hot” lines each have a switch, but a switch in the neutral line would not remove voltage from either side of the line and should never be used. At C, connections for both 120 and 240-V transformers. At D, operating a 120-V plate transformer from the 240-V line to avoid light blinking. T1 is a 2:1 step-down transformer.

ac neutral connection and a third wire for the safety ground connection.) This not only places the chassis of the equipment at earth ground for minimal RF energy on the chassis, but also provides a measure of safety for the operator in the event of accidental short or leakage of one side of the ac line to the chassis.

Remember, the antenna system is al-

most always bypassed to the chassis via an RF choke or tuning circuit, which could make the antenna electrically “live” with respect to the earth ground and create a potentially lethal shock hazard. A Ground Fault Circuit Interrupter (GFCI or GFI) is also desirable for safety reasons, and should be a part of the shack’s electrical power wiring.

FUSES AND CIRCUIT BREAKERS

All transformer primary circuits should be fused properly, and multiple secondary outputs should also be individually fused. To determine the approximate current rating of the fuse or circuit breaker to be used, multiply each current being drawn by the load or appliance, in amperes, by the voltage at which the current is being drawn. In the case of linear regulated power supplies, this voltage has to be the voltage appearing at the output of the rectifiers before being applied to the regulator stage. Include the current taken by bleeder resistors and voltage dividers. Also include filament power if the transformer is supplying filaments. The National Electrical Code also specifies maximum fuse ratings based on the wire sizes used in the transformer and connections.

After multiplying the various voltages and currents, add the individual products. This will be the total power drawn from the line by the supply. Then divide this power by the line voltage and add 10 or 20%. Use a fuse or circuit breaker with the nearest larger current rating. Remember that the charging of filter capacitors can take large surges of current when the supply is turned on. If turn on is a problem, use slow-blow fuses, which allow for high initial surge currents.

For low-power semiconductor circuits, use fast-blow fuses. As the name implies, such fuses open very quickly once the current exceeds the fuse rating by more than 10%.

ELECTRICAL POWER CONDITIONING

We often use the term “power supply” to denote a piece of equipment that will process the electrical power from a source, such as the ac power mains, by manipulating it so the device output will be acceptable to other equipment that we want to power. The common form of the power supply is the familiar direct-current power supply, which will power a transmitter, receiver or other of a wide variety of electronic devices.

In the strictest terms, however, the power supply is not actually a source, or “supply” of power, but is actually a processor of already existing energy. Therefore, the old term of “power supply” is becoming obsolete, and a new term has arisen to refer to the technology of the processing of electrical power: “power conditioning.” By contrast, the term “power supply” is now used to refer to devices for chemical to electrical energy conversion (batteries) or mechanical to electrical conversion (generators). Other varieties include thermoelectric generators (TEGs)

and radioactive thermoelectric generators (RTGs).

In this chapter, we shall examine the traditional forms of power conditioning, which consists of the following component parts in various combinations: transformer, rectifier, filter and regulator. We will also look briefly at true power supplies as we examine battery technology and emergency power generation.

POWER TRANSFORMERS

Numerous factors are considered in order to match a transformer to its intended use. Some of these parameters are listed below:

1. Output voltage and current (volt-ampere rating)
2. Power source voltage and frequency
3. Ambient temperature
4. Duty cycle and temperature rise of the transformer at rated load
5. Mechanical shape and mounting

Volt-Ampere Rating

In alternating-current equipment, the term “volt-ampere” is often used rather than the term “watt.” This is because ac components must handle reactive power as well as real power. If this is confusing, consider a capacitor connected directly across the secondary of a transformer. The capacitor appears as a reactance that permits current to flow, just as if the load were a resistor. The current is at a 90° phase angle, however. If we assume a perfect capacitor, there will be no heating of the capacitor, so no real power (watts) will be delivered by the transformer. The transformer must still be capable of supplying the voltage, and be able to handle the current required by the reactive load. The current in the transformer windings will heat the windings as a result of the I^2R losses in the winding resistances. The product of the voltage and current is referred to as “volt-amperes”, since “watts” is reserved for the real, or dissipated, power in the load. The volt-ampere rating will always be equal to, or greater than, the power actually being drawn by the load.

The number of volt-amperes (VA) delivered by a transformer depends not only upon the dc load requirements, but also upon the type of dc output filter used (capacitor or choke input), and the type of rectifier used (full-wave center tap or full-wave bridge). With a capacitive-input filter, the heating effect in the secondary is higher because of the high peak-to-average current ratio. The volt-amperes handled by the transformer may be several times the power delivered to the load. The primary winding volt-am-

peres will be somewhat higher because of transformer losses.

Source Voltage and Frequency

A transformer operates by producing a magnetic field in its core and windings. The intensity of this field varies directly with the instantaneous voltage applied to the transformer primary winding. These variations, coupled to the secondary windings, produce the desired output voltage. Since the transformer appears to the source as an inductance in parallel with the (equivalent) load, the primary will appear as a short circuit if dc is applied to it. The unloaded inductance of the primary must be high enough so as not to draw an excess amount of input current at the design line frequency (normally 60 Hz). This is achieved by providing sufficient turns on the primary and enough magnetic core material so that the core does not saturate during each half-cycle.

The magnetic field strength produced in the core is usually referred to as the *flux density*. It is set to some percentage of the maximum flux density that the core can stand without saturating, since at saturation the core becomes ineffective and causes the inductance of the primary to plummet to a very low level and input current to rise rapidly. This causes high primary currents and extreme heating in the primary windings. For this reason, transformers and other electromagnetic equipment designed for 60-Hz systems must not be used on 50-Hz power systems unless specifically designed to handle the lower frequency.

How to Evaluate an Unmarked Power Transformer

Many hams that regularly visit hamfests eventually end up with a junk box filled with used and unmarked transformers. After years of use, transformer labels or markings on the coil wrappings may come off or be obscured. There is a good possibility that the transformer is still useable. The problem is to determine what voltages and currents the transformer can supply. First consider the possibility that you may have an audio transformer or other impedance-matching device rather than a power transformer. If you aren't sure, don't connect it to ac power!

If the transformer has color-coded leads, you are in luck. There is a standard for transformer lead color-coding, as is given in the **Component Data and References** chapter. Where two colors are listed, the first one is the main color of the insulation; the second is the color of the stripe.

Check the transformer windings with an ohmmeter to determine that there are no

shorted (or open) windings. The primary winding usually has a resistance higher than a filament winding and lower than a high-voltage winding.

A convenient way to test the transformer is to rig a pair of test leads to an electrical plug with a 25-W household light bulb in series to limit current to safe (for the transformer) levels. See **Fig 17.2**. Use an isolation transformer, and be sure to insulate all connections before you plug into the ac mains. Switch off the power while making or changing any connections. Connect the test leads to each winding separately. **BE CAREFUL! YOU ARE DEALING WITH HAZARDOUS VOLTAGES!** The filament/heater windings will cause the bulb to light to full brilliance. The high-voltage winding will cause the bulb to be extremely dim or to show no light at all, and the primary winding will probably cause a small glow.

When you are connected to what you think is the primary winding, measure the voltages at the low-voltage windings with an ac voltmeter. If you find voltages close to 6-V ac and 5-V ac, you know that you have found the primary. Label the primary and low voltage windings.

Even with the light bulb, a transformer can be damaged by connecting ac mains power to a low-voltage or filament winding. In such a case the insulation could break down in a high-voltage winding.

Connect the voltmeter to the high-voltage windings. Remember that the old TV transformers will typically put out as much as 800 V or so across the winding, so make sure that your meter can withstand these potentials without damage. Divide

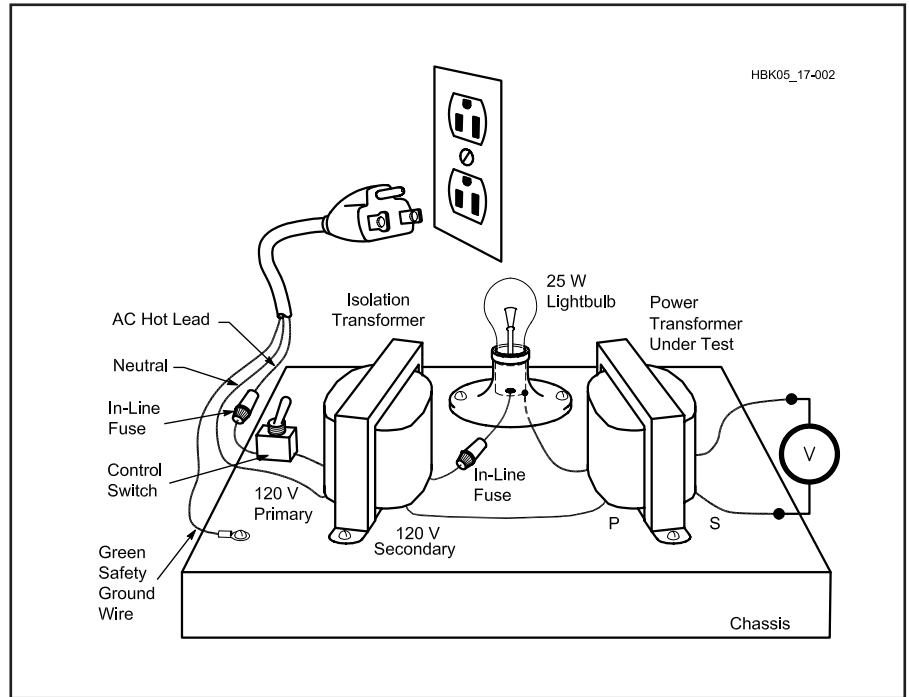


Fig 17.2 — Use a test fixture like this to test unknown transformers. Don't omit the isolation transformer, and be sure to insulate all connections before you plug into the ac mains.

6.3 by the voltage you measured across the 6.3-V winding in this test setup. This gives a multiplier that you can use to determine the actual no-load voltage rating of the high-voltage secondary. Simply multiply the ac voltage measured across the winding by the multiplier.

The current rating of the windings can

be determined by loading each winding with the primary connected directly (no bulb) to the ac line. Using power resistors, increase loading on each winding until its voltage drops by about 10% from the no-load figure. The current drawn by the resistors is the approximate winding load-current rating.

Rectifier Types

VACUUM TUBE

Once the mainstay of the rectifier field, the vacuum-tube rectifier has largely been supplanted by the silicon diode, but it may be found in vintage receivers still in use. Vacuum-tube rectifiers were characterized by high forward voltage drops and inherently poor regulation, but they were immune to ac line transients that can destroy other rectifier types.

MERCURY VAPOR

The mercury-vapor rectifier was an improvement over the vacuum tube rec-

tifier in that the electron stream from cathode to plate would ionize the vaporized mercury in the tube and greatly reduce the forward voltage drop. Since ionized mercury is a much better conductor of current than a vacuum, these tubes can carry relatively high currents. As a result, they were popular in transmitters and RF power amplifiers.

Mercury rectifiers had to be treated with special care, however. When power was initially applied, the tube filament had to be turned on first to vaporize condensed mercury before the high-voltage ac could

be applied to the plate. This could take from one to two minutes. Also, if the tube was handled or the equipment transported, filament power would have to be applied for about a half hour to vaporize any mercury droplets that might have been shaken onto tube insulating surfaces. Mercury vapor rectifiers have mostly been replaced by silicon diodes.

SELENIUM

The selenium rectifier was the first of the solid-state rectifiers to find its way into commercial electronic equipment. Of-

fering a relatively low forward voltage drop, selenium rectifiers found their way into the plate supplies of test equipment and accessories, which needed only a few tens of milliamperes of current at about a hundred volts, such as grid-dip meters, VTVMs and so forth.

Selenium rectifiers had a relatively low reverse resistance and were therefore inefficient. Voltage breakdown per rectifying junction was only about 20 V.

GERMANIUM

Germanium diodes were the first of the solid-state semiconductor rectifiers. They have an extremely low forward voltage drop. Germanium diodes are relatively temperature sensitive, however. They can be easily destroyed by overheating during soldering, for instance. Also, they have some degree of back resistance, which varies with temperature.

Germanium diodes are used for special applications where the very low forward drop is needed, such as signal diodes used for detectors and ring modulators.

SILICON

Silicon diodes are the main choice today for virtually all rectifier applications.

They are characterized by extremely high reverse resistance, forward drops of usually a volt or less and operation at high temperatures.

FAST RECOVERY

DC-DC converters regularly operate at 25 kHz and higher frequencies. Switch-mode regulators also operate in these same frequency ranges. When the switching transistors in these devices switch, voltage transitions take place within time periods usually much less than one microsecond, and the new FET switching transistors cause transitions that are often less than 100 ns.

When the transitions in these circuits occur, the previously conducting diodes see a reversal of current direction. This change tends to reverse bias those diodes, and thereby put them into an open-circuit condition. Unfortunately, solid-state rectifiers cannot be made to cease conduction instantaneously. As a result, when the opposing diodes in a bridge rectifier or full-wave rectifier become conductive at the time the converter switches states, the diodes being turned off will actually conduct in the reverse direction for a brief time, and effectively short circuit

the converter for several microseconds. This puts excessive strain on the switching transistors and creates high current spikes, leading to electromagnetic interference. As the switching frequency of the converter or regulator increases, more of these transitions happen each second, and more power is lost due to this diode cross-conduction.

Semiconductor manufacturers have recognized this as a problem for some time. Many companies have product lines of specially doped diodes designed to minimize this storage time. These diodes are called fast-recovery rectifiers and are commonly used in high-frequency dc-dc converters and regulators. Diodes are available that can recover in about 50 ns and less, as compared to standard-recovery diodes that can take several microseconds to cease conduction in the reverse direction.

Amateurs building their own switching power supplies and dc-dc converters will find greatly improved performance with the use of these diodes in their output rectifiers. Fast-recovery rectifiers are not needed for 60-Hz rectification because the source voltage is a sine wave (no fast transitions) and the input frequency is too slow for transitions to be of significance.

Rectifier Circuits

HALF-WAVE RECTIFIER

Fig 17.3 shows a simple half-wave rectifier circuit. A rectifier (in this case a semiconductor diode) conducts current in one direction but not the other. During one half of the ac cycle, the rectifier conducts and there is current through the rectifier to the load (indicated by the solid line in Fig 17.3B). During the other half cycle, the rectifier is reverse biased and there is no current (indicated by the broken line in Fig 17.3B) to the load. As shown, the output is in the form of pulsed dc, and current always flows in the same direction. A filter can be used to smooth out these variations and provide a higher average dc voltage from the circuit. This idea will be covered in the section on filtration further on in this chapter.

The average output voltage — the voltage read by a dc voltmeter — with this circuit (no filter connected) is $0.45 \times E_{RMS}$ of the ac voltage delivered by the transformer secondary. Because the frequency of the pulses is low (one pulse per cycle), considerable filtering is required to pro-

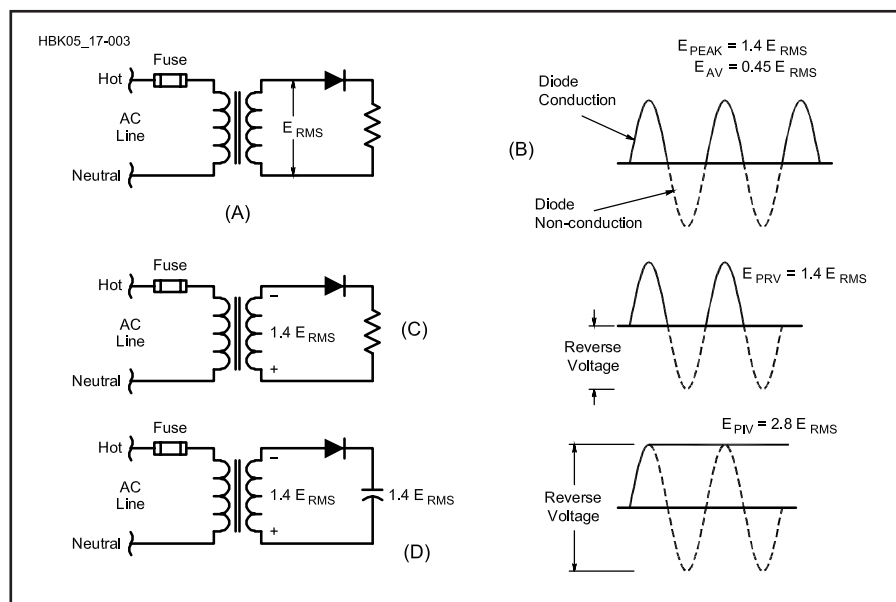


Fig 17.3 — Half-wave rectifier circuit. A illustrates the basic circuit, and B displays the diode conduction and nonconduction periods. The peak-inverse voltage impressed across the diode is shown at C and D, with a simple resistor load at C and a capacitor load at D. E_{PIV} is $1.4 E_{RMS}$ for the resistor load and $2.8 E_{RMS}$ for the capacitor load.

vide adequately smooth dc output. For this reason the circuit is usually limited to applications where the required current is small, as in a transmitter bias supply.

The peak inverse voltage (PIV), the voltage that the rectifier must withstand when it isn't conducting, varies with the load. With a resistive load, it is the peak ac voltage ($1.4 \times E_{RMS}$); with a capacitor filter and a load drawing little or no current, it can rise to $2.8 \times E_{RMS}$. The reason for this is shown in parts C and

D of Fig 17.3. With a resistive load as shown at C, the voltage applied to the diode is that voltage on the lower side of the zero-axis line, or $1.4 \times E_{RMS}$. A capacitor connected to the circuit (shown at D) will store the peak positive voltage when the diode conducts on the positive pulse. If the circuit is not supplying any current, the voltage across the capacitor will remain at that same level. The peak inverse voltage impressed across the diode is now the sum of the voltage stored in the

capacitor plus the peak negative swing of voltage from the transformer secondary. In this case the PIV is $2.8 \times E_{RMS}$.

FULL-WAVE CENTER-TAP RECTIFIER

A commonly used rectifier circuit is shown in Fig 17.4. Essentially an arrangement in which the outputs of two half-wave rectifiers are combined, it makes use of both halves of the ac cycle. A transformer with a center-tapped secondary is required with the circuit.

The average output voltage is $0.9 \times E_{RMS}$ of half the transformer secondary; this is the maximum that can be obtained with a suitable choke-input filter. The peak output voltage is $1.4 \times E_{RMS}$ of half the transformer secondary; this is the maximum voltage that can be obtained from a capacitor-input filter.

As can be seen in Fig 17.4C, the PIV impressed on each diode is independent of the type of load at the output. This is because the peak inverse voltage condition occurs when diode A conducts and diode B does not conduct. The positive and negative voltage peaks occur at precisely the same time, a condition different from that in the half-wave circuit. As the cathodes of diodes A and B reach a positive peak ($1.4 E_{RMS}$), the anode of diode B is at a negative peak, also $1.4 E_{RMS}$, but in the opposite direction. The total peak inverse voltage is therefore $2.8 E_{RMS}$.

Fig 17.4B shows that the frequency of the output pulses is twice that of the half-wave rectifier. Comparatively less filtering is required. Since the rectifiers work alternately, each handles half of the load current. The current rating of each rectifier need be only half the total current drawn from the supply.

FULL-WAVE BRIDGE RECTIFIER

Another commonly used rectifier circuit is illustrated in Fig 17.5. In this arrangement, two rectifiers operate in series on each half of the cycle, one rectifier being in the lead to the load, the other being the return lead. As shown in Fig 17.5A and B, when the top lead of the transformer secondary is positive with respect to the bottom lead, diodes A and C will conduct while diodes B and D are reverse biased. On the next half cycle, when the top lead of the transformer is negative with respect to the bottom, diodes B and D will conduct while diodes A and C are reverse biased.

The output wave shape is the same as that from the simple full-wave center-tap rectifier circuit. The average dc output voltage into a resistive load or choke-input filter is 0.9 times the RMS voltage delivered by the transformer secondary;

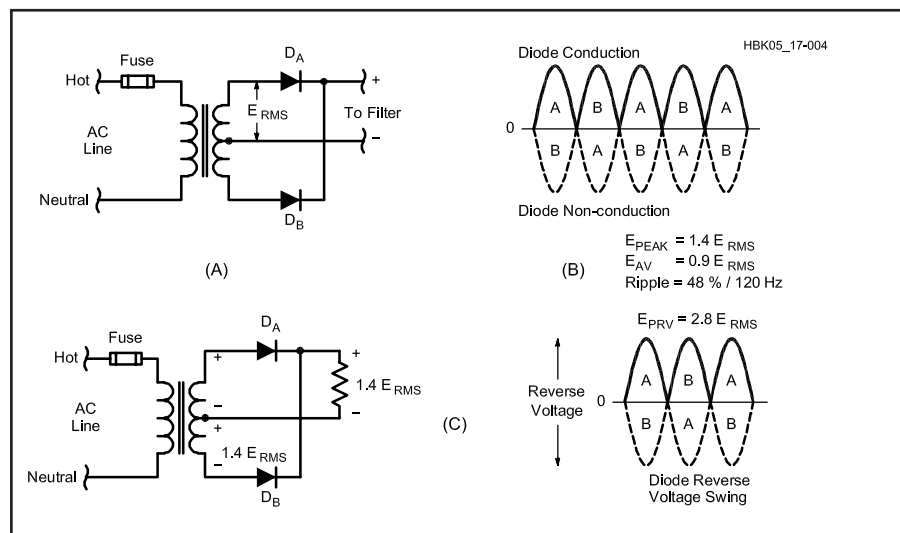


Fig 17.4 — Full-wave center-tap rectifier circuit. A illustrates the basic circuit. Diode conduction is shown at B with diodes A and B alternately conducting. The peak-inverse voltage for each diode is $2.8 E_{RMS}$ as depicted at C.

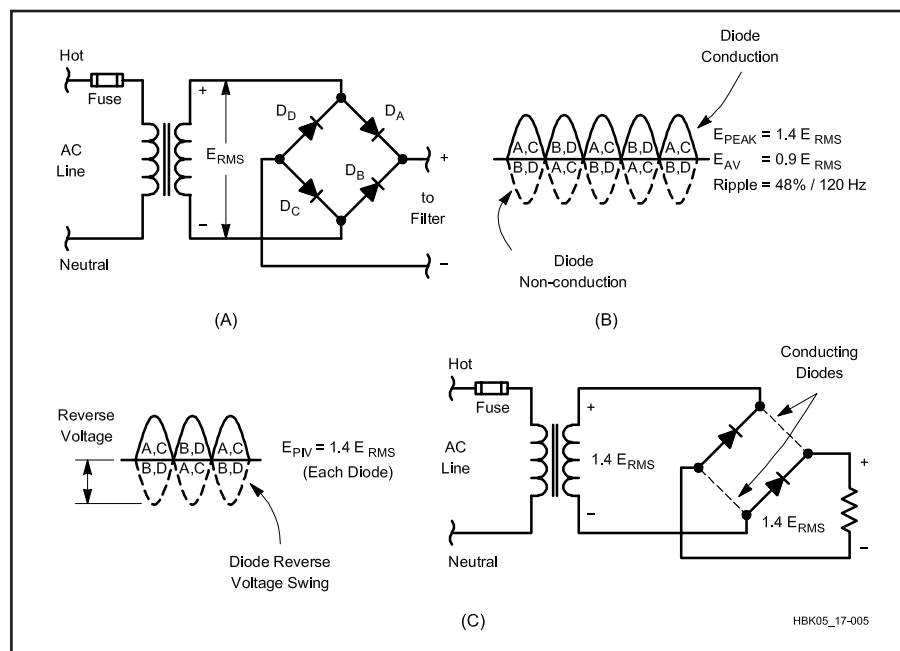


Fig 17.5 — Full-wave bridge rectifier circuit. The basic circuit is illustrated at A. Diode conduction and nonconduction times are shown at B. Diodes A and C conduct on one half of the input cycle, while diodes B and D conduct on the other. C displays the peak inverse voltage for one half cycle. Since this circuit reverse-biases two diodes essentially in parallel, $1.4 E_{RMS}$ is applied across each diode.

with a capacitor filter and a light load, the maximum output voltage is 1.4 times the secondary RMS voltage.

Fig 17.5C shows the inverse voltage to be $1.4 E_{RMS}$ for each diode. When an alternate pair of diodes (such as D_A and D_C) is conducting, the other diodes are essentially connected in parallel in a reverse-biased direction. The reverse stress is then $1.4 E_{RMS}$. Each pair of diodes conducts on alternate half cycles, with the full load current through each diode during its conducting half cycle. Since each diode is not conducting during the other half cycle the average current is one half the total load current drawn from the supply.

PROS AND CONS OF THE RECTIFIER CIRCUITS

Comparing the full-wave center-tap rectifier circuit and the full-wave bridge-rectifier circuit, we can see that both circuits have almost the same rectifier requirement, since the center tap has half the number of rectifiers as the bridge. These rectifiers have twice the inverse voltage rating requirement of the bridge diodes, however. The diode current ratings are identical for the two circuits. The bridge makes better use of the transformer's secondary than the center-tap rectifier, since the transformer's full winding supplies power during both half cycles, while each half of the center-tap circuit's secondary provides power only during its positive half-cycle. This is usually referred to as the *transformer utilization factor*, which is unity for the bridge configuration and 0.5 for the full-wave, center-tapped circuit.

The bridge rectifier often takes second place to the full-wave center tap rectifier in high-current low-voltage applications. This is because the two forward-conducting series-diode voltage drops in the bridge introduce a volt or more of additional loss, and thus more heat to be dissipated, than does the single diode drop of the full-wave rectifier.

The half-wave configuration is rarely used in 60-Hz rectification for other than bias supplies. It does see considerable use, however, in high-frequency switching power supplies in what are called *forward converter* and *flyback converter* topologies.

VOLTAGE MULTIPLIERS

Other rectification circuits of interest are the so-called *voltage multipliers*. These circuits function by the process of charging one or more capacitors on one half cycle of the ac waveform, and then connecting that capacitor or capacitors in series with the opposite polarity of the ac waveform

on the alternate half cycle. With full-wave multipliers, this charging occurs during both half-cycles.

Voltage multipliers, particularly doublers, find considerable use in high-voltage supplies. When a doubler is employed, the secondary winding of the power transformer need only be half the voltage that would be required for a bridge rectifier. This reduces voltage stress in the windings and decreases the transformer insulation requirements. It also reduces the chance of corona in the windings, prolonging the life of the transformer. This is not without cost, however, because the transformer-secondary current rating has to be correspondingly doubled.

Half-Wave Doubler

Fig 17.6 shows the circuit of a half-wave voltage doubler. Parts B, C and D illustrate the circuit operation. For clarity, assume the transformer voltage polarity at the moment the circuit is activated is that shown at B. During the first negative half cycle, D_A conducts (D_B is in a nonconductive state), charging $C1$ to the peak rectified voltage ($1.4 E_{RMS}$). $C1$ is charged with the polarity shown at B. During the positive half cycle of the secondary voltage, D_A is cut off and D_B conducts, charging capacitor $C2$. The amount of voltage delivered to $C2$ is the sum of the transformer peak secondary voltage plus the voltage stored in $C1$ ($1.4 E_{RMS}$). On the next negative half cycle, D_B is non-conducting and $C2$ will discharge into the load. If no load is connected across $C2$, the capacitors will remain charged — $C1$ to $1.4 E_{RMS}$ and $C2$

to $2.8 E_{RMS}$. When a load is connected to the circuit output, the voltage across $C2$ drops during the negative half cycle and is recharged up to $2.8 E_{RMS}$ during the positive half cycle.

The output waveform across $C2$ resembles that of a half-wave rectifier circuit because $C2$ is pulsed once every cycle. Fig 17.6D illustrates the levels to which the two capacitors are charged throughout the cycle. In actual operation, the capacitors will not discharge all the way to zero as shown.

Full-Wave Doubler

Fig 17.7 shows the circuit of a full-wave voltage doubler. The circuit operation can best be understood by following Parts B, C and D. During the positive half cycle of the transformer secondary voltage, as shown at B, D_A conducts charging capacitor $C1$ to $1.4 E_{RMS}$. D_B is not conducting at this time.

During the negative half cycle, as shown at C, D_B conducts, charging capacitor $C2$ to $1.4 E_{RMS}$, while D_A is non-conducting. The output voltage is the sum of the two capacitor voltages, which will be $2.8 E_{RMS}$ under no-load conditions. Fig 17.7D illustrates that each capacitor alternately receives a charge once per cycle. The effective filter capacitance is that of $C1$ and $C2$ in series, which is less than the capacitance of either $C1$ or $C2$ alone.

Resistors $R1$ and $R2$ in Fig 17.7A are used to limit the surge current through the rectifiers. Their values are based on the transformer voltage and the rectifier surge-current rating, since at the instant

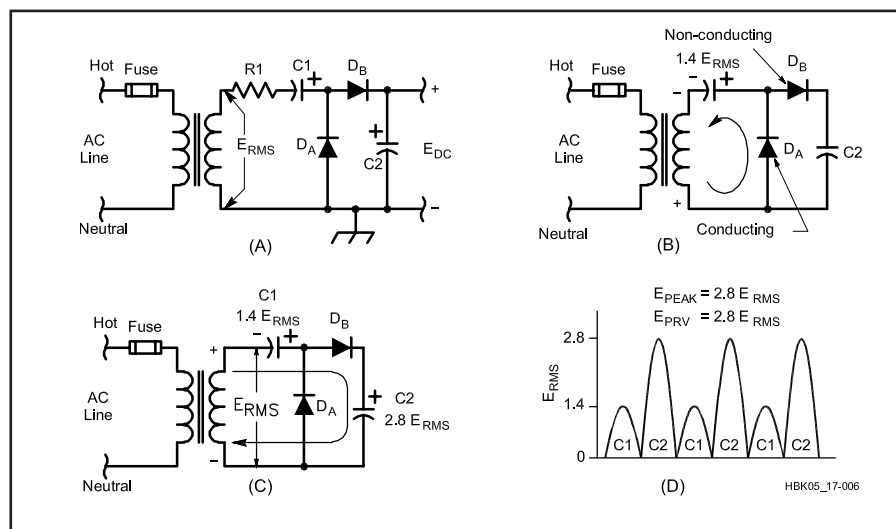


Fig 17.6 — Part A shows a half-wave voltage-doubler circuit. B displays how the first half cycle of input voltage charges $C1$. During the next half cycle (shown at C), capacitor $C2$ charges with the transformer secondary voltage plus that voltage stored in $C1$ from the previous half cycle. The arrows in parts B and C indicate the conventional current. D illustrates the levels to which each capacitor charges over several cycles.

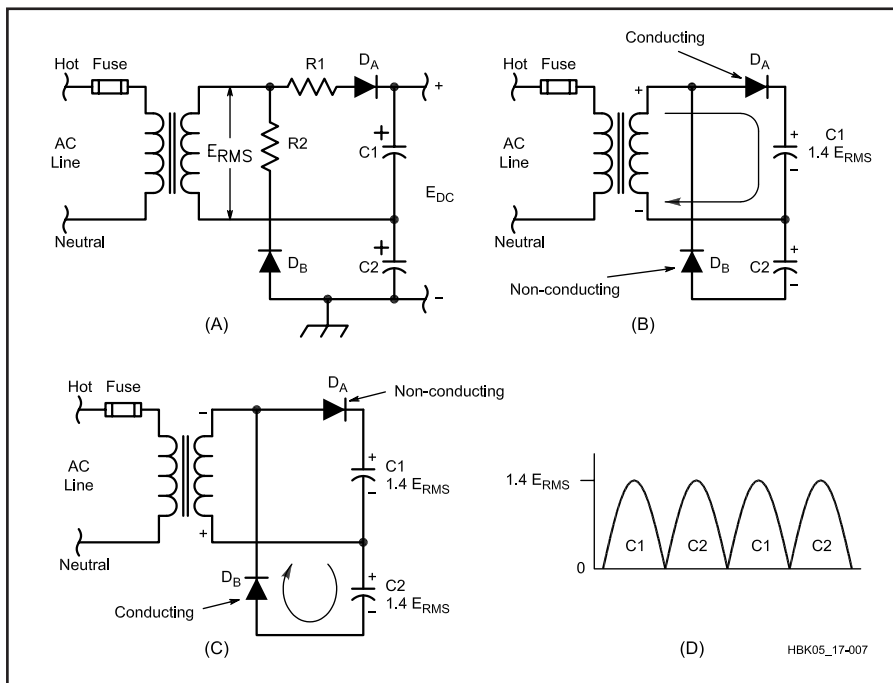


Fig 17.7 — Part A shows a full-wave voltage-doubler circuit. One-half cycle is shown at B and the next half cycle is shown at C. Each capacitor receives a charge during every input-voltage cycle. D illustrates how each capacitor is charged alternately.

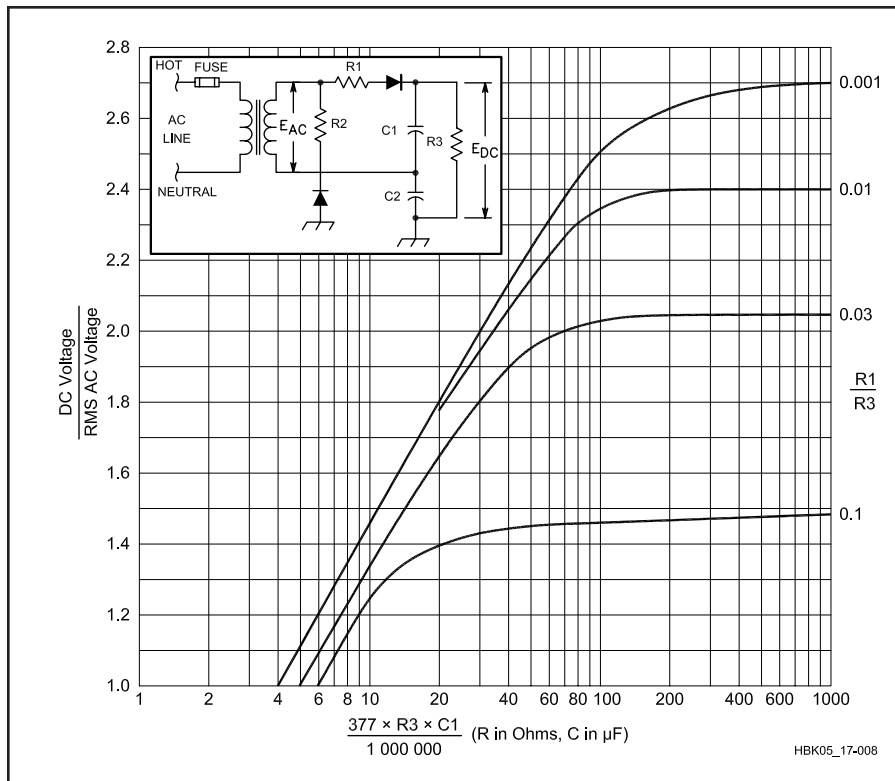


Fig 17.8 — DC output voltages from a full-wave voltage-doubler circuit as a function of the filter capacitances and load resistance. For the ratio R_1 / R_3 and for the $R_3 \times C_1$ product, resistance is in ohms and capacitance is in microfarads. Equal resistance values for R_1 and R_2 , and equal capacitance values for C_1 and C_2 are assumed. These curves are adapted from those published by Otto H. Schade in "Analysis of Rectifier Operation," *Proceedings of the I. R. E.*, July 1943.

the power supply is turned on, the filter capacitors look like a short-circuited load. Provided the limiting resistors can withstand the surge current, their current-handling capacity is based on the maximum load current from the supply. Output voltages approaching twice the peak voltage of the transformer can be obtained with the voltage doubling circuit shown in Fig 17.7. **Fig 17.8** shows how the voltage depends upon the ratio of the series resistance to the load resistance, and the load resistance times the filter capacitance. The peak inverse voltage across each diode is $2.8 E_{RMS}$.

Tripler and Quadrupler

Fig 17.9A shows a voltage-tripling circuit. On one half of the ac cycle, C₁ and C₃ are charged to the source voltage through D₁, D₂ and D₃. On the opposite half of the cycle, D₂ conducts and C₂ is charged to twice the source voltage, because it sees the transformer plus the charge in C₁ as its source (D₁ is cut off during this half cycle). At the same time, D₃ conducts, and with the transformer and the charge in C₂ as the source, C₃ is charged to three times the transformer voltage.

The voltage-quadrupling circuit of Fig 17.9B works in similar fashion. In either of the circuits of Fig 17.9, the output voltage will approach an exact multiple of the peak ac voltage when the output

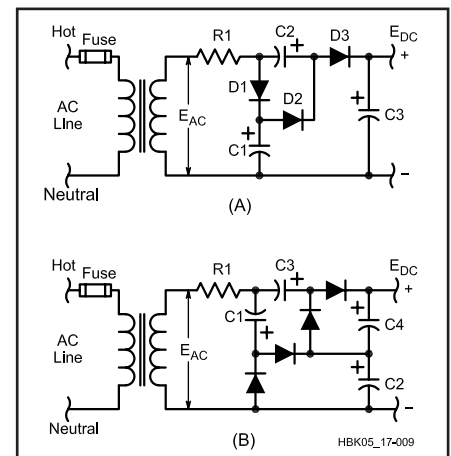


Fig 17.9 — Voltage-multiplying circuits with one side of the transformer secondary used as a common connection. A shows a voltage tripler and B shows a voltage quadrupler. Capacitances are typically 20 to 50 μF, depending on the output current demand. Capacitor dc ratings are related to E_{PEAK} ($1.4 E_{RMS}$):
 C₁ — Greater than E_{PEAK}
 C₂ — Greater than $2 E_{PEAK}$
 C₃ — Greater than $3 E_{PEAK}$
 C₄ — Greater than $2 E_{PEAK}$

current drain is low and the capacitance values are high.

RECTIFIER RATINGS VERSUS OPERATING STRESS

Power supplies designed for amateur equipment use silicon rectifiers almost exclusively. These rectifiers are available in a wide range of voltage and current ratings. In peak inverse voltage (PIV) ratings of 600 or less, silicon rectifiers carry current ratings as high as 400 A. At 1000 PIV, the current ratings may be several amperes. It is possible to stack several units in series for higher voltages. Stacks are available commercially that will handle peak inverse voltages up to 10 kV at a load current of 1 A or more.

RECTIFIER STRINGS OR STACKS

Diodes in Series

When the PIV rating of a single diode is not sufficient for the application, similar diodes may be used in series. (Two 500 PIV diodes in series will withstand 1000 PIV and so on.) There used to be a general recommendation to place a resistor across each diode in the string to equalize the PIV drops. With modern diodes, this practice is no longer necessary.

Modern silicon rectifier diodes are constructed to have an avalanche characteristic. Simply put, this means that the diffusion process is controlled so the diode will exhibit a Zener characteristic in the reverse biased direction before destructive breakdown of the junction can occur. This provides a measure of safety for diodes in series. A diode will go into Zener conduction before it self destructs. If other diodes in the chain have not reached their avalanche voltages, the current through the avalanched diode will be limited to the leakage current in the other diodes. This should normally be very low. For this reason, shunting resistors are generally not needed across diodes in series rectifier strings. In fact, shunt resistors

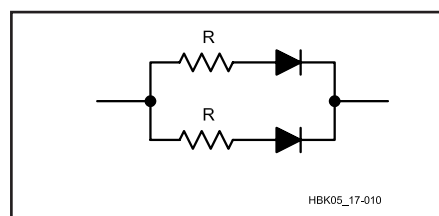


Fig 17.10 — Diodes can be connected in parallel to increase the current-handling capability of the circuit. Each diode should have a series current-equalizing resistor, with a value selected to provide a few tenths of a volt drop at the expected current.

can actually create problems because they can produce a low-impedance source of damaging current to any diode that may have reached avalanche potential.

Diodes in Parallel

Diodes can be placed in parallel to increase current-handling capability. Equalizing resistors should be added as shown in **Fig 17.10**. Without the resistors, one diode may take most of the current. The resistors should be selected to have several tenths of a volt drop at the expected peak current.

RECTIFIER PROTECTION

The important specifications of a silicon diode are:

1. PIV, the peak inverse voltage.
2. I_0 , the average dc current rating.
3. I_{REP} — the peak repetitive forward current.
4. I_{SURGE} , a non-repetitive peak half-sine wave of 8.3 ms duration (one-half cycle of 60-Hz line frequency).
5. Switching speed.
6. Power dissipation and thermal resistance.

The first two specifications appear in most catalogs. I_{REP} and I_{SURGE} often are not specified in catalogs, but they are very important. Because the rectifier never allows current to flow more than half the

time, when it does conduct it has to pass at least twice the average direct current. With a capacitor-input filter, the rectifier conducts much less than half the time, so that when it does conduct, it may pass as much as 10 to 20 times the average dc current, under certain conditions. This is shown in **Fig 17.11**. Part A shows a simple half-wave rectifier with a resistive load. The waveform to the right of the drawing shows the output voltage along with the diode current. Parts B and C show conditions for circuits with “low” capacitance and “high” capacitance to filter the output.

After the capacitor is charged to the peak-rectified voltage, a period of diode non-conduction elapses while the output voltage discharges through the load. As the voltage begins to rise on the next positive pulse, a point is reached where the rectified voltage equals the stored voltage in the capacitor. As the voltage rises beyond that point, the diode begins to supply current. The diode will continue to conduct until the waveform reaches the crest, as shown. Since the diode has only that short time in which to charge the capacitor with enough energy to provide power to the load for the non-conducting balance of the cycle, the current will be high. The larger the capacitor for a given load, the shorter the diode conduction time and the higher the peak repetitive current (I_{REP}).

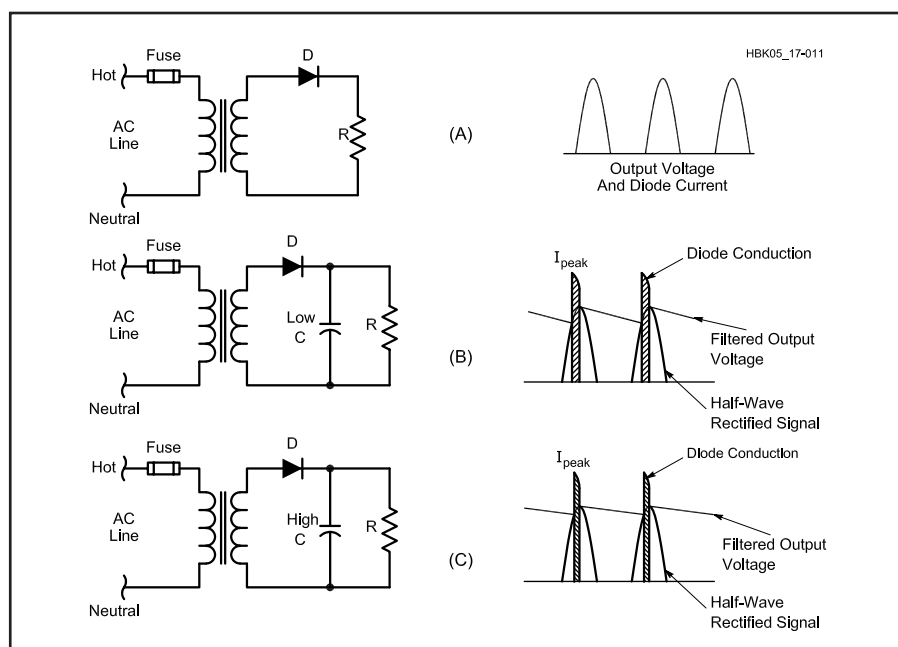


Fig 17.11 — The circuit shown at A is a simple half-wave rectifier with a resistive load. The waveform shown to the right is the output voltage and current. B illustrates how the diode current is modified by the addition of a capacitor filter. The diode conducts only when the rectified voltage is greater than the voltage stored in the capacitor. Since this time is usually only a short portion of a cycle, the peak current will be quite high. C shows an even higher peak current. This is caused by the larger capacitor, which effectively shortens the diode conduction period.

Current Inrush

When the supply is first turned on, the discharged input capacitor looks like a dead short, and the rectifier passes a very heavy current. This current transient is called I_{SURGE} . The maximum surge current rating for a diode is usually specified for a duration of one-half cycle (at 60 Hz), or about 8.3 ms. Some form of surge protection is usually necessary to protect the diodes until the input capacitor becomes nearly charged, unless the diodes used have a very high surge-current rating (several hundred amperes). If a manufacturer's data sheet is not available, an educated guess about a diode's capability can be made by using these rules of thumb for silicon diodes commonly used in Amateur Radio power supplies:

Rule 1. The maximum I_{REP} rating can be assumed to be approximately four times the maximum I_0 rating.

Rule 2. The maximum I_{SURGE} rating can be assumed to be approximately 12 times the maximum I_0 rating. (This figure should provide a reasonable safety factor. Silicon rectifiers with 750-mA dc ratings, for example, seldom have 1-cycle surge ratings of less than 15 A; some are rated up to 35 A or more.) From this you can see that the rectifier should be selected on the basis of I_{SURGE} and not on I_0 ratings.

Although you can sometimes rely on the dc resistance of the transformer secondary to provide ample surge-current limiting, this is seldom true in high-voltage power supplies. Series resistors are often installed between the secondary and the rectifier strings or in the transformer's primary circuit, but these can be a deterrent to good voltage regulation.

Voltage Spikes

Vacuum-tube rectifiers had little problem with voltage spikes on the incoming power lines — the possibility of an internal arc was of little consequence, since the heat produced was of very short duration and had little effect on the massive plate and cathode structures. Unfortunately, such is not the case with silicon diodes.

Silicon diodes, because of their forward voltage drop of about one volt, create very little heat with high forward currents and therefore have tiny junction areas. Conduction in the reverse direction, however, can cause junction temperatures to rise

extremely rapidly with the resultant melting of the silicon and migration of the dopants into the rectifying junction. Destruction of the semiconductor junction is the end result.

To protect semiconductor rectifiers, special surge-absorption devices are available for connection across the incoming ac bus or transformer secondary. These devices operate in a fashion similar to a Zener diode, by conducting heavily when a specific voltage level is reached. Unlike Zener diodes, however, they have the ability to absorb very high transient energy levels without damage. With the clamping level set well above the normal operating voltage range for the rectifiers, these devices normally appear as open circuits and have no effect on the power-supply circuits. When a voltage transient occurs, however, these protection devices clamp the spike and thereby prevent destruction of the rectifiers.

Transient protectors are available in three basic varieties:

1. Silicon Zener diodes — large junction Zeners specifically made for this purpose and available as single junction for dc (unipolar) and back-to-back junctions for ac (bipolar). These silicon protectors are available under the trade name of TransZorb from General Semiconductor Corporation and are also made by other manufacturers. They have the best transient suppressing characteristics of the three varieties mentioned here, but are expensive and have the least energy absorbing capability per dollar of the group.

2. Varistors — made of a composition metal-oxide material that breaks down at a certain voltage. Metal-oxide varistors, also known as MOVs, are cheap and easily obtained, but have a higher internal resistance, which allows a greater increase of clamped voltage than the Zener variety. Varistors can also degrade with successive transients within their rated power handling limits (this is not usually a problem in the ham shack where transients are few and replacement of the varistor is easily accomplished).

Varistors usually become short circuited when they fail. Large energy dissipation can result in device explosion. Therefore, it is a good idea to include a fuse that limits the short-circuit current through the varistor, and to protect people and circuitry

from debris.

3. Gas tube — similar in construction to the familiar neon bulb, but designed to limit conducting voltage rise under high transient currents. Gas tubes can usually withstand the highest transient energy levels of the group. Gas tubes suffer from an ionization time problem, however. A high voltage across the tube will not immediately cause conduction. The time required for the gas to ionize and clamp the spike is inversely proportional to the level of applied voltage in excess of the device ionization voltage. As a result, the gas tube will let a little of the transient through to the equipment before it activates.

In installations where reliable equipment operation is critical, the local power is poor and transients are a major problem, the usual practice is to use a combination of protectors. Such systems consist of a varistor or Zener protector, combined with a gas-tube device. Operationally, the solid-state device clamps the surge immediately, with the beefy gas tube firing shortly thereafter to take most of the surge from the solid-state device.

Heat

The junction of a diode is quite small; hence, it must operate at a high current density. The heat-handling capability is, therefore, quite small. Normally, this is not a prime consideration in high-voltage, low-current supplies. Use of high-current rectifiers at or near their maximum ratings (usually 2-A or larger stud-mount rectifiers) requires some form of heat sinking. Frequently, mounting the rectifier on the main chassis — directly, or with thin mica insulating washers — will suffice. If insulated from the chassis, a thin layer of silicone grease should be used between the diode and the insulator, and between the insulator and the chassis, to assure good heat conduction. Large, high-current rectifiers often require special heat sinks to maintain a safe operating temperature. Forced-air cooling is sometimes used as a further aid. Safe case temperatures are usually given in the manufacturer's data sheets and should be observed if the maximum capabilities of the diode are to be realized. See the thermal design section in the **Real-World Component Characteristics** chapter for more information.

Filtration

The pulsating dc waves from the rectifiers are not sufficiently constant in amplitude to prevent hum corresponding to the pulsations. Filters are required between the rectifier and the load to smooth out the pulsations into an essentially constant dc voltage. The design of the filter depends to a large extent on the dc voltage output, the voltage regulation of the power supply and the maximum load current rating of the rectifier. Power-supply filters are low-pass devices using series inductors and shunt capacitors.

LOAD RESISTANCE

In discussing the performance of power-supply filters, it is sometimes convenient to express the load connected to the output terminals of the supply in terms of resistance. The load resistance is equal to the output voltage divided by the total current drawn, including the current drawn by the bleeder resistor.

VOLTAGE REGULATION

The output voltage of a power supply always decreases as more current is drawn, not only because of increased voltage drops in the transformer and filter chokes, but also because the output voltage at light loads tends to soar to the peak value of the transformer voltage as a result of charging the first capacitor. Proper filter design can eliminate the soaring effect. The change in output voltage with load is called voltage regulation, and is expressed as a percentage.

$$\text{Percent Regulation} = \frac{(E_1 - E_2)}{E_2} \times 100\% \quad (1)$$

where:

E1 = the no-load voltage
E2 = the full-load voltage.

A steady load, such as that represented by a receiver, speech amplifier or unkeyed stages of a transmitter, does not require good (low) regulation as long as the proper voltage is obtained under load conditions. The filter capacitors must have a voltage rating safe for the highest value to which the voltage will soar when the external load is removed.

A power supply will show more (higher) regulation with long-term changes in load resistance than with short temporary changes. The regulation with long-term changes is often called the static regulation, to distinguish it from the dynamic regulation (short temporary load changes). A load that varies at a syllabic or keyed rate, as represented by some audio and RF amplifiers, usually requires good dynamic regulation (15% or

less) if distortion products are to be held to a low level. The dynamic regulation of a power supply can be improved by increasing the value of the output capacitor.

When essentially constant voltage regardless of current variation is required (for stabilizing an oscillator, for example), special voltage regulating circuits described later in this chapter are used.

BLEEDER RESISTOR

A bleeder resistor is a resistance connected across the output terminals of the power supply. Its functions are to discharge the filter capacitors as a safety measure when the power is turned off and to improve voltage regulation by providing a minimum load resistance. When voltage regulation is not of importance, the resistance may be as high as 100-W per volt of power supply output voltage. The resistance value to be used for voltage-regulating purposes is discussed in later sections. From the consideration of safety, the power rating of the resistor should be as conservative as possible, since a burned-out bleeder resistor is dangerous!

RIPPLE FREQUENCY AND VOLTAGE

Pulsations at the output of the rectifier can be considered to be the result of an alternating current superimposed on a steady direct current. From this viewpoint, the filter may be considered to consist of shunt capacitors that short circuit the ac component while not interfering with the flow of the dc component. Series chokes will readily pass dc but will impede the flow of the ac component.

The alternating component is called ripple. The effectiveness of the filter can

be expressed in terms of percent ripple, which is the ratio of the RMS value of the ripple to the dc value in terms of percentage.

$$\text{Percent Ripple (RMS)} = \frac{E_1}{E_2} \times 100\% \quad (2)$$

where:

E1 = the RMS value of ripple voltage
E2 = the steady dc voltage.

Any frequency multiplier or amplifier supply in a CW transmitter should have less than 5% ripple. A linear amplifier can tolerate about 3% ripple on the plate voltage. Bias supplies for linear amplifiers should have less than 1% ripple. VFOs, speech amplifiers and receivers may require a ripple no greater than to 0.01%.

Ripple frequency refers to the frequency of the pulsations in the rectifier output waveform—the number of pulsations per second. The ripple frequency of half-wave rectifiers is the same as the line-supply frequency—60 Hz with a 60-Hz supply. Since the output pulses are doubled with a full-wave rectifier, the ripple frequency is doubled—to 120 Hz with a 60-Hz supply.

The amount of filtering (values of inductance and capacitance) required to give adequate smoothing depends on the ripple frequency. More filtering is required as the ripple frequency is reduced.

CAPACITOR-INPUT FILTERS

Capacitor-input filter systems are shown in **Fig 17.12**. Disregarding voltage drops in the chokes, all have the same characteristics except with respect to ripple. Better ripple reduction will be obtained when LC sections are added as shown in Fig 17.12B and C.

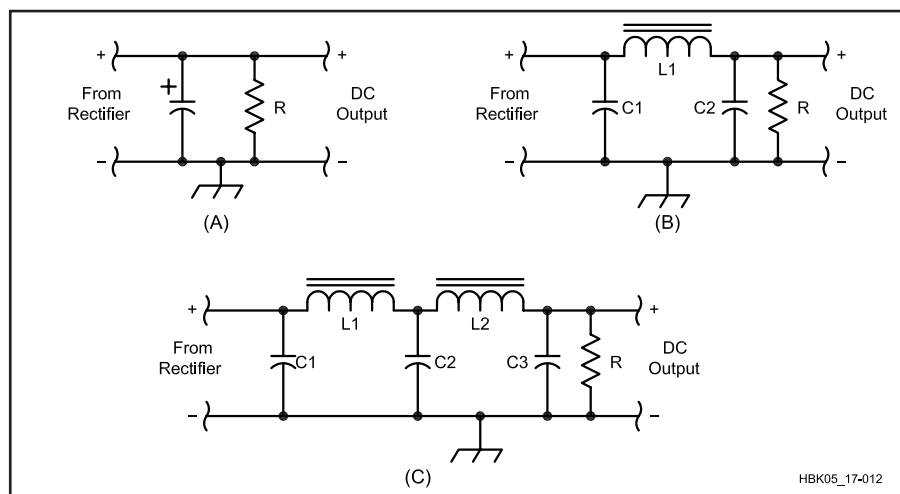


Fig 17.12 — Capacitor-input filter circuits. At A is a simple capacitor filter. B and C are single- and double-section filters, respectively.

Input Versus Output Voltage

The average output voltage of a capacitor-input filter is generally poorly regulated with load-current variations. This is because the rectifier diodes conduct for only a small portion of the ac cycle to charge the filter capacitor to the peak value of the ac waveform. When the instantaneous voltage of the ac passes its peak, the diode ceases to conduct. This forces the capacitor to support the load current until the ac voltage on the opposing diode in the bridge or full wave rectifier is high enough to pick up the load and recharge the capacitor. For this reason, the diode currents are usually quite high.

Since the cyclic peak voltage of the capacitor-filter output is determined by the peak of the input ac waveform, the minimum voltage and, therefore, the ripple amplitude, is determined by the amount of voltage discharge, or “droop,” occurring in the capacitor while it is discharging and supporting the load. Obviously, the higher the load current, the proportionately greater the discharge, and therefore the lower the average output.

Although not exactly accurate, an easy way to determine the peak-to-peak ripple for a certain capacitor and load is to assume a constant load current. We can calculate the droop in the capacitor by using the relationship:

$$C \times E = I \times t \quad (3)$$

where:

C = the capacitance in microfarads,

E = the voltage droop, or peak-to-peak ripple voltage,

I = the load current in milliamperes and

t = the length of time per cycle when the rectifiers are not conducting, and the filter capacitor must support the load current. For 60-Hz, full-wave rectifiers, t is about 7.5 ms.

As an example, let's assume that we need to determine the peak to peak ripple voltage at the dc output of a full-wave rectifier/filter combination that produces 13.8 V dc and supplies a transceiver drawing 2.0 A. The filter capacitor in the power supply is 5000 μ F. Using the above relationship:

$$C \times E = I \times t$$

$$5000 \mu\text{F} \times E = 2000 \text{ mA} \times 7.5 \text{ ms}$$

$$E = \frac{2000 \text{ mA} \times 7.5 \text{ ms}}{5000 \mu\text{F}} = 3 \text{ V P-P}$$

Obviously, this is too much ripple. A capacitor value of about 20000 μ F would be better suited for this application. If a linear regulator is used after this rectifier/filter combination, however, and the source voltage raised to produce a dc voltage of about 20 V, the 5000- μ F capacitor with its 3-V peak-to-peak ripple would work well, since the regulator would remove the ripple content before the output power

was applied to the transceiver.

CHOKE-INPUT FILTERS

Choke-input filters have become less popular than they once were, because of the high surge current capability of silicon rectifiers. Choke-input filters provide the benefits of greatly improved output voltage stability over varying loads and low peak-current surges in the rectifiers. On the negative side, however, the choke is bulky and heavy, and the output voltage is lower than that of a capacitor-input filter.

As long as the inductance of the choke is large enough to maintain a continuous current over the complete cycle of the input ac waveform, the filter output voltage will be the average value of the rectified output. The average dc value of a full-wave rectified sine wave is 0.637 times its peak voltage. Since the RMS value is 0.707 times the peak, the output of the choke input filter will be (0.637 / 0.707), or 0.90 times the RMS ac voltage. For light loads, however, there may not be enough energy stored in the choke during the input waveform crest to allow continuous current over the full cycle. When this happens, the filter output voltage will rise as the filter assumes more and more of the characteristics of a capacitor-input filter.

Choke-input filters see extensive use in the energy-storage networks of switch-mode regulators.

Regulation

The output of a rectifier/filter system may be usable for some electronic equipment, but for today's transceivers and accessories, further measures may be necessary to provide power sufficiently clean and stable for their needs. Voltage regulators are often used to provide this additional level of conditioning.

Rectifier/filter circuits by themselves are unable to protect the equipment from the problems associated with input-power-line fluctuations, load-current variations and residual ripple voltages. Regulators can eliminate these problems, but not without costs in circuit complexity and power-conversion efficiency.

ZENER DIODES

A Zener diode (named after American physicist Dr. Clarence Zener) can be used to maintain the voltage applied to a circuit at a practically constant value, regardless of the voltage regulation of the power supply or variations in load current. The typical

circuit is shown in **Fig 17.13**. Note that the cathode side of the diode is connected to the positive side of the supply. The electrical characteristics of a Zener diode under conditions of forward and reverse voltage are given in the **Real-World Component**

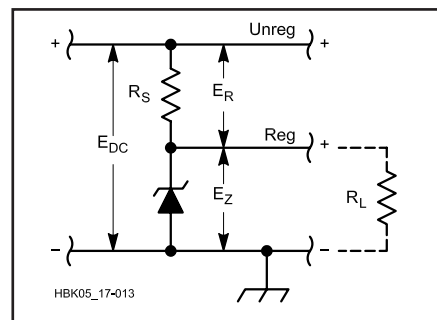


Fig 17.13 — Zener-diode voltage regulation. The voltage from a negative supply may be regulated by reversing the power-supply connections and the diode polarity.

Characteristics chapter.

Zener diodes are available in a wide variety of voltages and power ratings. The voltages range from less than two to a few hundred, while the power ratings (power the diode can dissipate) run from less than 0.25 W to 50 W. The ability of the Zener diode to stabilize a voltage depends on the diode's conducting impedance. This can be as low as 1 Ω or less in a low-voltage, high-power diode or as high as 1000 Ω in a high-voltage, low-power diode.

LINEAR REGULATORS

Linear regulators come in two varieties: *series* and *shunt*. The shunt regulator is simply an electronic (also called “active”) version of the Zener diode. For the most part, the active shunt regulator is rarely used since the series regulator is a superior choice for most applications. **Fig 17.14B** shows a shunt regulator.

The series regulator consists of a stable voltage reference, which is usually established by a Zener diode, a transistor in

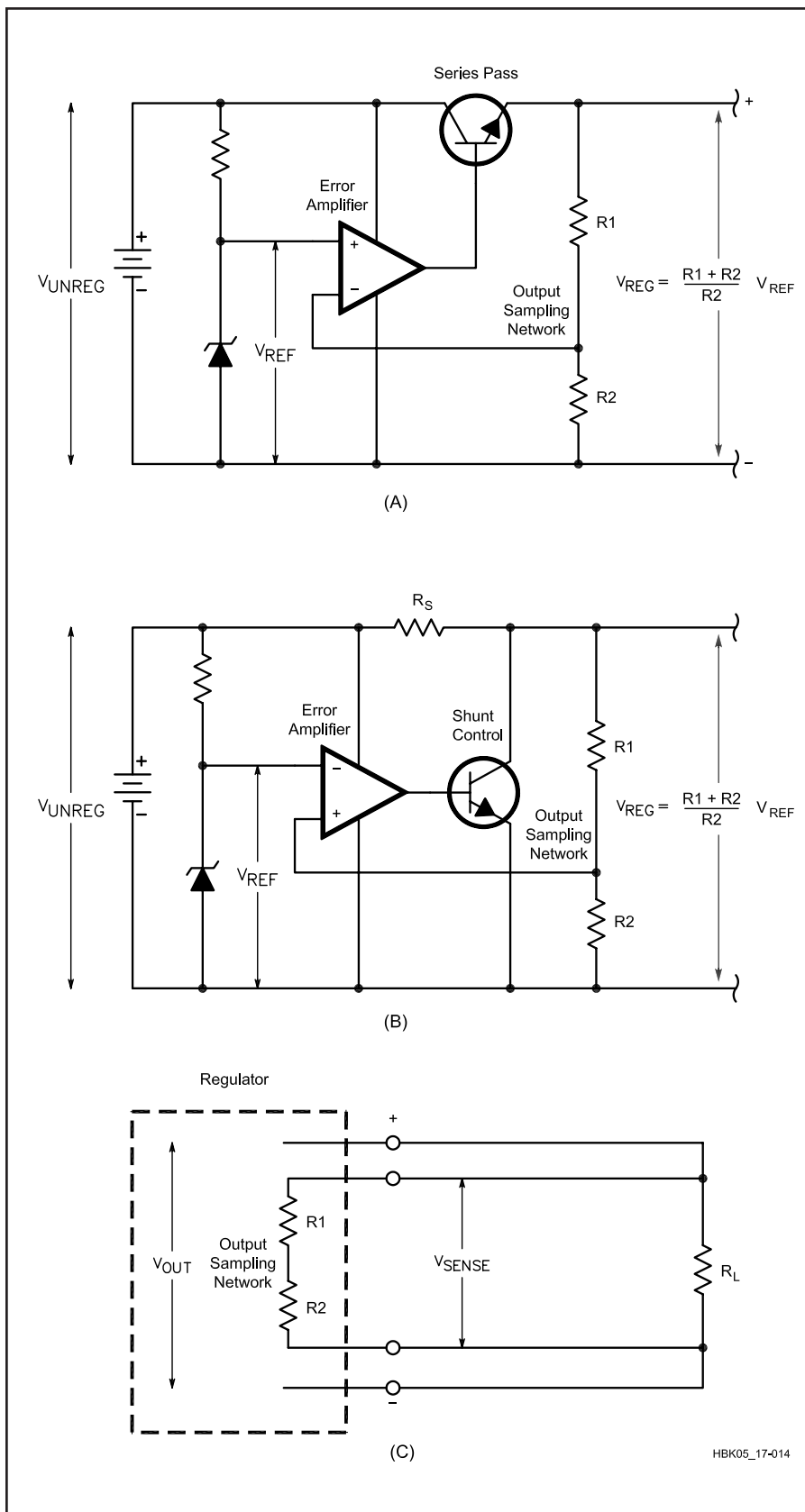


Fig 17.14 — Linear electronic voltage-regulator circuits. In these diagrams, batteries represent the unregulated input-voltage source. A transformer, rectifier and filter would serve this function in most applications. Part A shows a series regulator and Part B shows a shunt regulator. Part C shows how remote sensing overcomes poor load regulation caused by the IR drop in the connecting wires by bringing them inside the feedback loop.

series with the power source and the load (called a *series pass transistor*), and an error amplifier. In critical applications a temperature-compensated reference diode would be used instead of the Zener diode. (See Fig 17.14A.)

The output voltage is sampled by the error amplifier, which compares the output (usually scaled down by a voltage divider) to the reference. If the scaled-down output voltage becomes higher than the reference voltage, the error amplifier reduces the drive current to the pass transistor, thereby allowing the output voltage to drop slightly. Conversely, if the load pulls the output voltage below the desired value, the amplifier drives the pass transistor into increased conduction.

The “stiffness” or tightness of regulation of a linear regulator depends on the gain of the error amplifier and the ratio of the output scaling resistors. In any regulator, the output is cleanest and regulation stiffest at the point where the sampling network or error amplifier is connected. If heavy load current is drawn through long leads, the voltage drop can degrade the regulation at the load. To combat this effect, the feedback connection to the error amplifier can be made directly to the load. This technique, called *remote sensing*, moves the point of best regulation to the load by bringing the connecting loads inside the feedback loop. This is shown in Fig 17.14C.

Input Versus Output Voltage

In a series regulator, the pass-transistor power dissipation is directly proportional to the load current and input/output voltage differential. The series pass element can be located in either leg of the supply. Either NPN or PNP devices can be used, depending on the ground polarity of the unregulated input.

The differential between the input and output voltages is a design tradeoff. If the input voltage from the rectifiers and filter is only slightly higher than the required output voltage, there will be minimal voltage drop across the series pass transistor resulting in minimal thermal dissipation and high power-supply efficiency. The supply will have less capability to provide regulated power in the event of power line brownout and other reduced line voltage conditions, however. Conversely, a higher input voltage will provide operation over a wider range of input voltage, but at the expense of increased heat dissipation.

Pass Transistors

Darlington Pairs

A simple Zener-diode reference or IC op-amp error amplifier may not be able to

source enough current to a pass transistor that must conduct heavy load current. The Darlington configuration of **Fig 17.15A** multiplies the pass-transistor beta, thereby extending the control range of the error amplifier. If the Darlington arrangement is implemented with discrete transistors, resistors across the base-emitter junctions may be necessary to prevent collector-to-base leakage currents in Q1 from being amplified and turning on the transistor pair. These resistors are contained in the envelope of a monolithic Darlington device.

When a single pass transistor is not available to handle the current required from a regulator, the current-handling capability may be increased by connecting two or more pass transistors in parallel. The circuit of Fig 17.15B shows the method of connecting these pass transistors. The resistances in the emitter leads of each transistor are necessary to equalize the currents.

Transistor Ratings

When bipolar (NPN, PNP) power transistors are used in applications in which they are called upon to handle power on a continuous basis, rather than switching, there are four parameters that must be examined to see if any maximum limits are being exceeded. Operation of the transistor outside these limits can easily result in device failure. Unfortunately, not many hams (nor, sometimes, equipment manufacturers) are aware of all these parameters. Yet, for a transistor to provide reliable operation, the circuit designer must be sure not to allow his power supply or amplifier to cause overstress.

The four limits are maximum collector current (I_C), maximum collector-emitter voltage (V_{CEO}), maximum power and second breakdown (I_{SB}). All four of these parameters are graphically shown on the transistor's data sheet on what is known as a Safe Operating Area (SOAR) graph. (See **Fig 17.16**.) The first three of these limits are usually also listed prominently with the other device information, but it is often the fourth parameter that is responsible for the "sudden death" of the power transistor after an extended operating period.

The maximum current limit of the transistor (I_C MAX) is usually the current limit for fusing of the bond wire connected to the emitter, rather than anything pertaining to the transistor chip itself. When this limit is exceeded, the bond wire can melt and open circuit the emitter. On the operating curve, this limit is shown as a horizontal line extending out from the Y-axis (zero volts between collector and emitter) and ending at the voltage point where the constant power limit begins.

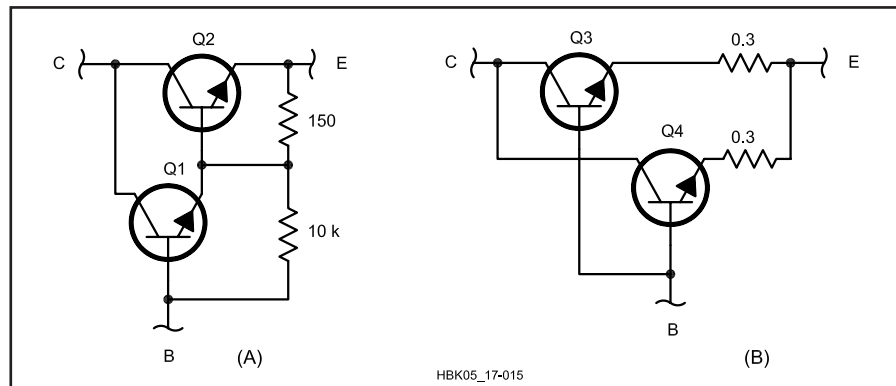


Fig 17.15 — At A, a Darlington-connected transistor pair for use as the pass element in a series-regulating circuit. At B, the method of connecting two or more transistors in parallel for high-current output. Resistances are in ohms. The circuit at A may be used for load currents from 100 mA to 5 A, and the one at B may be used for currents from 6 A to 10 A.

Q1 — Motorola MJE 340 or equivalent

Q2 - Q4 — Power transistor such as 2N3055 or 2N3772

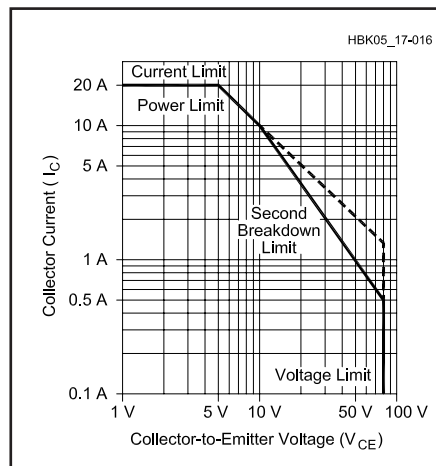


Fig 17.16 — Typical graph of the Safe Operating Area (SOAR) of a transistor. See text for details. Safe operating conditions for specific devices may be quite different from those shown here.

The maximum collector-emitter voltage limit of the transistor (V_{CE} MAX) is the point at which the transistor can no longer stand off the voltage between collector and emitter.

With increasing collector-emitter voltage drop at maximum collector current, a point is reached where the power in the transistor will cause the junction temperature to rise to a level where the device leakage current rapidly increases and begins to dominate. In this region, the product of the voltage drop and the current would be constant and represent the maximum power (P_T) rating for the

transistor; that is, as the voltage drop continues to increase, the collector current must decrease to maintain the power dissipation at a constant value.

With most of the higher voltage rated transistors, a point is reached on the constant power portion of the curve whereby, with further increased voltage drop, the maximum power rating is *not* constant, but decreases as the collector to emitter voltage increases. This decrease in power handling capability continues until the maximum voltage limit is reached.

This special region is known as the forward bias second breakdown (FBSB) area. Reduction in the transistor's power handling capability is caused by localized heating in certain small areas of the transistor junction ("hot spots"), rather than a uniform distribution of power dissipation over the entire surface of the device.

The region of operating conditions contained within these curves is called the Safe Operating Area, or SOAR. If the transistor is always operated within these limits, it should provide reliable and continuous service for a long time.

MOSFET Transistors

The bipolar junction transistor (BJT) is rapidly being replaced by the MOSFET transistor in new power supply designs due to the latter's ease of drive. Just as the BJT comes in both NPN and PNP varieties, the MOSFET is available in N-channel and P-channel types, with the N-channel being the more popular of the two. The N-channel MOSFET is equivalent to the NPN bipolar, and the P-channel is equivalent to the PNP.

There are some considerations that should be observed when using a MOSFET as a linear regulator series pass transistor. Several volts of gate drive are needed in order to start conduction of the device, as opposed to less than one volt for the BJT. MOSFETs are inherently very-high-frequency devices, and will readily oscillate with stray-circuit capacitances. In order to prevent oscillation in the transistor and surrounding circuits, it is common practice to insert a small resistor of about 100 ohms directly in series with the gate of the series-pass transistor to reduce the gate circuit Q.

Overcurrent Protection

Damage to a pass transistor can occur when the load current exceeds the safe amount. **Fig 17.17A** illustrates a simple current-limiter circuit that will protect Q1. All of the load current is routed through R1. A voltage difference will exist across R1; the value will depend on the exact load current at a given time. When the load current exceeds a predetermined safe value, the voltage drop across R1 will forward-bias Q2 and cause it to conduct. Because Q2 is a silicon transistor, the voltage drop across R1 must exceed 0.6 V to turn Q2 on. This being the case, R1 is chosen for a value that provides a drop of 0.6 V when the maximum safe-load current is drawn. In this instance, the drop will be 0.6 V when I_L reaches 0.5 A. R2 protects the base-emitter junction of Q2 from current spikes, or from destruction in the event Q1 fails under short-circuit conditions.

When Q2 turns on, some of the current through R_S flows through Q2, thereby depriving Q1 of some of its base current. This action, depending upon the amount of Q1 base current at a precise moment, cuts off Q1 conduction to some degree, thus limiting the current through it.

Foldback Current Limiting

Under short-circuit conditions, a constant-current-type current limiter must still withstand the full source voltage and limited short-circuit current simultaneously, which can impose a very high-power dissipation or second-breakdown stress on the series pass transistor. For example, a 12-V regulator with current limiting set for 10 A and having a source of 16 V will have a dissipation of 40 W $[(16 \text{ V} - 12 \text{ V}) \times 10 \text{ A}]$ at the point of current limiting (knee). But its dissipation will rise to 160 W under short-circuit conditions $(16 \text{ V} \times 10 \text{ amps})$.

A modification of the limiter circuit can cause the regulated-output current to decrease with decreasing load resistance

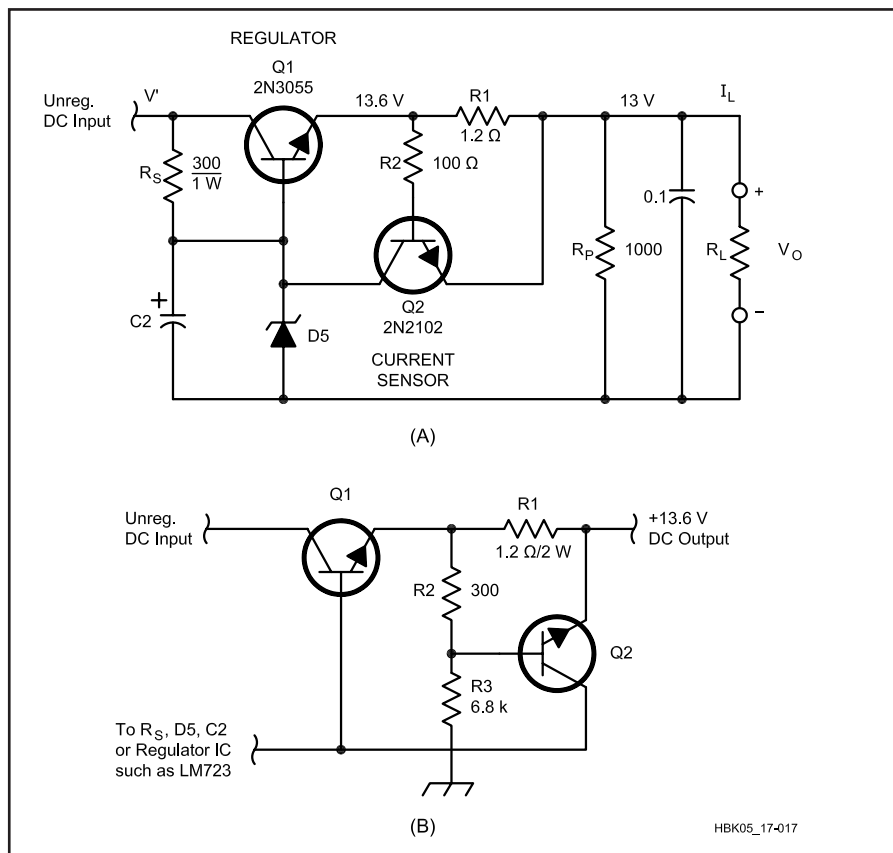


Fig 17.17 — Overload protection for a regulated supply can be implemented by addition of a current-overload-protective circuit, as shown at A. At B, the circuit has been modified to employ current-foldback limiting.

after the over-current knee. With the output shorted, the output current is only a fraction of the knee-current value, which protects the series-pass transistor from excessive dissipation and possible failure. Using the previous example of the 12-V, 10-A regulator, if the short-circuit current is designed to be 3 A (the knee is still 10 A), the transistor dissipation with a short circuit will be only $16 \text{ V} \times 3 \text{ A} = 48 \text{ W}$.

Fig 17.17B shows how the current-limiter example given in the previous section would be modified to incorporate foldback limiting. The divider string formed by R2 and R3 provides a negative bias to the base of Q2, which prevents Q2 from turning on until this bias is overcome by the drop in R1 caused by load current. Since this hold-off bias decreases as the output voltage drops, Q2 becomes more sensitive to current through R1 with decreasing output voltage. See **Fig 17.18**.

The circuit is designed by first calculating the value of R1 for short-circuit current. For example, if 0.5 A is chosen, the value for R1 is simply $0.6 \text{ V} / 0.5 \text{ A} = 1.2 \Omega$ (with the output shorted, the amount of hold-off bias supplied by R2 and R3 is very small and can be neglected). The knee

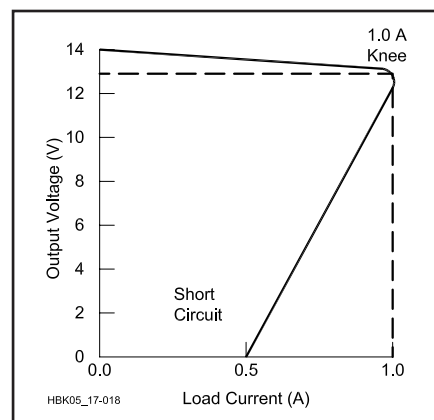


Fig 17.18 — The 1-A regulator shown in Fig 17.17B will fold back to 0.5 A under short-circuit conditions. See text.

current is then chosen. For this example, the selected value will be 1.0 A. The divider string is then proportioned to provide a base voltage at the knee that is just sufficient to turn on Q2 (a value of 13.6 V for 13.0 V output). With 1.0 A flowing through R1, the voltage across the divider will be 14.2 V. The voltage dropped by R2

must then be 14.2 V –13.6 V, or 0.6 V. Choosing a divider current of 2 mA, the value of R2 is then 0.6 V / 0.002 A = 300 Ω. R3 is calculated to be 13.6 V / 0.002 A = 6800 Ω.

“Crowbar” Circuits

Electronic components *do* fail from time to time. In a regulated power supply, the only component standing between an elevated dc source voltage and your rig is one transistor, or a group of transistors wired in parallel. If the transistor, or one of the transistors in the group, happens to short internally, your rig could suffer lots of damage.

To safeguard the rig or other load equipment against possible overvoltage, some power-supply manufacturers include a circuit known as a crowbar. This circuit usually consists of a silicon-controlled rectifier (SCR) connected directly across the output of the power supply, with a voltage-sensing trigger circuit tied to its gate. In the event the output voltage exceeds the trigger set point, the SCR will fire, and the output is short circuited. The resulting high current in the power supply (shorted output in series with a series pass transistor failed short) will blow the power supply’s line fuses. This is both a protection for the supply as well as an indicator that something has malfunctioned internally. For these reasons, never replace blown fuses with ones that have a higher current rating.

IC VOLTAGE REGULATORS

The modern trend in regulators is toward the use of three-terminal devices commonly referred to as *three-terminal regulators*. Inside each regulator is a voltage reference, a high-gain error amplifier, temperature-compensated voltage sensing resistors and a pass element. Many currently available units have thermal shut-down, overvoltage protection and current foldback, making them virtually destruction-proof.

Three-terminal regulators (a connection for unregulated dc input, regulated dc output and ground) are available in a wide range of voltage and current ratings. It is easy to see why regulators of this sort are so popular when you consider the low price and the number of individual components they can replace. The regulators are available in several different package styles, depending on current ratings. Low-current (100 mA) devices frequently use the plastic TO-92 and DIP-style cases. TO-220 packages are popular in the 1.5-A range, and TO-3 cases house the larger 3-A and 5-A devices.

Three-terminal regulators are available

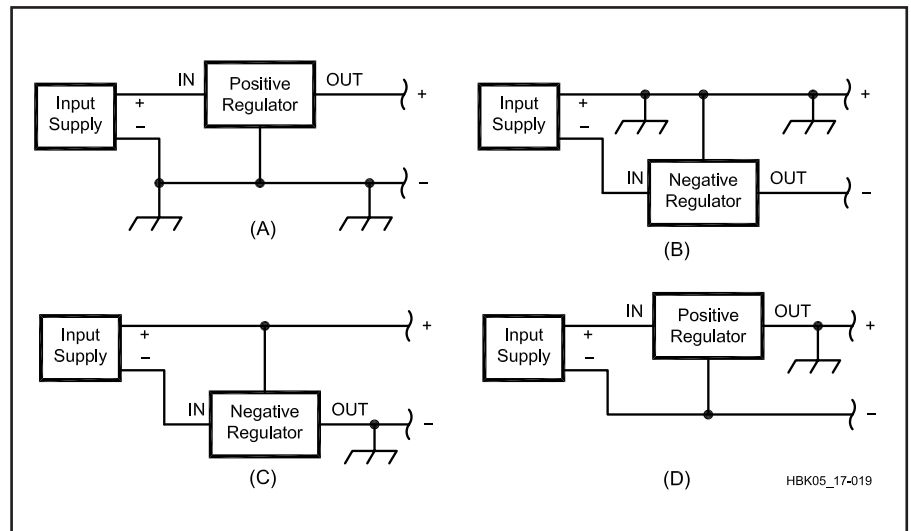


Fig 17.19 — Parts A and B illustrate the conventional manner in which three-terminal regulators are used. Parts C and D show how one polarity regulator can be used to regulate the opposite-polarity voltage.

as positive or negative types. In most cases, a positive regulator is used to regulate a positive voltage and a negative regulator a negative voltage. Depending on the system ground requirements, however, each regulator type may be used to regulate the “opposite” voltage.

Fig 17.19A and B illustrate how the regulators are used in the conventional mode. Several regulators can be used with a common-input supply to deliver several voltages with a common ground. Negative regulators may be used in the same manner. If no other common supplies operate from the input supply to the regulator, the circuits of Fig 17.19C and D may be used to regulate positive voltages with a negative regulator and vice versa. In these configurations the input supply is floated; neither side of the input is tied to the system ground.

Manufacturers have adopted a system of family numbers to classify three-terminal regulators in terms of supply polarity, output current and regulated voltage. For example, National uses the number LM7805C to describe a positive 5-V, 1.5-A regulator; the comparable unit from Texas Instruments is a UA7805KC. LM7812C describes a 12-V regulator of similar characteristics. LM7905C denotes a negative 5-V, 1.5-A device. There are many such families with widely varied ratings available from manufacturers. Fixed-voltage regulators are available with output ratings in most common values between 5 and 28 V. Other families

include devices that can be adjusted from 1.25 to 50 V.

Regulator Specifications

When choosing a three-terminal regulator for a given application, the most important specifications to consider are device output voltage, output current, input-to-output differential voltage, line regulation and power dissipation. Output voltage and current requirements are determined by the load with which the supply will ultimately be used.

Input-to-output differential voltage is one of the most important three-terminal regulator specifications to consider when designing a supply. The differential value (the difference between the voltage applied to the input terminal and the voltage on the output terminal) must be within a specified range. The minimum differential value, usually about 2.5 V, is called the dropout voltage. If the differential value is less than the dropout voltage, no regulation will take place. At the other end of the scale, maximum input-output differential voltage is generally about 40 V. If this differential value is exceeded, device failure may occur.

Increases in either output current or differential voltage produce proportional increases in device power consumption. By employing a safety feature called current foldback, some manufacturers ensure that maximum dissipation will never be exceeded in normal operation. **Fig 17.20** shows the relationship between output current, input-output differential and cur-

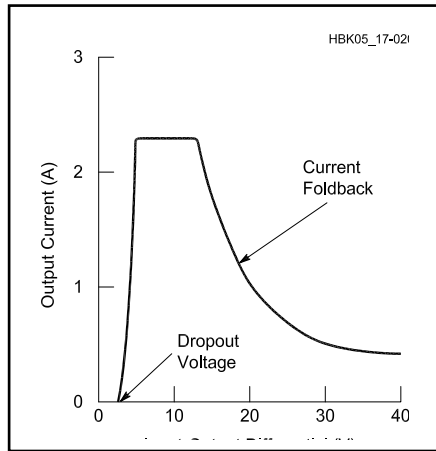


Fig 17.20 — Effects of input-output differential voltage on three-terminal regulator current.

rent limiting for a three-terminal regulator nominally rated for 1.5-A output current. Maximum output current is available with differential voltages ranging from about 2.5 V (dropout voltage) to 12 V. Above 12 V, the output current decreases, limiting the device dissipation to a safe value. If the output terminals are accidentally short circuited, the input-output differential will rise, causing current foldback, and thus preventing the power-supply components from being over stressed. This protective feature makes three-terminal regulators particularly attractive in simple power supplies.

When designing a power supply around a particular three-terminal regulator, input-output voltage characteristics of the regulator should play a major role in selecting the transformer-secondary and filter-capacitor component values. The unregulated voltage applied to the input of the three-terminal device should be higher than the dropout voltage, yet low enough that the regulator does not go into current limiting caused by an excessive differential voltage. If, for example, the regulated output voltage of the device shown in Fig 17.20 was 12, then unregulated input voltages of between 14.5 and 24 would be acceptable if maximum output current is desired.

In use, all but the lowest current regulators generally require an adequate external heat sink because they may be called on to dissipate a fair amount of power. Also, because the regulator chip contains a high-gain error amplifier, bypassing of the input and output leads is essential for stable operation.

Most manufacturers recommend bypassing the input and output directly at the leads where they protrude through the heat sink. Solid tantalum capacitors are usu-

ally recommended because of their good high-frequency capabilities.

External capacitors used with IC regulators may discharge through the IC junctions under certain circuit conditions, and high-current discharges can harm ICs. Look at the regulator data sheet to see whether protection diodes are needed, what diodes to use and how to place them in any particular application.

In addition to fixed-output-voltage ICs, high-current, adjustable voltage regulators are available. These ICs require little more than an external potentiometer for an adjustable output range from 5 to 24 V at up to 5 A. The unit price on these items is only a few dollars, making them ideal for test-bench power supplies. A very popular low current, adjustable output voltage three terminal regulator, the LM317, is shown in Fig 17.21. It develops a steady 1.25-V reference, V_{REF} , between the output and adjustment terminals. By installing $R1$ between these terminals, a constant current, $I1$, is developed, governed by the equation:

$$I1 = \frac{V_{REF}}{R1} \quad (4)$$

Both $I1$ and a 100- μ A error current, $I2$, flow through $R2$, resulting in output voltage V_O . V_O can be calculated using the equation:

$$V_O = V_{REF} \left(1 + \frac{R2}{R1} \right) + I2 \times R2 \quad (5)$$

Any voltage between 1.2 and 37 V may be obtained with a 40-V input by changing the ratio of $R2$ to $R1$. At lower output voltages, however, the available current will be limited by the power dissipation of the regulator.

Fig 17.22 shows one of many flexible applications for the LM317. By adding only one resistor with the regulator, the voltage regulator can be changed into a constant-current source capable of charging NiCd batteries, for example. Design equations are given in the figure. The same precautions should be taken with adjustable regulators as with the fixed-voltage units. Proper heat sinking and lead bypassing are essential for proper circuit operation.

Increasing Regulator Output Current

When the maximum output current from an IC voltage regulator is insufficient to operate the load, discrete power transistors may be connected to increase the current capability. Fig 17.23 shows two methods for boosting the output current of a positive regulator, although the same techniques can be applied to negative regulators.

In A, an NPN transistor is connected as an emitter follower, multiplying the output current capacity by the transistor beta. The shortcoming of this approach is that the base-emitter junction is not inside the feed-back loop. The result is that the output voltage is reduced by the base-emitter

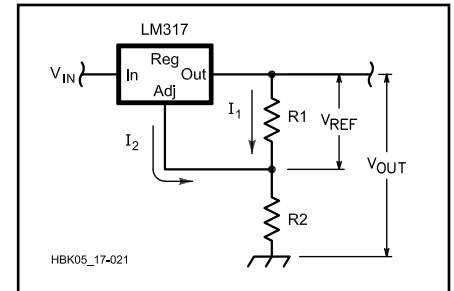


Fig 17.21 — By varying the ratio of $R2$ to $R1$ in this simple LM317 schematic diagram, a wide range of output voltages is possible. See text for details.

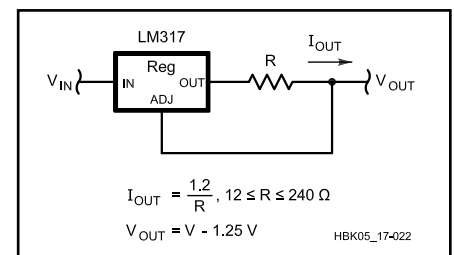


Fig 17.22 — The basic LM317 voltage regulator is converted into a constant-current source by adding only one resistor.

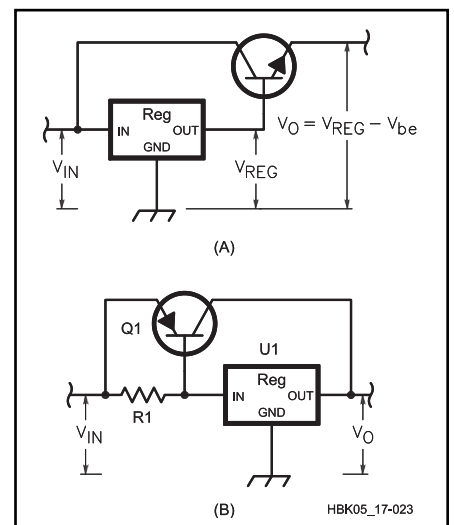


Fig 17.23 — Two methods for boosting the output-current capacity of an IC voltage regulator. Part A shows an NPN emitter follower and B shows a PNP "wrap-around" configuration. Operation of these circuits is explained in the text.

drop, and the load regulation is degraded by variations in this drop.

The circuit at B has a PNP transistor “wrapped around” the regulator. The regulator draws current through the base-emitter junction, causing the transistor to conduct. R1 provides bias voltage for turning on Q1 so that U1 doesn't see the excess current. For example, a 6 Ω resistor will limit the current U1 sees to 100 mA. The IC output voltage is unchanged by the transistor because the collector is connected directly to the IC output (sense point). Any increase in output voltage is detected by the IC regulator, which shuts off its internal-pass transistor, and this stops the boost-transistor base current.

HIGH-PRECISION SERIES REGULATOR LOOP DESIGN

This regulator-loop-design material was contributed by William E. Sabin, WØIYH. (A similar discussion appears in May 1991 *QEX*, pp 3-9.) The discussion here concerns some of the important factors in the design and testing of a series-regulator feedback loop. These techniques were used to design “A Series Regulated 4.5- to 25-V 2.5-A Power Supply,” which appears later in this

chapter. The values and measurements discussed here are from that circuit. **Fig 17.24** is a simplified version of that supply, which is adequate for this discussion.

The series regulator is a good example of a feedback-control system. Open-loop gain and bandwidth, the phase and gain margins and the transient response are important factors. The goal of the design is to maximize the regulator closed-loop performance. One approach is to use a high value of open-loop gain and establish the open-loop frequency response in two ways: (1) an RC low-pass filter consisting of C6, R2, R3, $\frac{1}{2} R_e$ and the output resistances of Q1 and Q2; and (2) a single small capacitor (C4) at the regulator IC. Note that the voltage drop across R2 and R3 is applied to pins 2 and 3 of the LM723 regulator IC, which are used for current limiting. R2 sets the current limit value, and R2's value affects the RC filter.

Test Circuits

Fig 17.24 shows three test circuits. One is an adjustable Load-Test Circuit that can be modulated linearly (almost) by: (1) a sine or triangle wave from a function generator with a dc-offset adjustment (so that the

waveform always has positive polarity), or (2) by a bidirectional square wave. This circuit is used to test the loop response to various load fluctuations. It has proved to be very informative, as discussed later.

The second test circuit (Loop Gain Tester) is inserted into the regulator loop, so that a test signal can be injected into the loop in order to measure the open-loop gain and frequency response. Notice that the loop is closed through the feedback path of R4, R_b and R_a at dc and very low frequencies (less than 0.5 Hz), and the dc-output voltage is reasonably well regulated (which is essential to loop testing). By observing the magnitude (and rate of change) of the frequency response, it is possible to deduce information about phase shift. With this information available, the gain and phase margins (and therefore the regulation, stability, transient response and output impedance) of the closed-loop regulator can be estimated.

The third test circuit is a two-stage op amp preamplifier and oscilloscope. It is used to measure very small signals in the 0.1-Hz to 400-kHz range.

Open-Loop Tests

The test signal applied to points A and

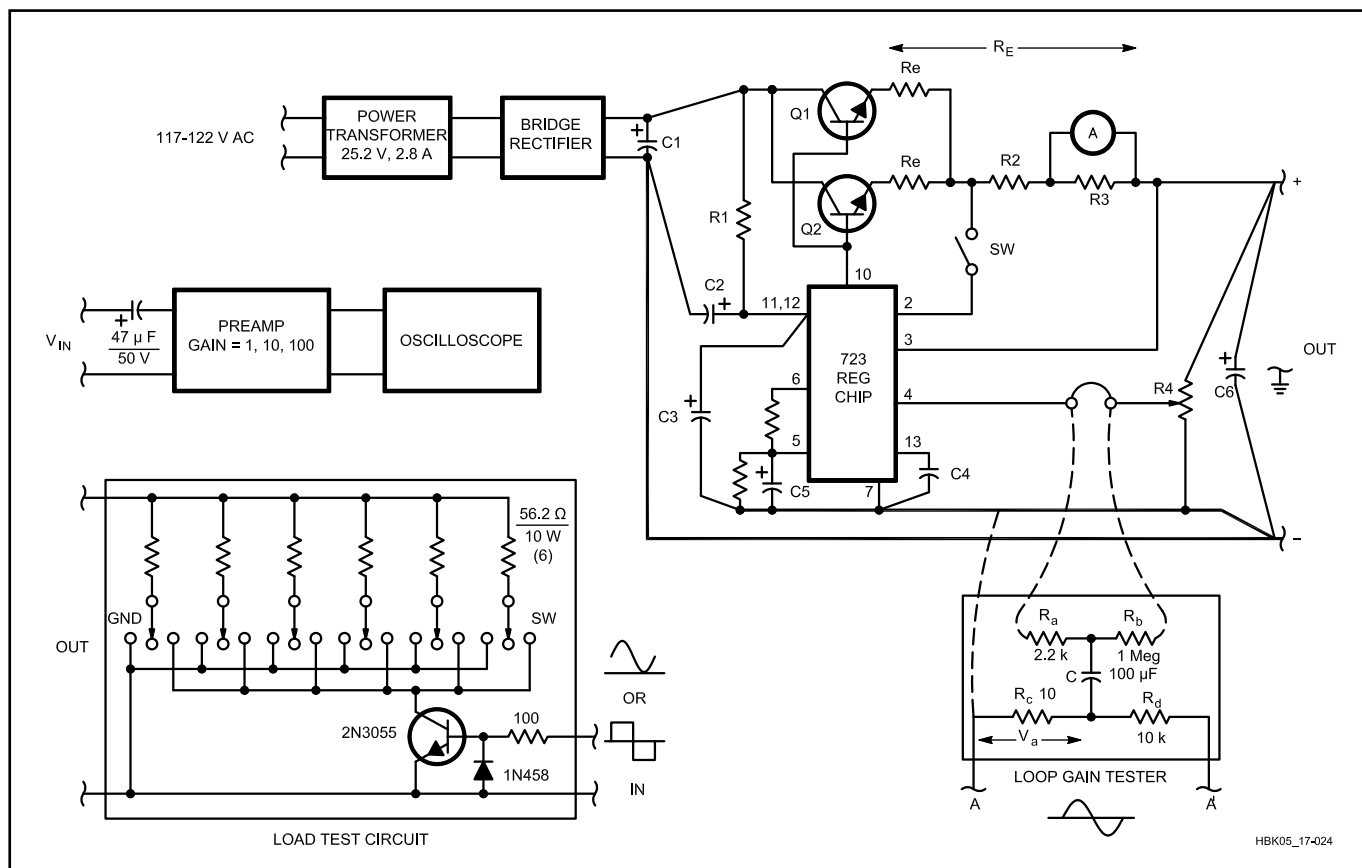


Fig 17.24 — A simplified voltage-regulator feedback loop. The Loop-Gain Tester, Load Tester, Load-Test Circuit and oscilloscope circuits are used to test open-loop response and gain. The heavy lines indicate critical low-impedance circuit paths.

A' is reduced 60 dB by a voltage divider: R_d and R_c . (The voltage division converts convenient input voltages, which we can measure with ordinary equipment, to microvolt levels in the loop.) Capacitor C couples V_a , the voltage across R_c , to the '723 through R_a . R_a is roughly the resistance that the '723 sees in normal operation. The test signal is amplified by at most 74 dB on its way (clockwise around the loop and through the regulator) to the right-hand end of R_b . It is then attenuated 100 dB by R_b and R_c . This means that the "leak-through" back to the '723 input is much smaller than the V_a that we started with, if the frequency is 2 Hz or greater. At dc (and very low frequencies) the regulator functions somewhat normally. Above 2 Hz, then, the magnitude of the open-loop gain at the test frequency is very nearly the ratio $|V_{out}| / |V_a|$.

The first benefit of this test circuit was that it isolated an instability in the '723. The oscillation, at several hundred kHz, was cured by adding C4 (33 pF) and C3 (100 μ F / 50 V with very short leads). Normally, one would suspect an oscillation to involve the overall loop, but this was not the case. This kind of instability is common in feedback control systems: Everything appears to function (usually not to full specification), but an embedded element is not stable.

Open-Loop Frequency Response

Referring to Fig 17.24, the open-loop gain is the product of three factors. The test signal is:

1. Voltage amplified by the regulator IC (about 74 dB for the '723) on its way (clockwise) to the emitters of Q1 and Q2.
 2. Low-pass filtered by C6 and R_E (the combination of $\frac{1}{2} R_c + R_2 + R_3$).
 3. Divided by potentiometer R4.
- For the 2.5-A supply, the greatest open-

loop gain values are 59 dB at 25 V output and 74 dB at 4.5 V.

Fig 17.25 shows the open-loop frequency response to the top of R4 when R_E is set for a 2.5-A current limit. At very low frequencies, the drop-off is due to the gradual closure of the feedback loop, as mentioned above. At higher frequencies, the roll off results from the combined effects of C4 and C6; it occurs at a 6-dB-per-octave rate (within the errors of instrumentation). The cutoff frequency is about 280 Hz, which is:

$$f_{co} = \frac{1}{2 \times \pi \times R_E \times C6} \quad (6)$$

where:

f_{co} = cutoff frequency in Hz

$R_E = 0.57 \Omega$

$C6 = 1000 \mu\text{F}$

For comparison, a reference curve (6 dB per octave at the high and low ends) is superimposed. At about 1.2 kHz or so, the reactance of C6 is roughly equal to its equivalent series resistance (ESR), which is about 0.13 Ω for a small 1000- μ F aluminum-electrolytic capacitor. Beyond this frequency the impedance of C6 does not diminish, and C4 takes over (thereby maintaining the 6-dB-per-octave roll-off rate). Careful measurements and computer simulations of the regulator loop verified that C4 and C6 do, in fact, collaborate quite well in this manner.

This characteristic is the desired effect. At 120 Hz (the major ripple frequency) the loop gain is maximum, so the regulator loop works hard to suppress output ripple. At higher frequencies, the roll-off rate implies a loop phase shift in the neighborhood of 90°, which assures closed-loop stability and good transient response. Closed-loop transient response tests (using a square-wave signal injected into

the Load Test Circuit) verify the absence of ringing or large overshoot.

When R_E is increased to limit at smaller currents, the cutoff frequency decreases. In the example supply, the 0.5-A and 0.1-A range cutoff frequencies are 58 Hz and 12 Hz, respectively, and the roll-off rate remains 6 dB per octave as before. Hence, the loop gain at 120 Hz is reduced. The ripple voltage across C1, however, is also greatly reduced at lighter load currents. In the end, output ripple remains very low.

Closed-Loop Response

The closed-loop gain of the regulator is:

$$G_{CL} = 20 \log \left(\frac{V_{out}}{V_{ref}} \right) \quad (7)$$

where:

G_{CL} = closed-loop gain, in dB

V_{out} = output voltage

V_{ref} = reference voltage.

Here, V_{out} is 4.5 V, minimum (25.0 V, maximum) and V_{ref} is 4.5 V. Fig 17.25 shows the locations of the minimum and maximum gain values and also the corresponding closed-loop bandwidths. By locating the 280-Hz cutoff frequency fairly close to the 120-Hz ripple frequency, the closed-loop bandwidth is minimized, which is desirable in a voltage regulator.

Another important regulator parameter is closed-loop output impedance. **Fig 17.26** shows a computer simulation of this parameter. Mathematical analysis and actual measurements using the Load Test Circuit with a sine-wave test signal corroborate the simulations quite well. Two results are shown. For curve A, the C6 component (of Fig 17.24) is removed from the circuit, and C4 is increased so that the 280-Hz cutoff frequency is maintained, as

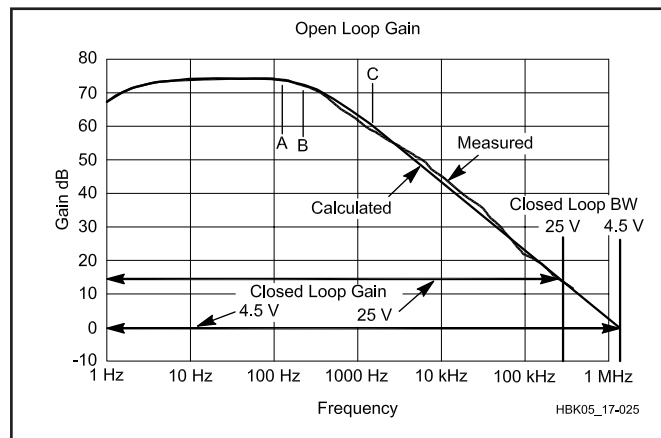


Fig 17.25 — The open-loop frequency-response curves of the voltage-regulator feedback loop. Point A is 120 Hz; point B is 280 Hz; point C is 1.2 kHz (above 1.2 kHz, C6 is no longer

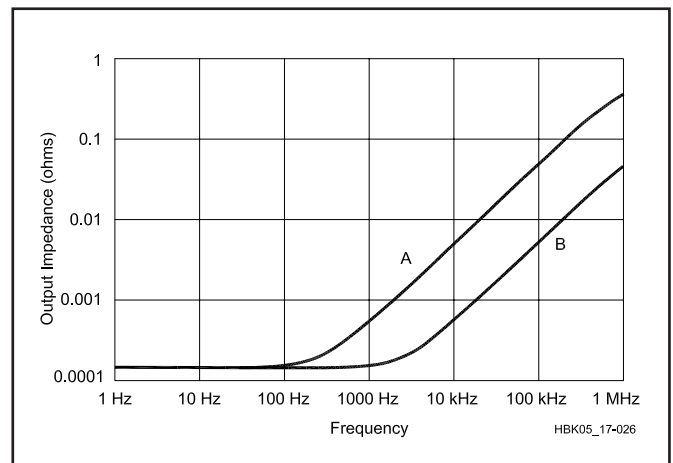


Fig 17.26 — Output impedance magnitude for the voltage-regulator feedback loop.

we discussed before. At low frequencies, the output impedance should be R_E ($0.57\ \Omega$) divided by the open-loop voltage gain (5000 maximum), about $0.11\ \text{m}\Omega$. Above 280 Hz, though, the output impedance increases rapidly because the open-loop gain is decreasing. It will eventually reach the value of R_E .

For curve B, the original values of C6 and C4 are used, and the output impedance remains low up to about 1.2 kHz. It then increases, but remains much lower than curve A. This happens because C4 is smaller than in curve

A and C4 mainly determines the frequency characteristic. In other words, the impedance of C6 (its reactance plus its ESR) is in parallel with the relatively small output impedance of a high-gain feedback amplifier. Therefore, C4 is much less influential in determining the power-supply output impedance. This situation gradually changes as frequency increases.

This discussion shows that the output-impedance characteristic of the power supply is reduced at frequencies that are significant in certain applications. Furthermore, it can be reduced by feedback to levels that are

impossible with practical capacitors. To take advantage of this lower impedance, the regulator must be located extremely close to the load (remote sensing is another possibility).

When extremely tight regulation and low-output impedance are important, the leads to the load must be very short, heavy straps. Multiple loads should be connected in parallel directly at the binding posts: A “daisy-chain” connection scheme does not assure equal regulation for each load; it counteracts precision regulation.

High-Voltage Techniques

The construction of high-voltage supplies poses special considerations in addition to the normal design and construction practices used for lower-voltage supplies. In general, the constructor needs to remember that physical spacing between leads, connections, parts and the chassis must be sufficient to prevent arcing. Also, the series connection of components such as capacitor and resistor strings needs to be done with consideration for voltage stresses in the components.

CAPACITORS

Capacitors will usually need to be connected in series strings to form an equivalent capacitor with the capability to withstand the applied voltage. When this is done, equal-value bypassing resistors need to be connected across each capacitor in the string in order to distribute the voltage equally across the capacitors. The *equalizing resistors* should have a value low enough to equalize differences in capacitor leakage resistance between the capacitors, while high enough not to dissipate excessive power. Also, capacitor bodies need to be insulated from the chassis and from each other by mounting them on insulating panels, thereby preventing arcing to the chassis or other capacitors in the string.

For high voltages, oil-filled paper-dielectric capacitors are superior to elec-

trolytics because they have lower internal impedance at high frequencies, lower leakage resistance and are available with higher working voltages. These capacitors are available in values of several microfarads and have working voltage ratings of thousands of volts. Avoid older oil-filled capacitors. They may contain polychlorinated biphenyls (PCBs), a known cancer-causing agent. Newer capacitors have eliminated PCBs and have a notice on the case to that effect.

BLEEDER RESISTORS

Bleeder resistors should be given careful consideration. These resistors provide protection against shock when the power supply is turned off and dangerous wiring is exposed. A general rule is that the bleeder should be designed to reduce the output voltage to 30 V or less within 2 seconds of turning off the power supply. Take care to ensure that the maximum voltage rating of the resistor is not exceeded. The bleeder will consist of several resistors in series. One additional recommendation is that two separate bleeder strings be used, to provide safety in the event one of the strings fails.

METERING TECHNIQUES

Special considerations should be observed for metering of high-voltage supplies, such as the plate supplies for linear

amplifiers. This is to provide safety to both personnel and also to the meters themselves.

To monitor the current, it is customary to place the ammeter in the supply return (ground) line. This ensures that both meter terminals are close to ground potential, as compared to the hazard created by placing the meter in the positive output line — in which case the voltage on each meter terminal would be near the full high-voltage potential. Also, there is the strong possibility that an arc could occur between the wiring and coils inside the meter and the chassis of the amplifier or power supply itself. This hazardous potential cannot exist with the meter in the negative leg. Another good safety practice is to place a low-voltage Zener diode across the terminals of the ammeter. This will bypass the meter in the event of an internal open circuit in the meter.

For metering of high voltage, the builder should remember that resistors to be used in multiplier strings have voltage-breakdown ratings. Usually, several resistors need to be used in series to reduce voltage stress across each resistor. A basic rule of thumb is that resistors should be limited to a maximum of 200 V, unless rated otherwise. Therefore, for a 2000-V power supply, the voltmeter would have a string of 10 resistors connected in series to distribute the voltage equally.

Batteries and Charging

The availability of solid-state equipment makes it practical to use battery power under portable or emergency conditions. Hand-held transceivers and instruments are obvious applications, but even fairly powerful transceivers (100 W or so output) may be practical users of battery power

(for example, emergency power for the home station for ARES operation).

Lower-power equipment can be powered from two types of batteries. The “primary” battery is intended for one-time use and is then discarded; the “storage” (or “secondary”) battery may be recharged

many times.

A battery is a group of chemical cells, usually series-connected to give some desired multiple of the cell voltage. Each assortment of chemicals used in the cell gives a particular nominal voltage. This must be taken into account to make up a

particular battery voltage. For example, four 1.5-V carbon-zinc cells make a 6-V battery and six 2-V lead-acid cells make a 12-V battery. The **Electrical Fundamentals** chapter has more information about energy storage in batteries. In addition, the **Real-World Component Characteristics** chapter has information about battery capacity and charge/discharge rates.

PRIMARY BATTERIES

One of the most common primary-cell types is the alkaline cell, in which chemical oxidation occurs during discharge. When there is no current, the oxidation essentially stops until current is required. A slight amount of chemical action does continue, however, so stored batteries eventually will degrade to the point where the battery will no longer supply the desired current. The time taken for degradation without battery use is called *shelf life*.

The alkaline battery has a nominal voltage of 1.5 V. Larger cells are capable of producing more milliampere hours and less voltage drop than smaller cells. Heavy-duty and industrial batteries usually have a longer shelf life.

Lithium primary batteries have a nominal voltage of about 3 V per cell and by far the best capacity, discharge, shelf-life and temperature characteristics. Their disadvantages are high cost and the fact that they cannot be readily replaced by other types in an emergency.

The lithium-thionyl-chloride battery is a primary cell, and should not be recharged under any circumstances. The charging process vents hydrogen, and a catastrophic hydrogen explosion can result. Even accidental charging caused by wiring errors or a short circuit should be avoided.

Silver oxide (1.5 V) and mercury (1.4 V) batteries are very good where nearly constant voltage is desired at low currents for long time periods. Their main use (in subminiature versions) is in hearing aids, though they may be found in other mass-produced devices such as household smoke alarms.

SECONDARY OR RECHARGEABLE BATTERIES

Many of the chemical reactions in primary batteries are theoretically reversible if current is passed through the battery in the reverse direction.

Primary batteries should not be recharged for two reasons: It may be dangerous because of heat generated within sealed cells, and even in cases where there may be some success, both the charge and life are limited. One type of alkaline battery is rechargeable, and is so marked.

Nickel Cadmium

The most common type of small rechargeable battery is the nickel-cadmium (NiCd), with a nominal voltage of 1.2 V per cell. Carefully used, these are capable of 500 or more charge and discharge cycles. For best life, the NiCd battery must not be fully discharged. Where there is more than one cell in the battery, the most-discharged cell may suffer polarity reversal, resulting in a short circuit, or seal rupture. All storage batteries have discharge limits, and NiCd types should not be discharged to less than 1.0 V per cell. There is a popular belief that it is necessary to completely discharge NiCd cells in order to recharge them to full capacity. Called the “memory effect,” professional engineers have proved this to be a myth.

Nickel-cadmium cells are not limited to “D” cells and smaller sizes. They also are available in larger varieties ranging to mammoth 1000 Ah units having carrying handles on the sides and caps on the top for adding water, similar to lead-acid types. These large cells are sold to the aircraft industry for jet-engine starting, and to the railroads for starting locomotive diesel engines. They also are used extensively for uninterruptible power supplies. Although expensive, they have very long life. Surplus cells are often available through surplus electronics dealers, and these cells often have close to their full rated capacity.

Advantages for the ham in these vented-cell batteries lie in the availability of high discharge current to the point of full discharge. Also, cell reversal is not the problem that it is in the sealed cell, since water lost through gas evolution can easily be replaced. Simply remove the cap and add distilled water. By the way, tap water should never be added to either nickel-cadmium or lead-acid cells, since dissolved minerals in the water can hasten self discharge and interfere with the electrochemical process.

Lead Acid

The most widely used high-capacity rechargeable battery is the lead-acid type. In automotive service, the battery is usually expected to discharge partially at a very high rate, and then to be recharged promptly while the alternator is also carrying the electrical load. If the conventional auto battery is allowed to discharge fully from its nominal 2 V per cell to 1.75 V per cell, fewer than 50 charge and discharge cycles may be expected, with reduced storage capacity.

The most attractive battery for extended high-power electronic applications is the so-called “deep-cycle” battery, which is

intended for such uses as powering electric fishing motors and the accessories in recreational vehicles. Size 24 and 27 batteries furnish a nominal 12 V and are about the size of small and medium automotive batteries. These batteries may furnish between 1000 and 1200 W-hr per charge at room temperature. When properly cared for, they may be expected to last more than 200 cycles. They often have lifting handles and screw terminals, as well as the conventional truncated-cone automotive terminals. They may also be fitted with accessories, such as plastic carrying cases, with or without built-in chargers.

Lead-acid batteries are also available with gelled electrolyte. Commonly called *gel cells*, these may be mounted in any position if sealed, but some vented types are position sensitive.

Lead-acid batteries with liquid electrolyte usually fall into one of three classes — conventional, with filling holes and vents to permit the addition of distilled water lost from evaporation or during high-rate charge or discharge; maintenance-free, from which gas may escape but water cannot be added; and sealed. Generally, the deep-cycle batteries have filling holes and vents.

Nickel Metal Hydride

This battery type is quite similar to the NiCd, but the Cadmium electrode is replaced by one made from a porous metal alloy that traps hydrogen; therefore the name of metal hydride. Many of the basic characteristics of these cells are similar to NiCds. For example, the voltage is very nearly the same, they can be slow-charged from a constant current source, and they can safely be deep cycled. There are also some important differences: The most attractive feature is a much higher capacity for the same cell size — often nearly twice as much as the NiCd types! The typical size AA NiMH cell has a capacity between 1000 and 1300 mAh, compared to the 600 to 830 mAh for the same size NiCd. Another advantage of these cells is a complete freedom from memory effect. We can also find comfort in the fact that NiMH cells do not contain any dangerous substances, while both NiCd and lead-acid cells do contain quantities of toxic heavy metals.

The internal resistance of NiMH cells is somewhat higher than that of NiCd cells, resulting in reduced performance at very high discharge current. This can cause slightly reduced power output from an HT powered by a NiMH pack, but the effect is barely noticeable, and the higher capacity and resulting longer run time far outweigh this. At least one manufacturer warns that

the self-discharge of NiMH cells is higher than for NiCd, but again, in practice this can hardly be noticed. The fast-charge process is different for NiMH batteries. A fast charger designed for NiCd will not correctly charge NiMH batteries. But many commercial fast chargers are designed for both types of batteries. NiMH batteries outperform NiCd batteries whenever high capacity is desired, while NiCd batteries still have advantages when delivering very high peak currents.

At the time of this writing, many cell phones and portable computers use NiMH batteries, and several manufacturers offer NiMH packs for Amateur Radio applications. Standard-sized NiMH cells are widely available from the major electronic parts suppliers.

Lithium-Ion Cells

The lithium-ion cell is another possible alternative to NiCd cells. It features, for the same energy storage, about one third the weight and one half the volume of a NiCd. It also has a lower self-discharge rate. Typically, at room temperature, a NiCd cell will lose from 0.5 to 2% of its charge per day. The Lithium-ion cell will lose less than 0.5% per day and even this loss rate decreases after about 10% of the charge has been lost. At higher temperatures the difference is even greater. The result is that Lithium-ion cells are a much better choice for standby operation where frequent recharge is not available.

One major difference between NiCd and Li-ion cells is the cell voltage. The nominal voltage for a NiCd cell is about 1.2 V. For the Li-ion cell it is 3.6 V with a maximum cell charging voltage of 4 V. You cannot substitute Li-ion cells directly for NiCd cells. You will need one Li-ion cell for three NiCd cells. Chargers intended for NiCd batteries must not be used with Li-ion batteries, and vice versa.

PROS AND CONS

Chemical Hazards of Each Battery Type

In addition to the precautions given above, the following precautions are recommended. (Always follow the manufacturer's advice.)

Gas escaping from storage batteries may be explosive. Keep flames or lighted tobacco products away.

Dry-charged storage batteries should be given electrolyte and allowed to soak for at least half an hour. They should then be charged at about a 15 A rate for 15 minutes or so. The capacity of the battery will build up slightly for the first few cycles of charge and discharge, and then have fairly constant

capacity for many cycles. Slow capacity decrease may then be noticed.

No battery should be subjected to unnecessary heat, vibration or physical shock. The battery should be kept clean. Frequent inspection for leaks is a good idea. Electrolyte that has leaked or sprayed from the battery should be cleaned from all surfaces. The electrolyte is chemically active and electrically conductive, and may ruin electrical equipment. Acid may be neutralized with sodium bicarbonate (baking soda), and alkalis may be neutralized with a weak acid such as vinegar. Both neutralizers will dissolve in water, and should be quickly washed off. Do not let any of the neutralizer enter the battery.

Keep a record of the battery use, and include the last output voltage and (for lead-acid storage batteries) the hydrometer reading. This allows prediction of useful charge remaining, and the recharging or procuring of extra batteries, thus minimizing failure of battery power during an excursion or emergency.

Internal Resistance

Cell internal resistance is very important to handheld-transceiver users. This is because the internal resistance is in series with the battery's output and therefore reduces the available battery voltage at the high discharge currents demanded by the transmitter. The result is reduced transmitter output power and power wasted in the cell itself by internal heating. Because of cell-construction techniques and battery chemistry, certain types of cells typically have lower internal resistance than others.

The NiCd cell is the undisputed king of cell types for high discharge current capability. Also, the NiCd maintains this low internal resistance throughout its discharge curve, because the specific gravity of its potassium-hydroxide electrolyte does not change.

Next in line is probably the alkaline primary cell. When these cells are used with handheld transceivers, it is not uncommon to have lower output power, and often to have the low battery indicator come on, even with fresh cells.

The lead-acid cell, which is finding popularity in belt-hung battery packs, is pretty close to the alkaline cell for internal resistance, but this is only at full charge. Unlike the NiCd, the electrolyte in the lead-acid cell enters into the chemical reaction. During discharge, the specific gravity of the electrolyte gradually drops as it approaches water, and the conductivity decreases. Therefore, as the lead-acid cell approaches a discharged state, the internal resistance increases. For the belt pack,

larger cells are used (approximately 2 Ah) and the internal resistance is consequently reduced.

The worst cell of all is the common carbon-zinc flashlight cell. With the transmit current demand levels of handheld radios, these cells are pretty much useless.

BATTERY CAPACITY

The common rating of battery capacity is ampere hours (Ah), the product of current drain and time. The symbol "C" is commonly used; C/10, for example, would be the current available for 10 hours continuously. The value of C changes with the discharge rate and might be 110 at 2 A but only 80 at 20 A. **Fig 17.27** gives capacity-to-discharge rates for two standard-size lead-acid batteries. Capacity may vary from 35 mAh for some of the small hearing-aid batteries to more than 100 Ah for a size 28 deep-cycle storage battery.

Sealed primary cells usually benefit from intermittent (rather than continuous) use. The resting period allows completion of chemical reactions needed to dispose of by-products of the discharge.

The output voltage of all batteries drops as they discharge. "Discharged" condition for a 12-V lead-acid battery, for instance, should not be less than 10.5 volts. It is also good to keep a running record of hydrometer readings, but the conventional readings of 1.265 charged and 1.100 discharged apply only to a long, low-rate discharge. Heavy loads may discharge the battery with little reduction in the hydrometer reading.

Batteries that become cold have less of their charge available, and some attempt to keep a battery warm before use is worthwhile. A battery may lose 70% or more of its capacity at cold extremes, but it will recover with warmth. All batteries have some tendency to freeze, but those

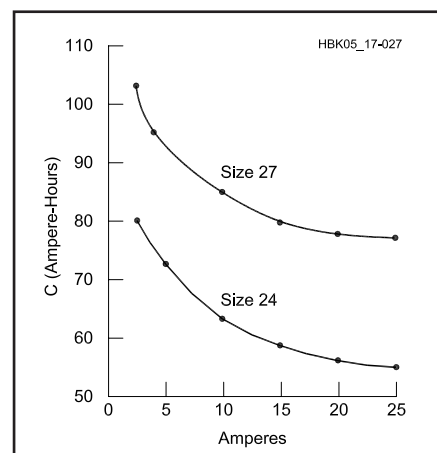


Fig 17.27 — Output capacity as a function of discharge rate for two sizes of lead-acid batteries.

with full charges are less susceptible. A fully charged lead-acid battery is safe to -30°F (-34°C) or colder. Storage batteries may be warmed somewhat by charging. Blowtorches or other flame should never be used to heat any type of battery.

A practical discharge limit occurs when the load will no longer operate satisfactorily on the lower output voltage near the “discharged” point. Much gear intended for “mobile” use may be designed for an average of 13.6 V and a peak of perhaps 15 V, but will not operate well below 12 V. For full use of battery charge, the gear should operate well (if not at full power) on as little as 10.5 V with a nominal 12 to 13.6-V rating.

Somewhat the same condition may be seen in the replacement of carbon-zinc cells by NiCd storage cells. Eight carbon-zinc cells will give 12 V, while 10 of the same size NiCd cells are required for the same voltage. If a 10-cell battery holder is used, the equipment should be designed for 15 V in case the carbon-zinc units are plugged in.

Discharge Planning

Transceivers usually drain a battery at two or three rates: one for receiving, one for transmit standby and one for key-down or average voice transmit. Considering just the first and last of these (assuming the transmit standby is equal to receive), average two-way communication would require the low rate $\frac{3}{4}$ of the time and the high rate $\frac{1}{4}$ of the time. The ratio may vary somewhat with voice. The user may calculate the percentage of battery charge used in an hour by the combination (sum) of rates. If, for example, 20% of the battery capacity is used in an hour, the battery will provide five hours of communications per charge. In most actual traffic and DX-chasing situations the time spent listening should be much greater than that spent transmitting.

Charging/Discharging Requirements

The rated full charge of a battery, C, is expressed in ampere-hours. No battery is perfect, so more charge than this must be offered to the battery for a full-charge. If, for instance, the charge rate is 0.1 C (the 10-hour rate), 12 or more hours may be needed for the charge.

Basically NiCd batteries differ from the lead-acid types in the methods of charging. It is important to note these differences,

since improper charging can drastically shorten the life of a battery. NiCd cells have a flat voltage-versus-charge characteristic until full charge is reached; at this point the charge voltage rises abruptly. With further charging, the electrolyte begins to break down and oxygen gas is generated at the positive (nickel) electrode and hydrogen at the negative (cadmium) electrode.

Since the cell should be made capable of accepting an overcharge, battery manufacturers typically prevent the generation of hydrogen by increasing the capacity of the cadmium electrode. This allows the oxygen formed at the positive electrode to reach the metallic cadmium of the negative electrode and reoxidize it. During overcharge, therefore, the cell is in equilibrium. The positive electrode is fully charged and the negative electrode less than fully charged, so oxygen evolution and recombination “wastes” the charging power being supplied.

In order to ensure that all cells in a NiCd battery reach a fully-charged condition, NiCd batteries should be charged by a constant current at about a 0.1-C current level. This level is about 50 mA for the AA-size cells used in most hand-held radios. This is the optimum rate for most NiCds since 0.1 C is high enough to provide a full charge, yet it is low enough to prevent over-charge damage and provide good charge efficiency.

Although fast-charge-rate (3 to 5 hours typically) chargers are available for hand-held transceivers, they should be used with care. The current delivered by these units is capable of causing the generation of large quantities of oxygen in a fully charged cell. If the generation rate is greater than the oxygen recombination rate, pressure will build in the cell, forcing the vent to open and the oxygen to escape. This can eventually cause drying of the electrolyte, and then cell failure. The cell temperature can also rise, which can shorten cell life. To prevent overcharge from occurring, fast-rate chargers should have automatic charge-limiting circuitry that will switch or taper the charging current to a safe rate as the battery reaches a fully-charged state.

Gelled-electrolyte lead-acid batteries provide 2.4 V/cell when fully charged. Damage results, however, if they are overcharged. (Avoid constant-current or trickle charging unless battery voltage is monitored and charging is terminated when a full charge is reached.) Voltage-limited charging is

best for these batteries. A proper charger maintains a safe charge-current level until 2.3 V/cell is reached (13.8 V for a 12-V battery). Then, the charge current is tapered off until 2.4 V/cell is reached. Once charged, the battery may be safely maintained at the “float” level, 2.3 V/cell. Thus, a 12-V gel-cell battery can be “floated” across a regulated 13.8-V system as a battery backup in the event of power failure.

Deep-cycle lead-acid cells are best charged at a slow rate, while automotive and some NiCd types may safely be given quick charges. This depends on the amount of heat generated within each cell, and cell venting to prevent pressure build-up. Some batteries have built-in temperature sensing, used to stop or reduce charging before the heat rise becomes a danger. Quick and fast charges do not usually allow gas recombination, so some of the battery water will escape in the form of gas. If the water level falls below a certain point, acid hydrometer readings are no longer reliable. If the water level falls to plate level, permanent battery damage may result.

Overcharging NiCds in moderation causes little loss of battery life. Continuous overcharge, however, may generate a voltage depression when the cells are later discharged. For best results, charging of NiCd cells should be terminated after 15 hours at the slow rate. Better yet, circuitry may be included in the charger to stop charging, or reduce the current to about 0.02 C when the 1.43-V-per-cell terminal voltage is reached. For lead-acid batteries, a timer may be used to run the charger to make up for the recorded discharge, plus perhaps 20%. Some chargers will switch over automatically to an acceptable standby charge.

Solar Charging Systems

Price and availability make solar panels an attractive way to maintain the charge on your batteries. Relatively small, low-power solar arrays provide a convenient way to charge a NiCd or sealed-lead-acid battery for emergency and portable operation. This is especially popular with QRP operators. You should always connect some type of charge controller between the battery and the solar array. This will prevent overcharging the battery, and the possible resulting battery damage. The Micro M+ described in the projects section of this chapter is a suitable charge controller.

Emergency Operations

CARE AND FEEDING OF GENERATORS

For long-term-emergency operation, a generator is a must, as anyone who has operated field day can attest to. The generator will provide power as long as the fuel supply holds out. Proper care is necessary to keep the generator operating reliably, however.

When the generator runs out of fuel, the operator may be tempted to rush over with the gasoline can and begin refueling. This is very hazardous, since the engine's manifold and muffler are at temperatures that can ignite spilled gasoline. The operator should wait a few minutes to allow hot surfaces to cool sufficiently to ensure safety. For these periods when the generator is shut down,

plan on having battery power available to support station operation until the generator can be brought back on line.

Check the level of the engine's lubricating oil from time to time. If the oil sump becomes empty, the engine can seize, putting the station out of operation and necessitating costly engine repairs.

Remember that the engine will produce carbon monoxide gas while it is running. The generator should never be run indoors, and should be placed away from open windows and doors to keep exhaust fumes from coming inside.

INVERTERS

For battery-powered operation of alternating-current loads, inverters are avail-

able. An inverter is a dc-to-ac converter, switching at 60 Hz to provide 120-V ac to the loads.

Inverters come in varying degrees of sophistication. The simplest, as mentioned above, produces a square-wave output. This is no problem for lighting and other loads that don't care about the input waveform. Lots of equipment using motors will work poorly or not at all when supplied with square wave power. Therefore, many higher-power inverters use waveform shaping to approximate a sine-wave output. The simplest of these methods is a resonant inductor and capacitor filter. Higher-power units employ pulse-width modulation of the converter switches to create a sinusoidal output waveform.

Power-Supply Projects

Construction of a power supply can be one of the most rewarding projects undertaken by a radio amateur. Whether it's a charger for the NiCd's in a VHF hand-held transceiver, a low-voltage, high-current monster for a new 100-W solid-state transceiver, or a high-voltage supply for a new linear amplifier, a power supply is basic to all of the radio equipment we operate and enjoy. Final testing and adjustment of most power-supply projects requires only a voltmeter, and perhaps an oscilloscope — tools commonly available to most amateurs.

General construction techniques that may be helpful in building the projects in this chapter are outlined in the **Circuit Construction** chapter. Other chapters in this *Handbook* contain basic information about the components that make up power supplies.

Safety must always be carefully considered during design and construction of any power supply. Power supplies contain potentially lethal voltages, and care must be taken to guard against accidental exposure. For example, electrical tape, insulated tubing (spaghetti) or heat-shrink tubing is recommended for covering exposed wires, components leads, component solder terminals and tie-down points. Whenever possible, connectors used to mate the power supply to the outside world should be of an insulated type designed to prevent accidental contact.

Connectors and wire should be checked for voltage and current ratings. Always use

wire with an insulation rating higher than the working voltages in the power supply. Special high-voltage wire is available for use in B+ supplies. The **Component Data and References** chapter contains a table showing the current-carrying capability of various wire sizes. Scrimping on wire and connectors to save money could result in flashover, meltdown or fire.

All fuses and switches should be placed in the hot leg(s) only. The neutral leg should not be interrupted. Use of a three-wire (grounded) power connection will greatly reduce the chance of accidental shock. The proper wiring color code for 120-V circuits is: black — hot; white — neutral; and green — ground. For 240-V circuits, the second hot lead generally uses a red wire.

POWER-SUPPLY PRIMARY CIRCUIT CONNECTOR STANDARD

The International Commission on Rules for the Approval of Electrical Equipment (CEE) standard for power-supply primary-circuit connectors for use with detachable cable assemblies is the CEE-22 (see **Fig 17.28**). The CEE-22 has been recognized by the ARRL and standards agencies of many countries. Rated for up to 250 V, 6 A at 65°C, the CEE-22 is the most commonly used three-wire (grounded), chassis-mount primary circuit connector for electronic equipment in North America and Europe. It is often used in Japan and Australia as well.

When building a power supply requir-

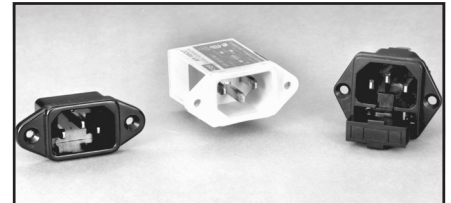


Fig 17.28 — CEE-22 connectors are available with built-in line filters and fuse holders.

ing 6 A or less for the primary supply, a builder would do well to consider using a CEE-22 connector and an appropriate cable assembly, rather than a permanently installed line cord. Use of a detachable line cord makes replacement easy in case of damage. CEE-22 compatible cable assemblies are available with a wide variety of power plugs including most types used overseas.

Some manufacturers even supply the CEE-22 connector with a built-in line filter. These connector/filter combinations are especially useful in supplies that are operated in RF fields. They are also useful in digital equipment to minimize conducted interference to the power lines.

CEE-22 connectors are available in many styles for chassis or PC-board mounting. Some have screw terminals; others have solder terminals. Some styles even contain built-in fuse holders.

A SERIES-REGULATED 4.5- TO 25-V, 2.5-A POWER SUPPLY

For home-laboratory requirements, a series-regulator supply is simpler and less expensive than a switching power supply. Series-regulated supplies are also free of electrical switching noise, which is a problem with some switching supplies. During tests of sensitive low-level circuitry, the power supply output should be pure dc; it should not contribute to problems in the circuit under test.

The power supply in **Fig 17.29** was designed and built by William E. Sabin, WØIYH. See “High-Precision Series Regulator Loop Design,” earlier in this chapter, for a discussion of the design, analysis and tests of the feedback control loop used in this power supply.

FEATURES

This supply was designed to meet the following objectives:

- Continuously variable output voltage from 4.5 to 25.0 V.
- Tight load voltage regulation, better than 0.03%, for load currents from 0 to 2.0 A, 0.1% to 2.5 A; 0.01% into a 2.0-A load for ac-line voltages from 117 to 122 V.
- Excellent response to load fluctuations and transients (low output impedance).
- Very low ac ripple, less than 2 μ V RMS with a 2.0-A load.
- Very low random noise, less than 2 μ V RMS from 0.1 Hz to 500 kHz.
- Use an off-the-shelf transformer and other easily obtainable parts.
- Load currents up to 2.5 A, continuous duty.
- Switch selectable current limiting, at 0.1, 0.5 or 2.5 A, to protect delicate circuits under test.

THE CIRCUIT

Fig 17.30 is a schematic of the power-supply circuit. An LM723 regulator was selected because it's simple, and its reference voltage is available (pin 6) for filtering. Reference noise (typical of zener diodes) is reduced to a very low level via C5, as suggested in the data sheet for the LM723. The current-limiting circuitry is also accessible (at pins 2 and 3). It senses the voltage drop across R2 and R3.

The combination of R2 and R3 sets the current limit at $0.62 / (R2 + R3)$ A. R3 (R3a and R3b together) forms an 0.11- Ω , 4-W resistor, which acts as a shunt for the digital meter that measures load current. R8 provides meter adjustment without affecting R3 significantly. S3 selects from three values of R2 to set current limits at approximately 0.1, 0.5 or 2.5 A.


C1 has a large value to reduce output ripple voltage. Smaller values would increase ripple and require a higher transformer voltage to prevent regulator drop out. Other voltage drops between the Q1/Q2 emitters and the output terminal are mini-mized to assure that a standard 25.2-V transformer can do the job. The R1-C2 combination reduces ac ripple at the LM723 by a factor of 25; this eliminates the need for an extremely large value of C1.

The circuitry of Q3, R10, C7 and D1 prevents the voltage on pins 11 and 12 of U2 from exceeding the 40-V maximum rating of the LM723 (especially with light loads and high line voltage). C7 eliminates a very small ac ripple at the dc output. As load current increases, the voltage at C1 decreases and Q3 is saturated.

When R4 is adjusted to reduce output voltage, U2 and Q1/Q2 are switched off until C6 discharges to the lower voltage. This causes the emitter-base junctions of Q1 and Q2 to break down (at about 2.0 V) so that C6 could discharge through R5. D2 provides an alternate path and prevents this breakdown. R5 provides a minimum load for U2.

The foldback circuit is interesting: Q4, D4 and R13 provide a constant current through, and therefore a constant voltage drop across, R16. This voltage makes the current limiting (pins 2 and 3 of U2) work properly over the entire 4.5- to 25.0-V range. As the current limiting action pulls the voltage at the top of R16 below about 4.0 V, D3 quickly stops conducting, the voltage across R16 approaches zero and the load current is limited at about 1.9 A. This limits Q1/Q2 and T1 dissipation and provides short-circuit protection. This is a regenerative positive feedback process. R14 sets the current at which foldback begins, 2.6 A. There is further discussion of foldback circuitry earlier in this chapter.

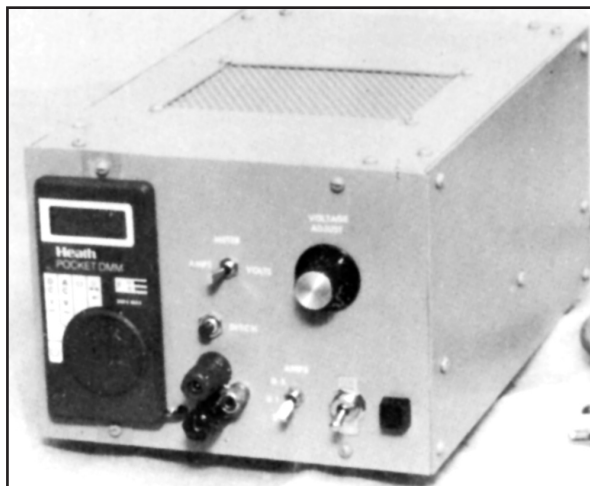An inexpensive Heath SM-2300-A auto ranging DMM (mounted on the front panel) displays the supply output levels. The dedicated DMM can display very small output changes. S2 selects either voltage or current (divided by ten) for display. (The DMM is left in its voltage range for both measurements.) The voltage across R3 is



0.11 times the load current. R8 provides the required ammeter adjustment without significantly affecting R3. The meter shows 0.2 for 2 A. Ordinary wire-wound resistors are adequate for R3 because they do not heat significantly at 2.5 A.

R9 sets the reference voltage on pin 5 of U2 at 4.5 V to establish the minimum output voltage. R11 sets the 25.0-V upper limit. A three-wire line cord assures that the supply chassis is always tied to the ac-line ground, for safety reasons. The dc output is not referenced to chassis ground, and performance is independent of the ac-ground connection. If the load current is very small, it may take a long time for C6 to discharge when the power is switched off; a press of S4 quickly discharges the capacitors (through R15) after turnoff. The mechanical construction emphasizes heat removal, so a cooling fan is not needed.

CONSTRUCTION

Several areas are critical to good performance. Pay particular attention to these:

- Wire C1 with short, heavy leads to present a minimum impedance to ac ripple. Also, connect C1 directly to the negative binding post with a heavy lead. This provides a low inductance path for load-current fluctuations and keeps them off the PC-board ground plane.
- Connect C2 directly to the negative lead of C1.
- Connect C6 directly across the binding posts.
- Connect R4 to R11 with a low-impedance lead and connect R11 directly to the PC board ground plane.

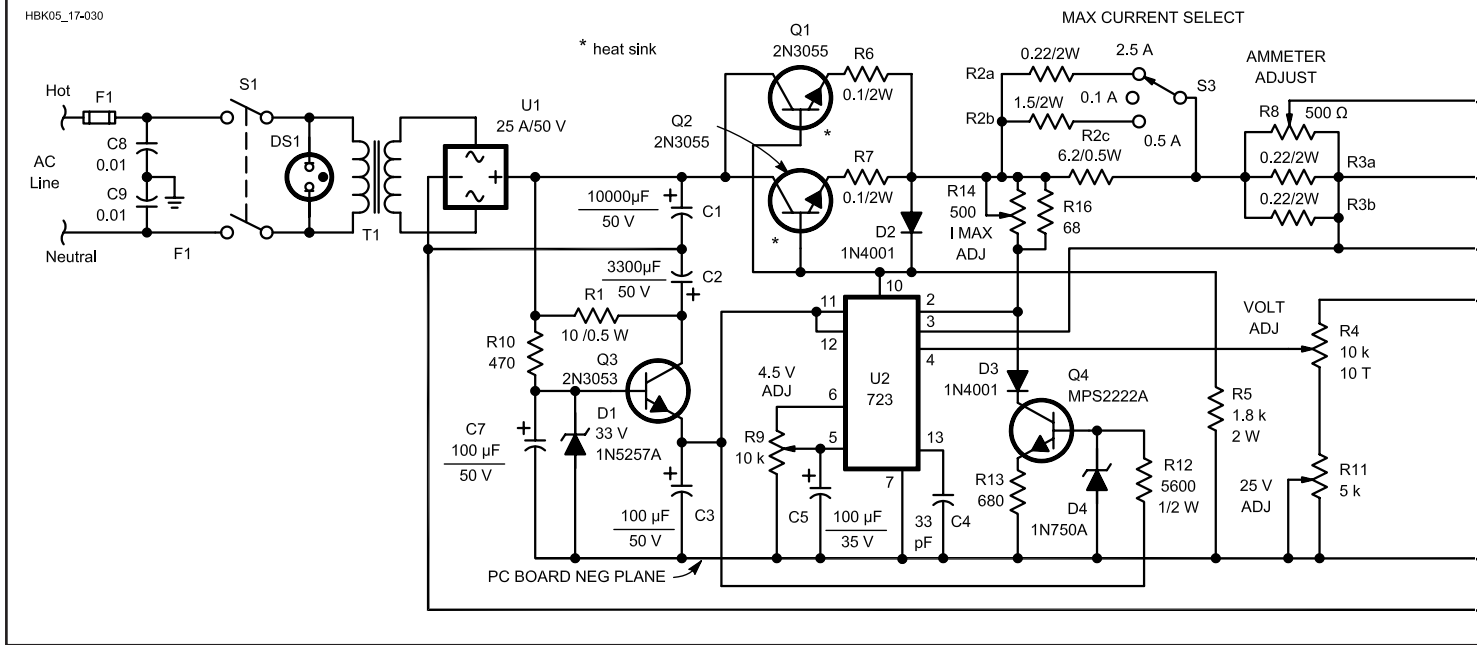


Fig 17.30 — Schematic of the 4.5 to 25-V, 2.5-A regulated dc power supply. Heavy lines indicate critical low-impedance conductors; use short conductors with large surface areas. “RS” signifies a RadioShack part number; “CDE” is a Cornell Dubilier Electric part.

- | | | |
|--|---|---|
| C1 — 10000 μ F, 50 V (CDE 10000-50-AC, or equiv) | P1 — Three-wire power cord and plug | R12 — 5.6 k Ω , 0.5 W |
| C2 — 3300 μ F, 50 V (CDE 3300-50-M, or equiv) | Q1, Q2 — 2N3055 (RS 276-2041, or equiv) | R13 — 680 Ω , 0.25 W |
| C3, C7 — 100 μ F, 50 V (RS 272-1044, or equiv) | Q3 — 2N3053 (RS 276-2030, or equiv). | R16 — 68 Ω 0.25 W |
| C4 — 33 pF, 50 V | Q4 — MPS2222A (RS 276-2009, or equiv) | S1, S2 — DPDT (RS 275-652, or equiv). |
| C5 — 100 μ F, 35 V (RS 272-1028, or equiv) | R1 — 10 Ω , 0.5 W | S3 — SPDT (center off) (RS 275-654, or equiv) |
| C6 — 1000 μ F, 35 V (RS 272-1032, or equiv) | R2a — 0.22 Ω , 2 W | S4 — Normally open, momentary-contact, push-button switch (RS 275-1547, or equiv) |
| C8, C9 — 0.01 μ F, ac-rated capacitor. | R2b — 1.5 Ω , 2 W | T1 — 120-V primary, 25.2-V, 2.8-A secondary (Stancor P-8388, or equiv) |
| D1 — 1N5257A 33-V Zener diode. | R2c — 6.2 Ω , 5%, 0.5 W | U1 — Rectifier bridge, 25 A, 50 V (RS 276-1185, or equiv) |
| D2, D3 — 1N4001 (RS 276-1101, or equiv) | R3 — 0.15 Ω , 2 W | U2 — LM723 regulator (RS 27-1740, or equiv) |
| D4 — 1N750A | R4 — 10 k Ω , 10-turn potentiometer (Bourns 3540S, or equiv) | Heat sink — Wakefield 403A, or equiv (two required). |
| DS1 — Neon lamp, 120-V ac (RS 272-704, or equiv) | R5 — 1.8 k Ω , 2 W | |
| F1 — 1.5 A slow-blow (RS 270-1284, or equiv) | R6, R7 — 0.1 Ω , 2 W | |
| M1 — DMM (Heath SM-2300-A, or equiv) | R8, R14 — 500 Ω potentiometer (RS 271-226, or equiv) | |
| | R9 — 10 k Ω potentiometer. | |
| | R10 — 470 Ω , 0.25 W | |
| | R11 — 5 k Ω potentiometer | |

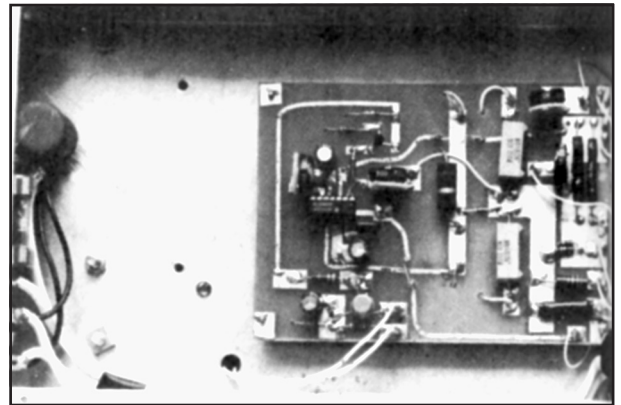
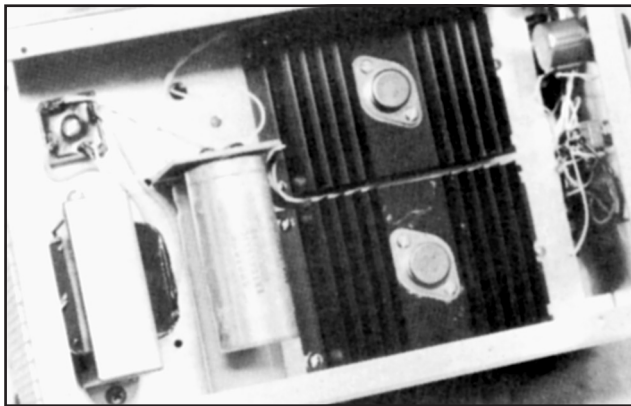


Fig 17.31 — A shows a top view of the open power-supply chassis. The $\frac{1}{8}$ -inch plate holding C1 is visible at the left edge of the heat sinks. B shows a bottom view. Notice that the components are mounted on the etched side of the board. The circuit pattern is simple enough for freehand layout. The front panel is at right in both views.

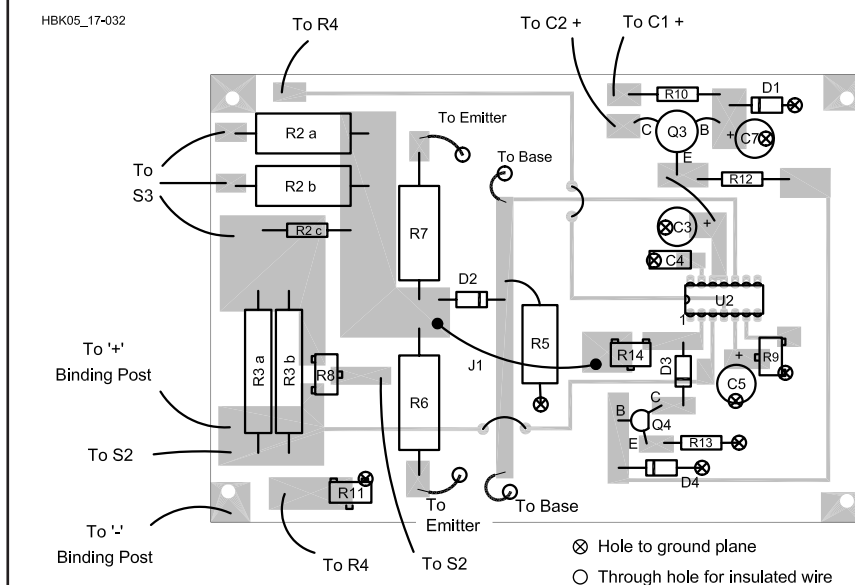
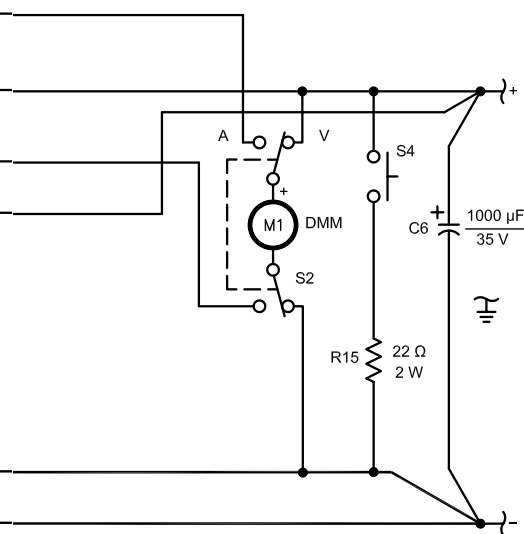


Fig 17.32 — A parts-placement diagram for the 2.5-A power supply. The component side is shown, and the etching is on the component side. Cross hairs indicate holes through the board. Component leads that terminate at cross hairs are grounded on the far side of the board. The emitter and base leads of Q1 and Q2 do not connect to the ground plane. Use insulated wire to pass through the PC board and holes in the chassis to the transistors on the heat sinks. Wire Jumper J1 is soldered to the pad surfaces without drilling holes. If you do drill holes for the jumper be sure to remove the ground plane around the holes on the non-component side. A full-size etching pattern is in the **Templates** section of the *Handbook* CD-ROM.

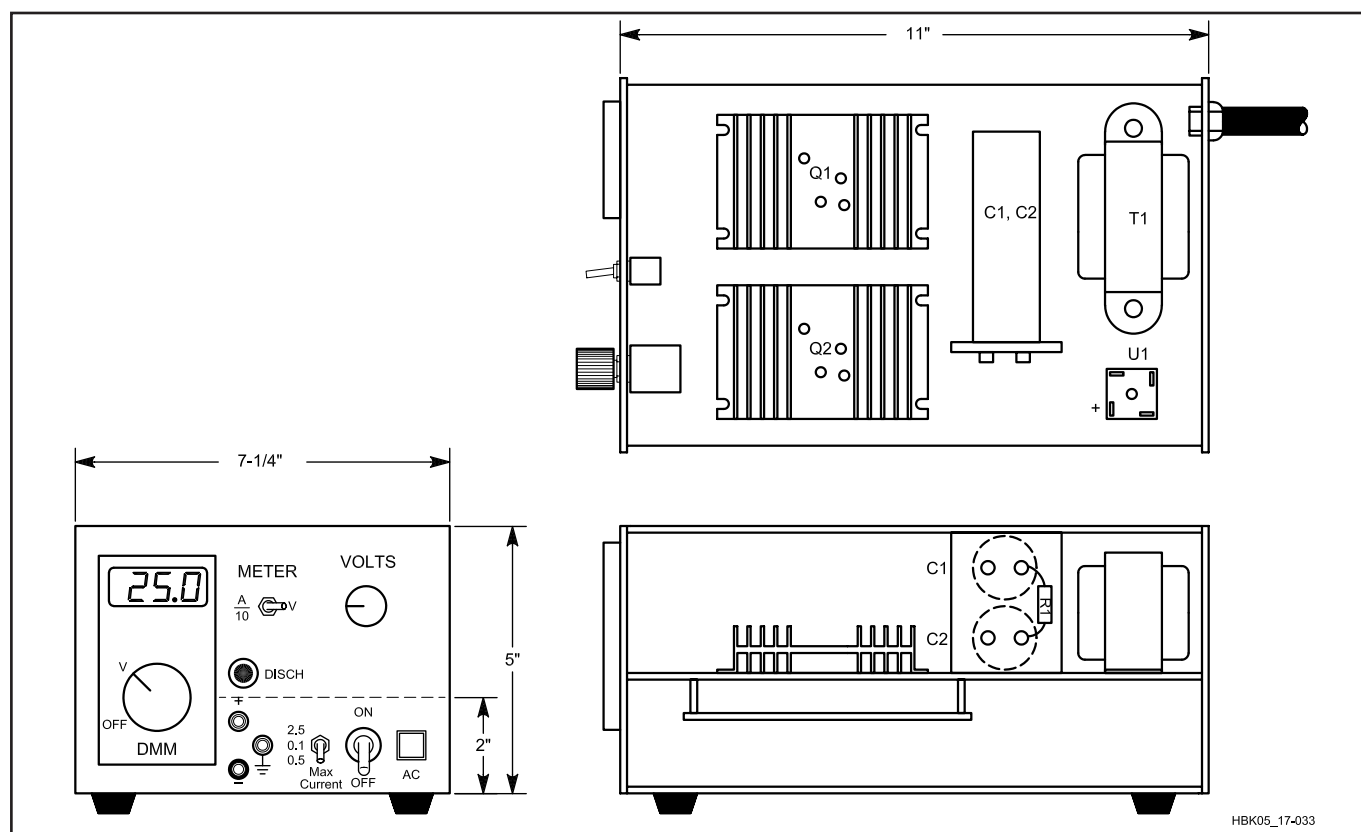


Fig 17.33 — This three-view drawing shows the panel layout and locations of major power-supply components.

- Connect the regulator PC board ground plane to the negative binding post at a single point.
- Use heavy-duty binding posts to reduce a small but significant voltage drop (from the rear to the front) at the front panel.

Fig 17.31 shows the general construction and **Fig 17.32** shows the front-panel layout. The cabinet and chassis surface are $\frac{1}{16}$ -inch aluminum plates connected by aluminum angle stock, drilled and tapped for #6-32 screws. Ventilation screens at the top and rear provide an excellent chimney effect. The chassis plate is tightly joined to the side plates for good heat transfer. Construction of the cabinet shown is somewhat labor intensive; it involves a lot of metal work. Any enclosure of similar size with good ventilation is suitable. For example, a $7 \times 11 \times 2$ -inch chassis with a bottom cover and rubber feet, a $7\frac{1}{2} \times 6$ -inch front panel and a U-shaped perforated metal cover would serve well.

Q1 and Q2 each have a Wakefield 403A heat sink. The sinks were selected according to the thermal design discussion in the **Real-World Component Characteristics** chapter. The worst-case 2N3055 junction temperature was calculated to be 145°C , based on a measured case temperature of 95°C and dissipation of 32 W (each) for Q1 and Q2. This temperature is a little higher than recommended, but it's acceptable for intermittent lab use.

The DMM is epoxied to a narrow aluminum strip, which is then screwed to the front panel. This allows easy removal to replace the DMM battery.

Fig 17.31B shows the supply underside. The PC board is mounted on standoff insulators and positioned so that the posi-

tive and negative outputs are close to the binding posts.

Fig 17.33 is a parts-placement diagram for the regulator board. A full-size etching pattern is included in the **Templates** section of the CD-ROM included with this *Handbook*. All components and wiring are on the etched side of the board (with the help of a few jumper wires). The other side is entirely ground plane. The components are surface mounted by bending a section of each lead and soldering it to the surface of the appropriate copper pad. The socket for U2 is mounted by bending the pins out 90° and soldering pins 11 and 12 to the pad for C3. Some leads pass through holes (marked with cross hairs in **Fig 17.33**) in the PC board and solder to the ground plane. The emitter and base leads of Q1 and Q2 are isolated from ground; use insulated-wire to pass from the PC-board pads through holes in the PC board and chassis to the transistors.

Fig 17.32 shows the placement of major parts in front, top and side views. Silastic and pieces of Kraft paper cover any exposed 120-V wiring.

C1, C2 and R1 are mounted on a $\frac{1}{8}$ -in thick plastic board as shown in **Fig 17.32**. In the supply shown, it's a piece of $\frac{1}{8}$ -in PC board with wide traces. A piece of angle stock mounts the board to the chassis.

The main voltage control, R4, is a 10-turn potentiometer, for ease of adjustment. C8 and C9 are ceramic capacitors rated for ac-line use. Once the supply is complete, double check all wiring and connections.

ADJUSTMENTS

Several adjustments are needed: the dedicated AMMETER ADJUST (R8), the foldback

limit (R 14, 1 MAX ADJ), the lower (R9, 4.5 VOLT ADJ) and upper (R11, 25 V ADJ) voltage limits. First, obtain an accurate external ammeter and a test load that can draw at least 3 A at 12 V or so (automobile sealed beam headlights work well). Series connect the load and external meter to the supply binding posts. Set S3 to the 2.5-A range; set R4 for minimum output; set S2 to A and switch on the power. Advance R4 until the ammeter reads 2.0 A, and adjust R8 until the panel meter also reads 0.200. Next, increase R4 until the current slightly exceeds 2.6 A, and adjust R14 so that current begins to decrease (foldback). Switch off the supply and remove the external meter and load.

Adjust the voltage limits with no load connected and S2 set to v. Switch on the supply, set R4 for minimum voltage and adjust R9 until the meter reads 4.5. Increase R4 to maximum voltage and adjust R11 so that the meter reads 25. The supply is ready for use.

PERFORMANCE AND USE

The example supply met the design goals: When the line voltage was varied from 117 to 122 V (with a 25-V dc 2.0-A load), the output voltage varied less than 0.01%. When the dc load was varied from 0 to 2.0 A, the output voltage changed less than 0.03%.

When extremely tight regulation and low output impedance are important, the leads to the load must be very short, heavy straps. Multiple loads should be parallel-connected directly at the binding posts. A "Daisy chain" connection scheme does not assure equal regulation for each load; it counteracts the precision regulation of this supply.

A 12 VOLT DC BOOST REGULATOR FOR MOBILE OPERATION

Varying battery voltage during mobile or portable operation or when using emergency power can be annoying and troublesome. Low battery charge, combined with voltage drops in wiring, can cause reduction in output power or transmit signal distortion in many radios. One solution to this problem is to build a switch-mode power supply (SMPS) to maintain the dc input voltage. An SMPS can offer boosted power levels and allow longer operating times from a given battery. This project, by Daniel R. Kemppainen, N8XJK, shows you how to build and test one. The completed boost regulator is shown in **Fig 17.34**.

OVERVIEW

This SMPS is a simple boost supply,

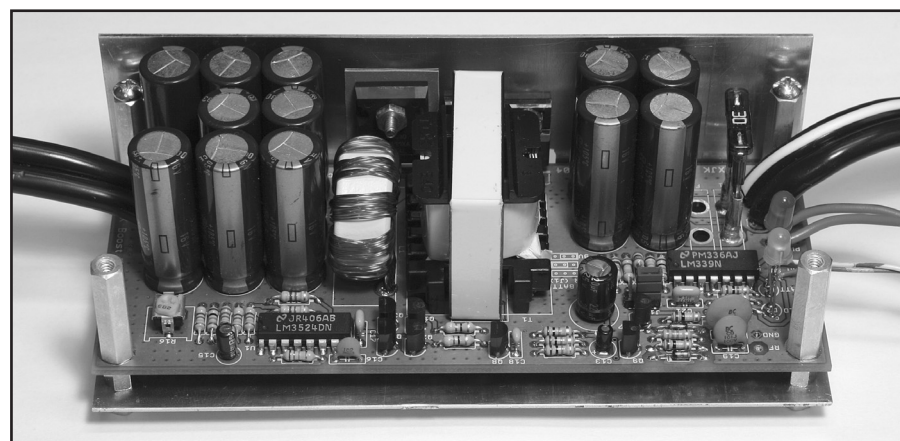


Fig 17.34 — The completed boost regulator supply. A sheet of bent aluminum acts as a mounting base and heat sink.

designed to make up the difference between battery voltage and a preferred output voltage level at the cost of some additional current draw from the battery. It was designed for an output current of about 25 A. When turned off, the battery voltage (less one diode voltage drop) is present at the output terminals of the supply. No power transfer relays or switches are required. The supply can be set up to operate on demand (during transmit) or continuously, depending on user requirements. A switch or relay contact is used to switch the power supply control power off when not in use. This reduces power consumption during periods of inactivity or when voltage is sufficient to power the radio.

Two “on demand” inputs are provided to enable the voltage boost function. One of the inputs is a simple remote enable input, and requires only a battery voltage signal. This can be used in conjunction with a control signal from a radio to key the supply or it can be enabled by a toggle

switch for manual operation.

The other input is an RF detector. The RF detector can be used to monitor the RF output of the attached radio and allow the voltage boost to take place when the radio is transmitting. This scheme works well because many radios operate correctly in receive mode when powered from a low-voltage source. The RF detector attaches directly to the antenna lead of most radios using a coaxial T fitting or a coupling transformer. This design has been tested with radios transmitting from several watts to 100 W. Operation at higher power levels may require some circuit modifications.

CIRCUIT DESCRIPTION

The SMPS uses a push-pull design topology as shown in **Fig 17.35**. The positive battery terminal is connected to the center tap of the primary of the switching transformer T1. The secondary of T1 is also a center tapped winding, with its center tap

also attached to the battery voltage. The voltages seen on the secondary legs of T1 are the battery voltage plus the voltage of the transformer windings. This configuration allows the transformer to supply only the difference between the output and battery voltages.

In addition, the power requirements of the transformer and switching transistors are reduced. This also allows battery voltage to be present at the output of the supply when it is switched off. MOSFET transistors Q5 and Q6 alternately switch the legs of the primary winding of T1 to ground, creating an ac flux waveform in the transformer. The secondary legs of transformer T1 are rectified by the dual Schottky diode D7. Inductor L1 and eight 3300 μF capacitors (C5-C12) form a low pass filter to smooth the rectified waveform.

A switch-mode power supply controller, U1, handles the voltage regulation. The controller used in this supply is an LM3524D. The LM3524D uses pulse width

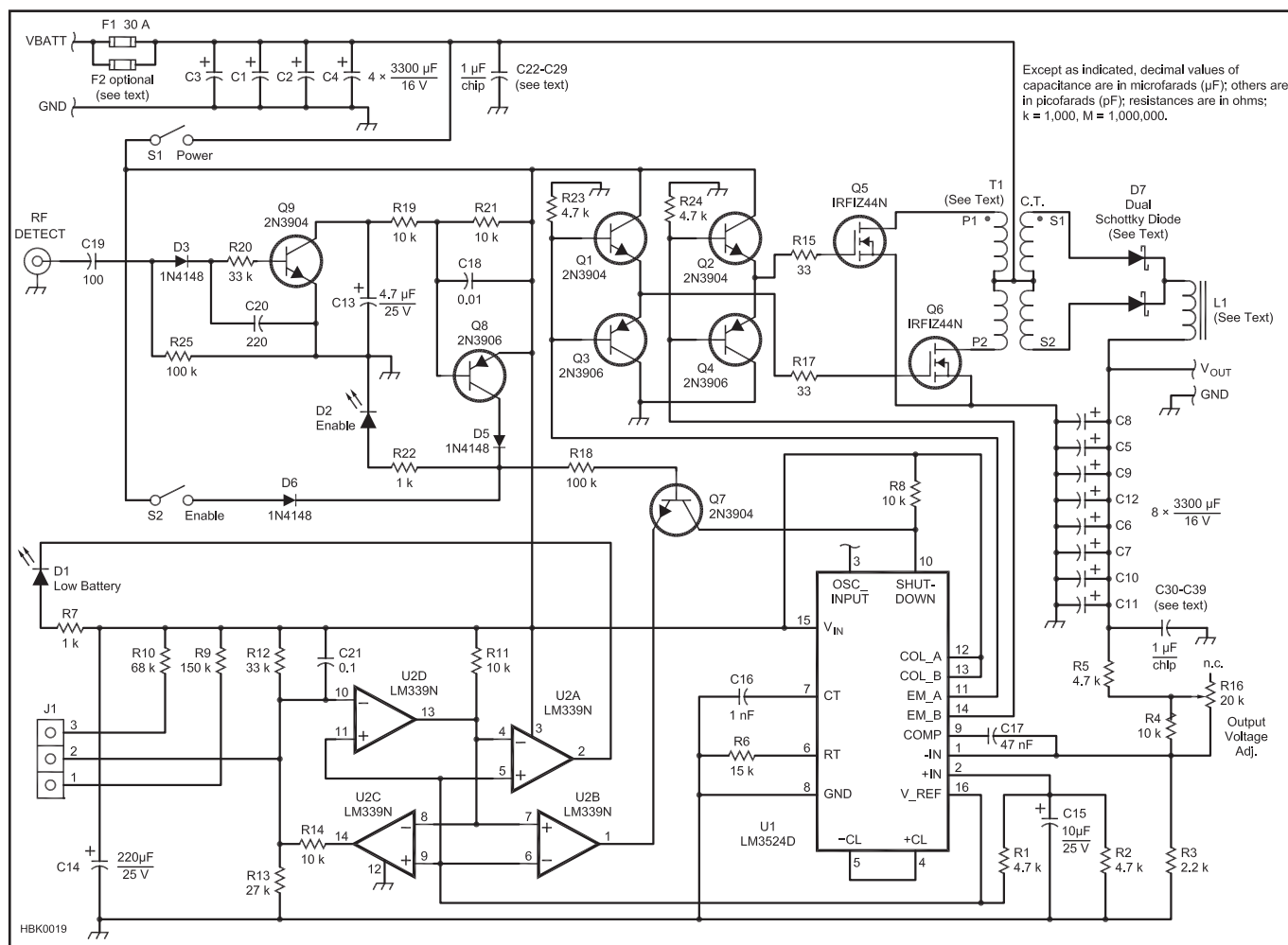


Fig 17.35 — Schematic diagram of the boost regulator. A complete parts list is included in the template package on the CD-ROM accompanying this book. PC boards and cores for T1 and L1 are available from FAR Circuits (www.farcircuits.net). Kits are available from TG Electronics (tgelectronics.org). Note that R25 is in the spot occupied by D4 in the original design; D4 is not used. C22-C29 and C30-C39 are 1206 size SMT chip capacitors that mount on the bottom of the double-sided PC board.

Detailed Transformer Calculations

The transformer used in the boost regulator is unusual because the input voltage is fed into the center tap of both the primary and secondary leads. This transformer is also unusual in that its input voltage is low compared to most switching transformers, so the primary is wound with a low number of turns.

The two main calculations needed to get a working transformer — the operating flux density and the turns ratio. We can assume that the transformer will be large enough to supply the power needed given the operating frequency and size of the core chosen.

The maximum flux density must be known to prevent the transformer from saturating. Saturation is a condition in which a transformer core cannot carry any more magnetic flux. At saturation the inductance of the primary winding falls, causing very high currents in the primary that can damage the transformer windings and switching transistors.

Faraday's law can be rearranged to give the transformer's operating flux density:

$$B_{\max} = \frac{E \times 10^8}{4 N_p f A_c}$$

where

$B_{\max}$ = the maximum flux density in Gauss

E = the primary voltage

N_p = the number of primary turns

f = the operating frequency in Hz

A_c = the core cross-sectional area in cm^2

The number 4 is a constant based on a square wave input.

Maximum flux density may also be limited to reduce losses in the transformer core. Typically flux density is limited to reduce losses at frequencies above a few kHz. An accepted industry rule of thumb is to limit flux density to around 2000 Gauss at 20 kHz. For our transformer we will use 2000 Gauss as a target flux level, but we will use a higher switching frequency (38 kHz). Because of the mode of operation of this supply, and because the saturation for most of the common ferrites starts to occur above 4000 to 5000 Gauss, we should not have any trouble. The switching frequency, input voltage, and maximum flux density are known, so we can simplify the equation to solve for the number of turns based on the area of the core:

$$A_c N_p = \frac{E \times 10^8}{4 B_{\max} f}$$

For this transformer, the operating frequency is 38 kHz.

The minimum and maximum input voltages are 9 V and 15 V respectively. The output voltage is also assumed to be 9-15 V. It will be important to remember that in this supply, the output voltage of the transformer is added to the supply voltage. This means that the transformer secondary windings need to generate only 6 V at worst case ($15 V_{\text{out}} - 9 V_{\text{in}} = 6 \text{ V}$).

Using the above equation, limiting $B_{\max}$ to 2000 Gauss, and knowing that $E_{\max} = 15 \text{ V}$, and $f = 38000 \text{ Hz}$, we can calculate

$$A_c N_p = \frac{15 \times 10^8}{4 \times 2000 \times 38000} \quad \text{or}$$

$$A_c N_p = 4.93.$$

We can rearrange the equation to solve for N_p given a known core area: $N_p = 4.93/A_c$.

For the transformer used in the supply pictured, the core area is 1.32 cm^2 . So the minimum number of turns needed on the primary is $4.93/1.32$, or 3.73. Remember that increasing

the number of turns reduces the flux density. This seems counterintuitive, but by careful inspection of the formula presented we see that N_p is in the denominator of the equation calculating $B_{\max}$. Therefore, increasing N_p reduces the maximum flux density. Because of this, we can round up the number of turns on each leg of the primary. For our design, we will use 5 turns for each leg of the primary.

Once the transformer primary turns are known, the secondary turns can be calculated. The primary-to-secondary ratio is not quite as simple as the ratio of input voltage to output voltage (in our case output voltage being equal to boost voltage). Although the voltage ratio typically does equal the turns ratio for a transformer, there are some things that must be taken into account and corrected for.

The first factor is the maximum duty cycle of the pulse width modulator used in the supply. The LM3524D runs with a maximum duty cycle of 45% per transistor, or 90% total maximum duty cycle. If the transformer had a primary-to-secondary ratio of 1:1, the output voltage would be limited to 90% of the input voltage. This maximum duty cycle must be taken into account and corrected for by adding 10% to the turns ratio.

Another item to consider is that the switching transistors are in series with the primary leads of the transformer, and will reduce the primary voltage by some amount. Given the worst case scenario, when the input voltage is 9 V and the output voltage is 15 V at the rated output current of 25 A, the primary current can be calculated. Since the transformer needs to supply $25 \text{ A} \times (15 \text{ V} - 9 \text{ V}) = 150 \text{ W}$ of power, the primary current can be calculated as $150 \text{ W}/9 \text{ V} = 16.67 \text{ A}$.

Remember that the average current is half of this value, so I^2R losses will be based on 8.3 A. The transistors, however, will see the full 16.7 A when conducting. The transistors used in this supply have a rated on-resistance of 0.024Ω , so we multiply this by the 16.7 A primary current to obtain the voltage drop across the transistors when conducting. That voltage drop works out to be around 0.4 V. That is roughly 4.5% of the minimum 9 V input voltage. To account for this drop, we will round up, adding 5% more to the turns ratio correction factor. With the duty cycle correction, we are up to a 15% increase in the turns ratio needed.

There are also voltage drops in circuit traces and in the fuse that must be accounted for. These voltage drops can be a little hard to predict, but for low-input-voltage transformers, adding 10% is a good rule of thumb. This additional 10% also adds a little bit of buffer. This brings our turns ratio correction up to 25%.

We must also remember that the output current flows through a diode. The diode forward voltage will likely be around 0.4 V, or 6.7% of the 6 V of boost required. Adding this to the 25% we already have results in a turns ratio correction of just under 32%.

Using the input-to-output voltage ratio and our correction factors, we can now calculate the turns ratio of the transformer. Since we need 6 V of boost from a 9 V input, the theoretical turns ratio would be $N_p:N_s = 9:6$. Adding the 32% correction factor to the secondary, the turns ratio becomes $N_p:N_s = 9:(6 \times 1.32)$, or 9:7.92. This can be simplified to 1:0.88, so the secondary winding will need to have 0.88 turn for every turn of the primary of the transformer. With 5 turns per leg of the primary, the secondary will need 5×0.88 or 4.4 turns per leg. The transformer layout used in the supply places the center tap of the secondary on the opposite side of the transformer from the ends of the secondary. This works out well, since the transformer needs about 4.5 turns per leg for the secondary.

modulation to control the time that switching transistors Q5 and Q6 are turned on. By varying the pulse width, the ac voltage of the transformer is varied and the output voltage is maintained. A simple battery voltage monitor circuit is used to monitor low battery conditions. The low voltage protection circuit shuts down the LM3524D in the event that battery voltage falls below a minimum level. The protection voltage is jumper selectable to 9, 10 or 11 V. The circuit uses an LM339 quad comparator in conjunction with a +5 V dc reference voltage provided by the LM3524D controller IC. When the protection circuit is tripped, the supply boost function is disabled and battery voltage is present at the output of the supply. A reset of the battery protection circuit is accomplished by cycling the POWER switch (S1).

Transformer Winding Calculations

Since the operating frequency, operating voltage, and transformer operating flux density are known, the calculations for the number of turns can be simplified. For more detail, see the sidebar “Detailed Transformer Calculations.”

The inductor and transformer are custom parts and will need to be wound for this supply. The original article used an E40 size metric switching transformer core salvaged from a old PC power supply (see the sidebar “Salvaging Parts for T1, L1 and D7”). A new transformer core and bobbin and inductor core are included with the FAR Circuits PC board available for this project.

The supply is designed to boost 150 W of power. This means that the transformer must supply 150 W of boosted voltage to the output of the supply. If we assume 9 V minimum input voltage and 15 V maximum output voltage, the current supplied is $150 \text{ W} / (15 \text{ V} - 9 \text{ V})$ or 25 A.

To calculate the turns ratio and number of turns needed on the primary, the area of the transformer core (A_c) will need to be measured. To obtain this value, simply multiply the dimensions of the center leg of the “E” section of the transformer core. The core area needs to be in cm^2 , so convert units as required. Typically the center leg of the core will measure around $1.15 \times 1.15 \text{ cm}$, with a core area around 1.15 to 1.35 cm^2 .

To calculate the *minimum* number of turns needed on the primary, divide 4.93 by the core area (A_c) in cm^2 . For the transformer shown, it is $4.93 / 1.32 = 3.73$ turns. The number will vary slightly but will usually be around 4 turns per leg. Increasing the number of turns a little on the primary will not hurt anything and may reduce transformer core losses a little. For the

transformer shown, 5 turns per leg of the primary works well.

The number of turns needed on the secondary can be calculated as 0.88 times the number of turns on the primary. Assuming 5 turns per leg on the primary, the number of turns on the secondary will be $5 \times 0.88 = 4.4$ turns. You can round the number of turns on the secondary up, as needed. Keep in mind that the number of turns on the primary is critical, since it sets the operating flux density in the transformer core (see the sidebar for details). Also remember to calculate the turns on the secondary based on the actual number of turns wound on the primary, and not the minimum number of turns needed. The switching controller will allow for small variations in the turns ratio and will compensate by adjusting the pulse width of the switching transistors to maintain the output voltage as long as the turns ratio is high enough to provide the voltage gain necessary.

The wire sizes for the primary and secondary can be easily calculated. Since the transformer is designed to supply 150 W of boost power from a minimum input of 9 V, the current in the primary winding can be calculated as $150 \text{ W} / 9 \text{ V}$, or 16.7 A. Because of the push-pull configuration, each leg of the primary will see the 16.7 A for no more than 50% of the time. Each leg of the primary winding can be sized at 50% of the 16.7 A, or 8.3 A.

The secondary current is the same as the rated supply output current because all of the current that passes through the supply is seen in the secondary winding. Assuming a maximum current of 25 A with a 50% duty cycle, the secondary current per leg can be calculated as 12.5 A. When the supply is off, the secondary legs of the transformer act in parallel so this 50% current rating holds true.

Winding the Transformer

Winding the transformer is the most difficult task in building this boost regulator. Given a little patience and preparation, the job should take about an hour. Paralleled #24 or #26 copper wire has proven the easiest to work with for the current-carrying conductors. Use three #24 (or five #26) wires paralleled for the primary and five #24 wires (or eight #26) for the secondary. Magnet wire with solderable polyurethane insulation makes assembly of the transformer much easier. Simply twist the wires together and tin the leads starting from the end of the lead. The insulation melts off wherever solder touches it.

Because of the relatively low voltages involved, this design relies solely on the insulation on the wire to serve as insulation between windings of the transformer.

A clear plastic tape (Scotch or similar) can be used to hold down the windings. Kapton, Ruban or similar dielectric tape could be used. The same tape will also be needed to hold the transformer core together after the bobbin and core have been assembled. After the supply has been tested, it is a good idea to use some silicone or similar glue to hold the core and bobbin together and secure them to the main circuit board.

The double sided circuit board requires a slightly different pin layout than the single sided circuit board. The center tap of the primary and secondary are in a different location than for the single sided version of the board. Other than the pin location change, the winding instructions are identical for both versions. Also, the double sided circuit board has an additional ground pad for a transformer shield (optional). If you use a shield, make sure that it does not act as a shorted turn on the transformer. This can be accomplished by wrapping the shield around the entire transformer core after the transformer is wound and core is assembled. By including the outside legs of the core, the net flux seen by the shield winding is zero. If you want to wind a shield winding between the primary and secondary, be sure that the shield is insulated from itself, and that you bring only one drain lead off of the shield to ground.

Fig 17.36 shows the transformer pin layouts. The “pins” used in this transformer are actually the windings, and the pins pressed into the transformer bobbin must be removed before assembly. Looking from the top side of the transformer (pins pointing down), pin 2 is the center tap for both the primary and secondary windings. Pins 1 and 3 are the legs of the primary, and pins 4 and 5 are the legs of the secondary.

All of the windings are wound in a counter-clockwise direction looking down onto the top of the transformer. Keep all windings as tight as possible. Gaps between the windings can result in increased flux leaking around the wires. Any leaked flux acts as inductance within the transformer. This leakage inductance, coupled with the fast switching transitions of the switching transistors, can generate transient voltages high enough to damage the switching transistors. If the transients prove to be excessive, the transformer must be rewound. Typically this is not a problem, but is important to keep in mind.

To wind the transformer, start with the primary. Each strand of wire is about 40 in. long. Use three of the #24 (or five #26) copper wires cut to length, and start at pin 1, as shown in Fig 17.36. Wind 5 turns

in the counterclockwise direction looking at the top of the transformer (pins away from you), and bring the winding out at pin 2. Secure the winding with some tape. Fold the wire back into pin 2, leaving a 1 inch long loop. Continue winding 5 more turns in the same direction as before, stopping at pin 3. Again secure the winding with tape. Although this sounds simple you may need to borrow additional fingers to help wind the tape. Once you have secured the end of the winding, the primary is complete (Fig 17.37).

For the secondary, use five #24 (or eight #26) copper wires, again about 40 inch long. Start at pin 5 with the secondary winding and wind 4.5 turns counterclockwise, stopping again at pin 2. Secure the winding with tape. As before, make a loop back into pin 2 and continue to wind 4.5 more turns, stopping at pin 4. This time add some additional tape to help secure all of the windings. Trim the windings at each of the pins to about 1 inch. Assemble the core, securing it with tape. Try to pre-stress the tape when attaching the top section of the core to make it tight.

The last step is to strip and tin the transformer leads. If you used solderable insulated wire, simply start tinning the leads. If you used standard enameled wire, scrape away the enamel with a knife. Do not use solvents because they can wick into the transformer and dissolve the enamel inside the windings. After stripping the transformer leads, twist them together and tin with solder. The transformer is now complete (Fig 17.38).

Winding the Filter Inductor

The only inductor is L1, used in conjunction with C5-C12 to make the output low-pass filter. The approximate value of L1 is 9 μ H and it must be capable of handling up to 25 A. Nine turns of wire on the toroid core will produce 9 μ H. Ten paralleled #24 copper wires work well for the winding. Each strand of wire is around 18 in. long, so plan on about 15 ft of wire for the winding. Strip, twist and tin the leads before inserting the inductor into the circuit board.

ASSEMBLING THE SUPPLY

Mount all of the components on the circuit board except Q5, Q6 and D7. There are a few items to note. The pads for Q5, Q6 and D7 are about 0.2 in. from the edge of the board. The leads must be bent for the devices to mount onto a vertical heat sink surface. Shape the leads before soldering the devices in place so that the devices are not stressed when bolting them to the heat sink. Initial testing must be done with these devices removed, so set them aside temporarily.

The automotive-style fuse, F1, is mounted with a pair of crimp style female spade connectors soldered to the board. Although the crimp connectors were not designed for this purpose, they work very well here. Have a fuse handy when selecting the connectors and pick a size that holds the pins

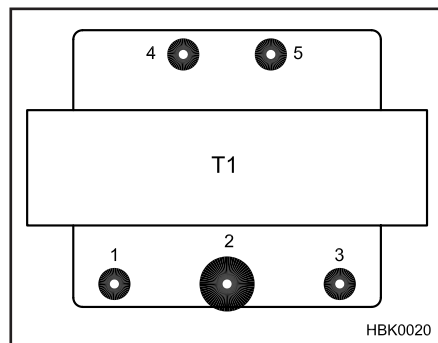


Fig 17.36 — Transformer pin layout looking down onto transformer (pins pointing away from viewer).

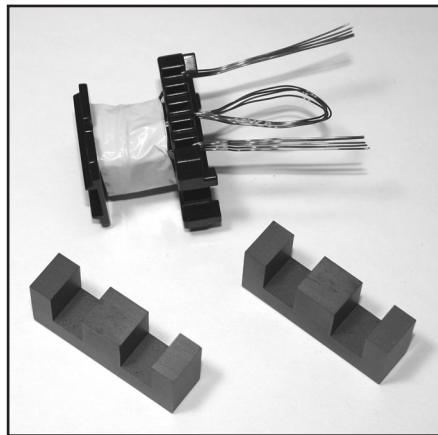


Fig 17.37 — Switching transformer with primary winding completed. This version uses five #26 wires for the primary, but three #24 wires would work as well.

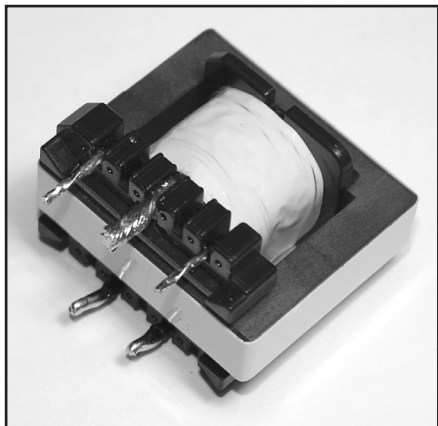


Fig 17.38 — Fully assembled transformer.

securely. Some spade connectors have a plastic sleeve that needs to be removed or an extra retaining ring that may get in the way. When mounting the fuse, it is usually easiest to stick the fuse clips onto a fuse and solder them into the board.

On the double sided version of the board, holes for an additional optional fuse (F2) were added for anyone interested in trying to build a supply for a higher output current. The transformer core, inductor windings and core, and heat dissipation in Q5, Q6 and D7 need to be evaluated before operating the supply at higher output power.

Use high-current wire for the input and output circuits. A good choice is high-end automotive speaker cable, usually available in sizes as large as 10 or 12 gauge. This wire is typically more flexible than most stranded wire, and it can be purchased by the foot from any car audio supplier. Use at least #12 for the battery leads and size the output leads according to the load.

TESTING THE SUPPLY

After mounting the components, run a quick check of the low voltage protection circuit, switching regulator, RF detection and enable circuits. To test these circuits, a frequency counter and voltmeter or oscilloscope are needed. A 12 V battery or low-current variable voltage bench supply will also be needed. If the bench supply has current limiting capability, set it to 1 or 2 A. For a battery, fuse the supply leads at about 2 A.

Battery Low Voltage Protection Circuit

The battery low voltage protection circuit was designed to protect the battery from being discharged too far. The circuit works by comparing a sample of the battery voltage to a reference voltage. The LM339 (U2) compares battery voltage to the reference from the LM3524D (U1).

The controller circuit shuts down when a low voltage condition is detected. R12 and R13 form the voltage divider used to sample battery voltage. R9 and R10 and the jumper J1 act in parallel with R12 to vary the voltage divider ratio. U2D compares the sample battery voltage to a reference voltage. When the voltage falls below the reference, U2D pulls its output pin to ground. U2C then seals the circuit by pulling the voltage going to U2D down even further. U2A acts as a simple switch, turning on the low voltage LED. U2B allows Q7's emitter to go high, allowing R8 to pull up the shutdown pin on the LM3524D, thereby disabling the supply.

An additional modification may be made to prevent the low voltage protec-

tion from permanently shutting down the supply. Simply remove R14 from the circuit. This prevents U2C from sealing the circuit, allowing the supply to boost voltage when the input again goes above the low voltage level. Several supplies have been tested with the modification, and they seemed to work well. The only thing you may notice is the supply starts to generate audible noise when the battery voltage is close to the low voltage limit. This happens because the low voltage circuit is fast enough to limit the boost regulator on each switching cycle of the PWM controller. This cycle-by-cycle limiting generates an audible hissing or chirping sound as you approach the low voltage cutoff.

To test the low voltage protection circuit, apply power and ground to the supply and close the POWER switch. With the POWER switch closed, remove the 12 V input from the supply. After a few seconds, the LOW BATTERY voltage LED should light up and stay on. Before depleting the voltage stored in the input capacitors (C1-C4), reconnect power to the supply. The LOW BATTERY voltage LED should still be on. Turn the POWER switch off for a few seconds, and then back on again. This should reset the battery protection circuit and the LOW BATTERY LED should be off.

Next, test the threshold voltage for the low battery protection circuit. Start by connecting a voltmeter or oscilloscope across the battery input to the supply. Set the battery protection voltage to 11 V by removing the voltage select jumper J1. Connect power to the supply, and cycle the POWER switch OFF and then ON. Remove the input voltage to the supply, and watch for the LOW BATTERY LED to come on. Note the voltage at which the LED turns on; it should be very close to 11 V. Reconnect power, and cycle the POWER switch. Repeat this test for the 10 V and 9 V threshold settings.

Supply Boost Enable Circuit

The supply enable circuit is designed to allow the supply to boost voltage when required. Two inputs allow the circuit to function. The first is a simple 12 V input and the second is an RF detection input. The ENABLE function can be forced manually by closing S2, feeding 12 V to D6 and supplying current to the base of Q7 through R18 and to the ENABLE LED through R22. Feeding current into the base of Q7 allows comparator U2B to pull the shutdown pin low, thus enabling the LM3524D.

The RF INPUT enables the supply when RF is present. The RF INPUT feeds current into the base of Q9 through D3, causing C13 to be discharged and current to flow through the base of Q8. Q8 then feeds

current into D5, enabling the supply just as the ENABLE input would. The charge time of C13 sets up a small delay that keeps the supply enabled after the RF signal is removed.

To test the ENABLE circuit, apply power to the supply and close the POWER switch. Apply 12 V to the ENABLE input (or close S2 if you have installed a switch there). The ENABLE LED should come on. Remove the 12 V feeding the ENABLE input, and the ENABLE LED should go off.

To test the RF INPUT, apply an RF signal (2 V p-p minimum) to the RF INPUT connector. The supply ENABLE LED should light up in the presence of RF and go off about a quarter of a second after removing the RF signal. The turn-off time may vary slightly, depending on the RF source.

Switching Regulator IC

The switching regulator is the heart of the circuit. The regulator uses pulse width modulation (PWM) to vary how long the switching transistors Q5 and Q6 stay on

for each switching cycle. By adjusting the pulse width of the switching transistors, the output voltage can be kept at a constant level. The switching regulator monitors the output through a voltage divider as a 2.5 V dc signal. Resistors R3, R4, R5 and R16 form the voltage divider that provides the feedback voltage. R16 is variable, allowing for adjustment of the output voltage. The reference signal comes from the LM3524D's internal 5 V reference and is divided down by the voltage divider formed by R1 and R2.

The next test will verify that the switching frequency is correct, the feedback network is working, and the gate driver transistors are operating correctly. *Note: D7, Q5 and Q6 must not be installed during this test.* Tie the supply positive input to the supply positive output. Turn the output voltage adjust resistor, R16, fully clockwise. This will help to ensure that the output voltage setting is above the input voltage. Attach a voltage source to the supply and close the POWER switch. Check that the input voltage

CHANGES FROM THE ORIGINAL DESIGN

This project was originally published in Nov 2004 *QST*. Since then, some changes have been made to the boost regulator, most notably the design of a new double-sided circuit board. The new board design has proven to reduce RFI, help make the circuit function optimally and make assembly easier.

The new PC board includes plated through holes, solder mask and silk-screened part placement guide. A large number of ground tie vias (plated through holes) were added to help reduce the impedance of the ground plane. These would be almost impossible to produce at home. For these reasons, I would suggest purchasing a professionally made board for the supply from FAR Circuits or the kit from TG Electronics.

If your heart is set on a completely homemade supply, you can build the single-sided version shown in Nov 2004 *QST*. It's a good, fully functional design in use all over the world. A template package with detailed information on building the original version of this supply is included on the CD-ROM accompanying this *Handbook*.

Circuit Changes

With the new PC board design, two of the transformer pin locations were moved to help balance the peak positive and negative flux excursions seen by the transformer core. The original transformer used four parallel #24 copper wires for the transformer secondary. While this number works fine, the use of five or six parallel #24 copper wires helps reduce losses a little.

The revised circuit is functionally identical to the original version. On the new board layout, some 1206-size surface mount capacitors were added on the bottom side of the board. These capacitors are in parallel with the electrolytic input and output filter capacitors. The capacitors were added as high frequency bypass capacitors to help reduce RFI. Surface mount capacitors were used because they exhibit lower inductance than leaded capacitors, so they function better as high frequency filters.

A couple of components were changed in the RF detect circuit. R20 was changed to 33 k Ω , and diode D4 was changed to a 100 k Ω resistor to help reduce power dissipation. The switching transistors (Q5, Q6) were changed to a more commonly available part, and the gate resistors (R15, R17) were also changed. Also, R23 and R24 were added to the driver transistors.

As an additional note, use the largest possible wire size for the battery leads and keep them as short as possible. This will help prevent the low-voltage lock-out feature from activating early. —Dan Kemppainen, N8XJK

to the supply is around 12-13 V dc.

Using an oscilloscope or frequency counter, check the frequency at the nodes between R15 and Q5 and R17 and Q6. This should be around 38 kHz, with a 50% duty cycle for each transistor. If the frequency is not within a few kilohertz of 38 kHz, the timing capacitor or resistor (C16 or R6) need to be adjusted. The waveform should have fast rising and falling edges. **Fig 17.39A** shows a sample of the gate driver waveform with Q5 and Q6 removed.

With the oscilloscope or frequency counter still attached to the nodes between R15 and Q5 or R17 and Q6, turn the R16 fully counterclockwise. This will set the minimum output voltage to around 9 V, which should be below the input voltage. The switching drive signals should be a steady 0 V signal, indicating that the output voltage is above the current voltage setting. When the test is complete, center R16. This should set the supply to around 13.3 V dc.

Putting It All Together

After the operation of the switching regulator IC, RF detect and enable inputs and the battery low voltage protection circuit have all been verified, mount Q5, Q6 and D7. It is important that a heat sink is attached to these components. The transistors come in an electrically isolated package and need only heat sink compound between them and the heat sink. The diode requires electrical isolation between its package and the heat sink using a mica insulator or sil-pad.

The first test with the switching transistors and rectifier diodes should be done with a 5 A fuse or a pair of 100 W, 12 V

light bulbs in series with the battery to limit current. If light bulbs are used, set the battery protection circuit to 9 V. Connect a voltmeter and a small 12 V automotive tail lamp or similar small load to the supply output. Hook the supply to the 12 V battery. With the POWER switch off, the 12 V load should be energized, and the meter should read the battery voltage minus one diode voltage drop (0.5-0.6 V).

Close the POWER switch. No LEDs should be on. If the battery protection LED is on, check the input voltage to the supply and cycle the POWER switch. Enable the supply with the RF DETECT input or ENABLE input and watch the output voltage. The voltage should jump slightly when the ENABLE LED comes on. If no change in voltage is detected, turn R16 clockwise until an increase is detected. As long as the battery protection LED is off, the ENABLE LED is on, and the output voltage setting is higher than the input voltage, the supply should be running. Set the output voltage to a desired level by adjusting R16. The supply is now running, and will regulate the minimum output voltage.


A final check of the supply should now be made. The transient voltages on the switching transistors need to be checked several times, with an increase in the load on the supply each time. This is important and should not be skipped. The minimum peak voltage normally seen is double the supply voltage. This is because the switching transformer acts as an autotransformer when each transistor is on and is not of any concern. The transient voltage of concern is generated when the switching transistors turn off. This happens when the voltage across the transistor starts to rise from the

0 V level (see **Fig 17.39B**). The changing current in the transformer combined with any leakage inductance causes these transients to be generated. The peak voltages need to be below the rated 55 V of the switching transistors.


Attach an oscilloscope or peak detecting voltmeter from the drain lead (center lead) of Q5 and Q6 to ground, and attach a 1 A load to the supply. Enable the supply and check the peak voltage across each transistor. If peak voltages are close to the transistor breakdown voltage (55 V) under light loading, stop testing. The switching transformer will need to be rewound with tighter spacing between all of the windings.

Repeat the previous test with a large load on the supply. Remove the fuse or current limiting from the battery and place a 30 A fuse in the fuse holder. Attach a load of around 100 W (such as an automotive light bulb) to the supply. You may have trouble with the battery protection circuit when trying to enable the supply with the 100 W light bulb attached. If so, leave the voltage on the ENABLE input to the supply, then cycle the POWER switch. The supply has a built in soft start circuit that brings up the output voltage slowly when the ENABLE input is powered before closing the POWER switch. It may be necessary to use this feature when testing the supply with large light bulb loads.

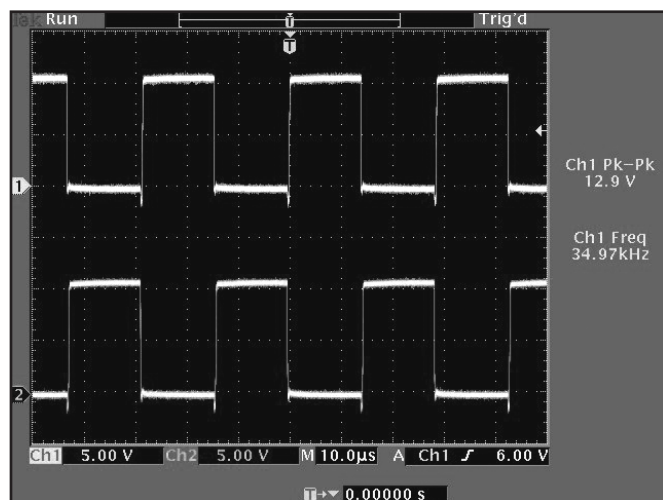With the 100 W load attached, check the transient voltages to make sure they are below 55 V. If the transients are low, repeat the test with a 200-300 W load. If any of the tests reveal transients close to the 55 V maximum, the transformer must be rewound with tighter spacing.



(A)

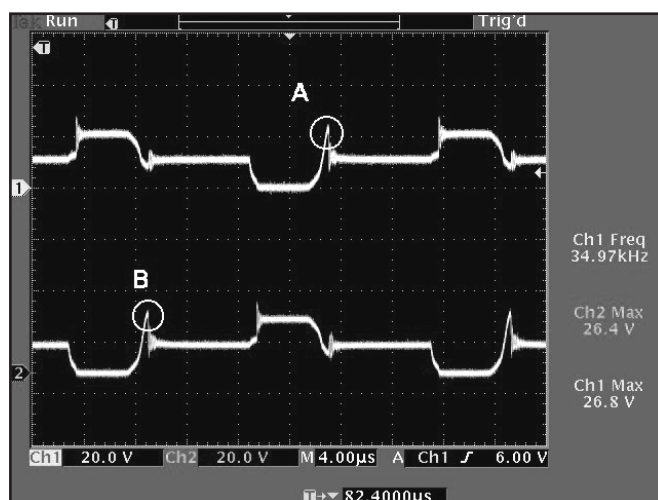

(B)

Fig 17.39 — At A, MOSFET gate driver waveforms shown with no MOSFET devices attached. Note the 180° phase shift between phases. At B, The drain to source voltages of Q5 and Q6 while operating the supply at a load of 300 W. The input voltage was between 10 and 11 V dc. The output voltage was set to 14 V dc. Note points A and B showing the transients generated during MOSFET turn-off.

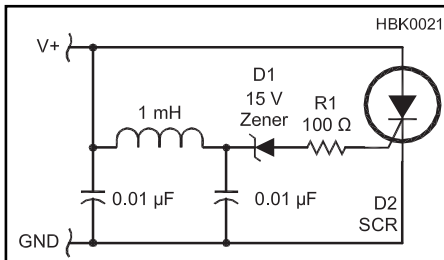


Fig 17.40 — A sample crowbar circuit. Values shown are recommended starting points. Determine the exact values experimentally, depending on the SCR and Zener diode used and the clamp voltage desired.

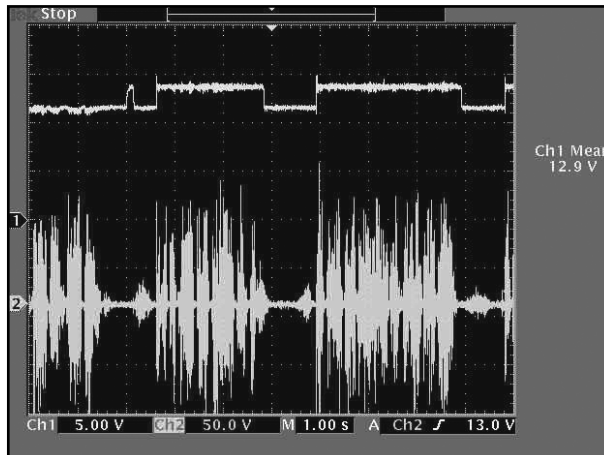


Fig 17.41 — The supply in operation. Trace 1 shows supply output voltage. Trace 2 shows the RF voltage at the input of the RF detector. The time base is set to 1 s/cm. The zero reference baseline for trace 1 is at arrow 1. The battery voltage is about 11 V dc (a weak battery) and the boost voltage is set to 13.8 V dc. The first two seconds the supply is OFF. It becomes enabled with RF excitation, as shown by the lower trace. It can also be enabled manually with the ENABLE switch.

Salvaging Parts for T1, L1 and D7

An old PC power supply is good source of recycled parts for T1, L1 and D7. Most PC supplies are rated for 250 W or more, so the components should be adequate. Note that a new core/bobbin for T1 and L1 core are included with the FAR Circuits PC board and D7 is available from Digi-Key, so salvaging these components is optional.

Start with the switching transformer, usually the largest one in the supply and covered with yellow tape. It's a good idea to collect an extra transformer or two for the project in case you break something during the disassembly process.

The transformer may be covered with electrical varnish, which can be removed by soaking the core and bobbin in acetone for several days. When the varnish is soft, start disassembly by unwinding the yellow tape from around the E-I core. Usually the smaller piece of the ferrite core will fall loose from the top of the transformer when this tape is removed (**Fig 17.42**). If this does not happen, carefully tap a small knife or chisel into the joint

between the two sections of the core. It should pry apart easily. Continue by gently pushing the E section of the core out of the bobbin. If this is difficult, soak the transformer for additional time in the acetone.

After removing the ferrite from the bobbin, unwind all of the wire but leave about an inch of wire attached to the pins protruding from the bottom of the bobbin. Once the old windings have been removed, grab the pins from the bottom with a pair of pliers and twist back and forth while pulling away from the bobbin. The bobbin is fragile and will break easily. If any of the pins are bridged by wire and solder, remove it before removing the pins.

Next, clean the bobbin and ferrite core with a small wire brush and acetone. A small rotary tool with a wire brush attachment works well. Remove as much of the old varnish as possible (**Fig 17.43**). Pay special attention to the junction area between the two pieces of ferrite. This needs to be clean so that no air gap is left when the transformer is reassembled.

The toroid inductor core used to make L1 can be found in the 5 V section of the PC power supply. Look for the largest donut inductor. The core itself is around an inch in diameter, pale yellow with one white axial surface. Usually the core is completely covered with #18 or similar copper wire, which needs to be removed and discarded.

As long as you're salvaging parts, you can save a few dollars by using the dual diode from the PC power supply. PC supplies use a common-cathode dual Schottky or similar fast switching type of diode in a TO-247 case. This diode is typically the largest three-lead package in the supply. You will find it attached to a heat sink, usually very close to the switching transformer. Often there will be a dual diode symbol in common cathode configuration on the package. A simple diode checker will determine if you have a good part. The diode will also have a mica insulator or sil-pad between it and the heat sink. Save this item, as it will be needed later.

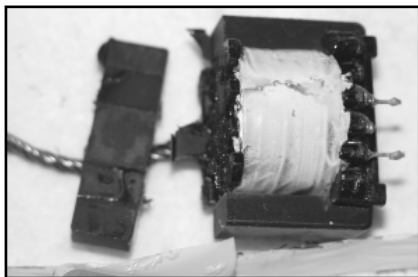


Fig 17.42 — Shown at A is a salvaged switching supply transformer before disassembly (shown with "I" section of core removed). Removal of pins from the transformer bobbin is shown at B.

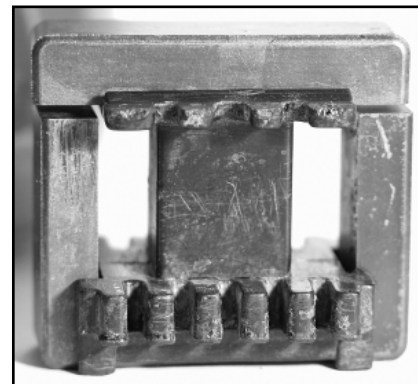
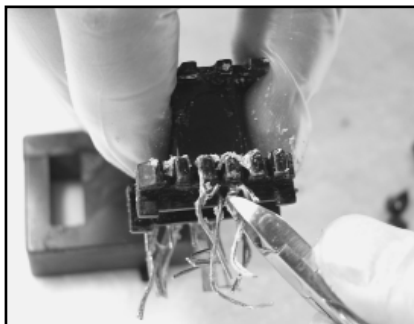


Fig 17.43 — Salvaged transformer core cleaned up and ready to go.

FINAL NOTES

The supply can be mounted in an enclosure provided that enough cooling is available for the switching transistors. The level of power drawn and the state of charge of the battery will determine the heat sink requirements. If the heat sink or transistor cases are too hot to touch, a bigger heat sink or more air flow is required.

A set of optional high frequency “snubbers” can also be added across T1 and the switching transistors. The snubbers are a series RC network used to reduce high frequency ringing that can occur during switching transitions. Place the snubbers from each leg of the transformer to the center tap of the transformer, and from the drain lead (center) of the switching transistors to ground. A 220 pF ceramic capacitor in series with a 220 Ω resistor is a good starting point for each snubber. It is best to determine the exact values experimentally. Find values that reduce the ringing without dissipating excessive heat in the resistors.

Some builders may want to add a crowbar circuit to the supply output. If a malfunction occurs in the supply feedback circuit, the output voltage could rise enough to damage attached equipment. The crowbar circuit watches the output voltage of the supply and shorts the output, blowing the fuse F1, if the voltage gets too high.

The simple circuit shown in **Fig 17.40** uses a Zener diode in series with the gate

of an SCR. A small current limiting resistor and RFI filter are also included. The current limiting resistor prevents damage to the gate of the SCR, and the filter prevents RF on the 12 V line from tripping the crowbar circuit. Values for the capacitors, inductor, resistor and Zener diode will depend on the particular SCR used. Although the values shown in the circuit are a good starting point, it is best to determine the exact values experimentally. When testing the crowbar circuit, use a large 12 V light bulb in series with the battery or voltage source. This can save on the cost of several fuses.

It may be desirable to add more filtering to the supply input and output leads and put the supply in a shielded enclosure. RFI generated by the supply should not be very strong, but at times it may be strong enough to be received by the attached radio. Shortening the input and output leads will also help. The best way to reduce received RFI is to use the RF DETECT input. Many radios receive properly with low input voltage and only need the boosted voltage when transmitting. The RF detect circuit allows the boost regulator to supply full power to the radio when transmitting (when RF is present at the input), and supply pass-through battery voltage on receive. This reduces EMI generated by the supply and received by the radio.

Fig 17.41 shows voltage traces of the supply in operation. The supply was power-

ing a radio that was being used to transmit SSB voice. In this case, the RF input was used to enable the supply and boost the rig voltage only when transmitting. Trace 1 shows the output voltage of the supply. The corresponding RF envelope is shown in trace 2. The terminal voltage of the battery was approximately 11 V dc, while the boosted output voltage was set at 13.8 V. The supply regulation action can be clearly seen as the higher levels of voltage shown in trace 1 after RF excitation turned the supply on. Test conditions are similar to normal operating conditions when running a transmitter from a battery.

This boost regulator has proven to be a useful and reliable way to regulate the voltage to a radio from a battery or weak power source. Many units have been built and used successfully. The booster can provide longer operation from a given battery and can enhance communications from mobile installations or from emergency power. Most of the components are available from one distributor, to make ordering easy. Even the most difficult task, winding the switching transformer, should take no more than an hour. Anyone who has had experience soldering can build and test this supply.

Thanks to John Kemppainen, N8BFL, and Jim Carstens, W8LTL (SK), for their encouragement and help with the original *QST* article, and for many hours field testing the design.

28-V, HIGH-CURRENT POWER SUPPLY

Many modern high-power transistors used in RF power amplifiers require 28-V dc collector supplies, rather than the traditional 12-V supply. By going to 28 V (or even 50 V), designers significantly reduce the current required for an amplifier in the 100-W or higher output class. The power supply shown in **Fig 17.44** through **Fig 17.48** is conservatively rated for 28 V at 10 A (enough for a 150-W output amplifier) — continuous duty! It was designed with simplicity and readily-available components in mind. Mark Wilson, K1RO, built this project in the ARRL lab.

CIRCUIT DETAILS

The schematic diagram of the 28-V supply is shown in **Fig 17.45**. T1 was designed by Avatar Magnetics specifically for this project. The primary requires 120-V ac, but a dual-primary (120/240 V) version is available. The secondary is rated for 32 V at 15 A, continuous duty. The primary is bypassed by two 0.01- μ F capacitors and protected from line transients by an MOV.

U1 is a 25-A bridge module available from a number of suppliers. It requires a heat sink in this application. Filter capacitor C1 is a computer-grade 22,000- μ F electrolytic. Bleeder resistor R1 is included for safety because of the high value of C1; bleeder current is about 12 mA.

There is a tradeoff between the transformer secondary voltage and the filter-

capacitor value. To maintain regulation, the minimum supply voltage to the regulator circuitry must remain above approximately 31 V. Ripple voltage must be taken into account. If the voltage on the bus drops below 31 V in ripple valleys, regulation may be lost.

In this supply, the transformer secondary voltage was chosen to allow use of a commonly available filter value. The builder found that 50-V electrolytic capacitors of up to about 25,000 μ F were common and the prices reasonable; few dealers stocked capacitors above that value, and the prices increased dramatically. If you have a larger filter capacitor, you can use a transformer with a lower secondary voltage; similarly, if you have a transformer in the 28- to 35-V range, you can calculate the size of the filter capacitor required. Equation 3, earlier in this chapter in the Filtration section, shows how to calculate ripple for different filter-capacitor and load-current values.

The regulator circuitry takes advantage


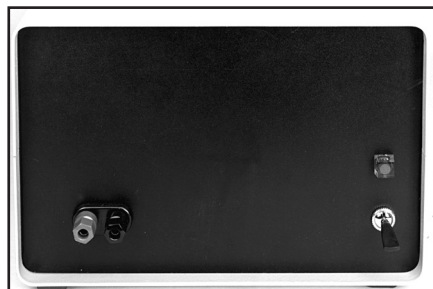


Fig 17.44 — The front panel of the 28-V power supply sports only a power switch, pilot lamp and binding posts for the voltage output. There is room for a voltmeter, should another builder desire one.

R9 is used to adjust supply output voltage. Since this supply was designed primarily for 28-V applications, R9 is a “set and forget” control mounted internally. A 25-turn potentiometer is used here to allow precise voltage adjustment. Another builder may wish to mount this control, and perhaps a voltmeter, on the front panel to easily vary the output voltage.

If the regulator circuitry should fail, or if a pass transistor should short, the unregulated supply voltage will appear at the output terminals. Most 28-V RF transistors would fail with 40-plus volts on the collector, so a prospective builder might wish to incorporate the overvoltage protection circuit shown in **Fig 17.46** in the power supply. This circuit is optional. It connects across the output terminals and

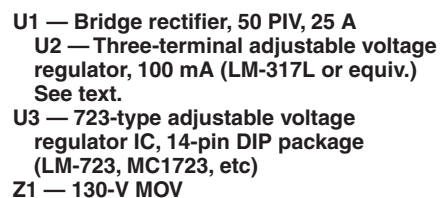

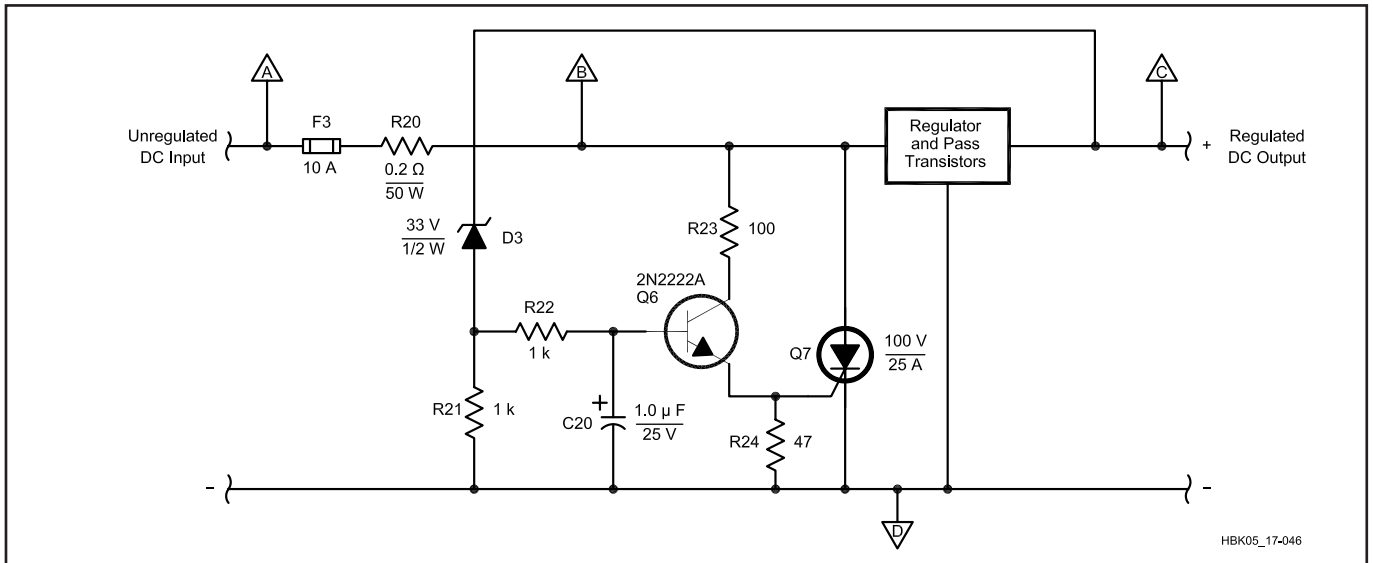


Fig 17.46 — Schematic diagram of the overvoltage protection circuit. Resistors are ¼-W, 5% carbon types unless noted.

D3 — 33 V, ½-W Zener (NTE 5036A or equiv.)

Q6 — NPN Transistor (2N2222A or equiv.)

Q7 — 100 V, 25A SCR (NTE 5522 or equiv.)

may be added or deleted with no effect on the rest of the supply. If you choose to use the “crowbar,” make the interconnections as shown. Note that R20 and F3 of Fig 17.46 are added between points A and B of Fig 17.45. If the crowbar is not used, connect F2 between points A and B of Fig 17.45.

The crowbar circuit functions as follows: The Zener-hold off diode (D3) blocks the positive regulated voltage from appearing at the base of Q6 until its avalanche voltage is exceeded. In the case of the device selected, this voltage level is 33 V, which provides for small overshoots that might occur with sudden removal of the output load (switching off a load, for instance).

In the event the output voltage exceeds 33 V, D3 will conduct, and forward bias Q6 through R22 and C20, which eliminates short duration transients and noise. When Q6 is biased on, trigger current flows through R23 and Q6 into the gate of SCR Q7, turning it on and shorting the raw dc source, forcing F3 to blow. Since some SCRs have a tendency to turn themselves on at high temperature, resistor R24 shunts any internal leakage current to ground.

CONSTRUCTION

Fig 17.47 shows the interior of the 28-V supply. It is built in a Hammond 1401K enclosure. All parts mount inside the box. The regulator components are mounted on a small PC board attached to the rear of the front panel. See **Fig 17.48**. Most of the parts were purchased at local electronics stores or from major national suppliers. Many parts, such as the heat sink, pass transistors, 0.1-Ω power resis-



Fig 17.47 — Interior of the 28-V, high-current power supply. The cooling fan is necessary only if the pass transistors and heat sink are mounted inside the cabinet. See text.

tors and filter capacitor can be obtained from scrap computer power supplies found at flea markets.

Q2-Q5 are mounted on a Wakefield model 441K heat sink. The transistors are mounted to the heat sink with insulating washers and thermal heat-sink compound to aid heat transfer. TO-3 sockets make electrical connections easier. The heat-sink surface under the transistors must be absolutely smooth. Carefully deburr all holes after drilling and lightly sand the edges with fine emery cloth.

A five-inch fan circulates air past the heat sink inside the cabinet. Forced-air cooling is necessary only because the heat sink is mounted inside the cabinet. If the heat sink was mounted on the rear panel with the fins vertical, natural convection would provide adequate cooling and no fan would be required.

U1 is mounted to the inside of the rear panel with heat-sink compound. Its heat sink is bolted to the outside of the rear panel to take advantage of convection cooling.

U2 may prove difficult to find. The 317L is a 100-mA version of the popular 317-series 1.5-A adjustable regulator. The 317L is packaged in a TO-92 case, while the normal 317 is usually packaged in a larger TO-220 case. Many electronics suppliers sell them, and direct replacements are available from many local electronics shops. If you can't find a 317L, you can use a regular 317.

R7 is made from two 0.1- Ω , 5-W resistors connected in parallel. These resistors get warm under sustained operation, so they are mounted approximately $\frac{1}{16}$ inch above the circuit board to allow air to circulate and to prevent the PC board from becoming discolored. Similarly, R6 gets warm to the touch, so it is mounted away from the board to allow air to circulate. Q1 becomes slightly warm during sustained operation, so it is mounted to a small TO-3 PC board heat sink.

Not obvious from the photograph is the use of a single-point ground to avoid

ground-loop problems. The PC-board ground connection and the minus lead of the supply are tied directly to the minus terminal of C1, rather than to a chassis ground.

The crowbar circuit is mounted on a small heat sink near the output terminals. Q7 is a stud-mount SCR and is insulated from the heat sink. The other components are mounted on a small circuit board attached to the heat sink with angle brackets.

Although the output current is not extremely high, #14 or #12 wire should be used for all high-current runs, including the wiring between C1 and the collectors of Q2-Q5; between R2-R5 and R7; between F2 and the positive output terminal; and between C1 and the negative output terminal. Similar wire should be used between the output terminals and the load.

TESTING

First, connect T1, U1 and C1 and verify that the no-load voltage is approximately 44 V dc. Then, connect unregulated voltage to the PC board and pass transistors. Leave the gate lead of Q6 disconnected from pin 8 of U4 at this time. You should be able to adjust the output voltage between approximately 20 and 30 V. Set the output to 28 V.

Next, short the output terminals to verify that the current foldback is working. Voltage should return to 28 when the shorting wire is disconnected. This completes testing and setup.

The supply shown in the photographs dropped approximately 0.1 V between no load and a 12-A resistive load. During testing in the ARRL Lab, this supply was run for four hours continuously with a 12-A resistive load on several occasions, without any difficulty.

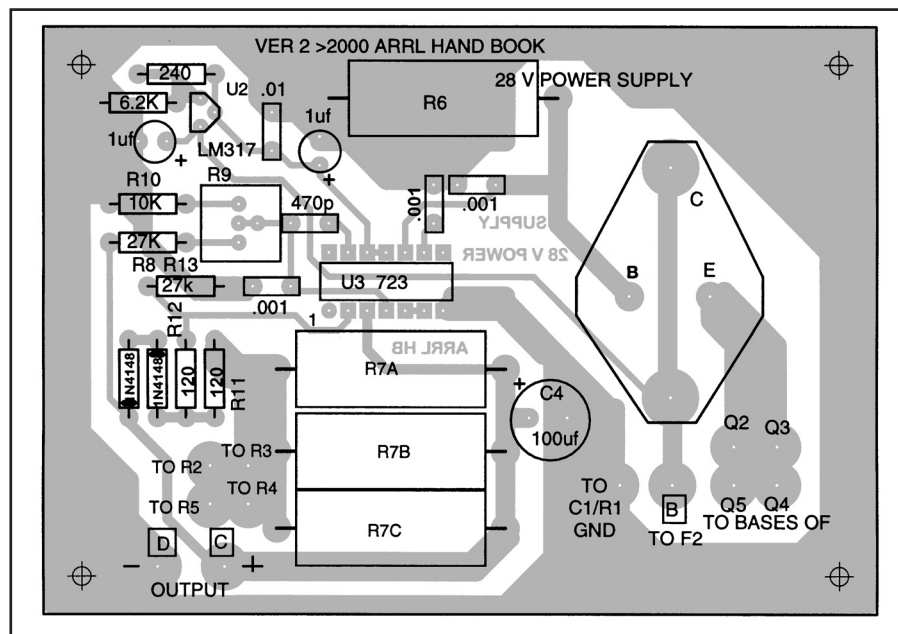


Fig 17.48 — Parts placement diagram for the 28-V power supply. A full-size etching pattern is in the **Templates** section of the *Handbook* CD-ROM.

A COMMERCIAL-QUALITY, HIGH-VOLTAGE POWER SUPPLY

This two-level, high-voltage power supply was designed and built by Dana G. Reed, W1LC. It was designed primarily for use with an RF power amplifier using a triode in class AB₂ grounded-grid operation. The supply is rated at a continuous output current of 1.5 A, and will easily handle intermittent peak currents of 2 A. The 12-V control circuitry, and the low-tap setting of the plate transformer secondary, can both be used with the N7ART 2-meter amplifier. See the **RF Power Amplifiers** chapter for details.

The step-start circuit is straightforward and ensures that the rectifier diodes are current-limited when the power supply is first turned on. A 6-kV meter is used to monitor high-voltage output.

Fig 17.49 is a schematic diagram of the bi-level supply. An ideal power supply for a high-power linear amplifier should operate from a 240-V circuit, for best line regulation. A special, hydraulic/magnetic circuit breaker also serves as the disconnect for the plate transformer primary. Don't substitute a standard circuit breaker, switch or fuses for this breaker; fuses won't operate quickly enough to protect the amplifier or power supply in case of an operating abnormality. The bleeder resistors are each 100 k Ω , 3 W and of stable MOF design. These resistors are wired across each of the 14 capacitors to equalize voltage drops in the series-connected bank. This choice of bleeder resistor value provides a lighter load (less than 25 watts total under high-tap output) and

benefits mainly the capacitor-bank filter by yielding much less heat as a result. A reasonable, but longer bleed-down time to fully discharge the capacitors results — about nine minutes after power is removed. A small fan is included to remove any excess heat from the power supply cabinet during operation.

POWER SUPPLY CONSTRUCTION

The power supply can be built into a 23 1/2 × 10 3/4 × 16-inch cabinet. The plate transformer is quite heavy at 67 lbs, so use 1/8-inch aluminum for the cabinet bottom and reinforce it with aluminum angle for extra strength and stability. The capacitor bank will be sized for the specific capacitors used. This project employed 3/8-inch thick polycarbonate for reasonable mechanical stabil-

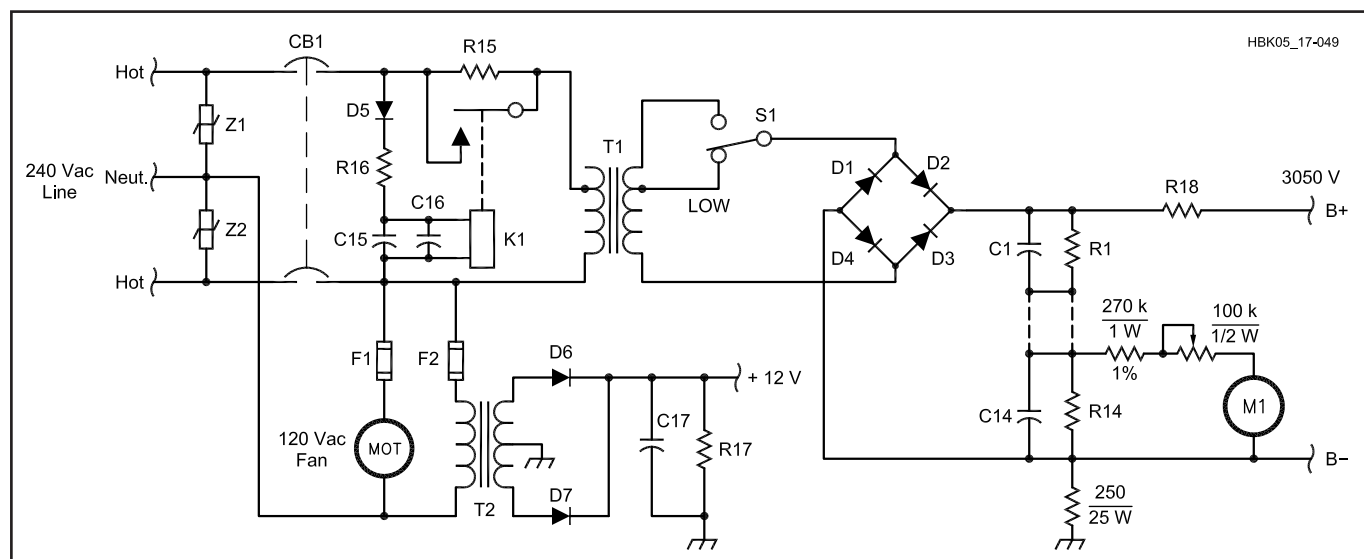


Fig 17.49 — Schematic diagram of the 3050-V/5400-V high-voltage power supply.

C1 to C14 — Electrolytic capacitor, 800 μ F, 450 V (Mallory CGS801T450V4L or equiv)

C15-C16 — Electrolytic capacitor, 4700 μ F, 50 V

C17 — Electrolytic capacitor, 1000 μ F, 50 V

CB1 — 20-A hydraulic/magnetic circuit breaker (Potter and Brumfield W68X2Q12-20 or equiv). 40-A version required for commercial applications/service (Potter and Brumfield W92X112-40)

D1-D4 — Commercial diode block assembly: K2AW HV14-1, from K2AW's Silicon Alley

D5 — 1000-PIV, 3-A diode, 1N5408 or equiv

D6-D7 — 200-PIV, 3-A diode, 1N5402 or equiv

F1-F2 — Fuse, 0.5 A, 250 V (Littelfuse® 313 Series, 3AG Glass Body or equiv)

K1 — DPDT power relay, 24-V dc coil; both poles of 240-V ac/25-A contacts in parallel (Potter & Brumfield PRD-11DY0-24 or equiv)

M1 — High-voltage meter, 6-kV dc full scale. (Important: Use a 1-mA or smaller meter movement to minimize parallel-resistive loading at R14. Also, select series meter-resistor and adjustment-potentiometer values to calibrate your specific meter. Values shown are for a 1-mA meter movement.)

MOT1 — Cooling fan, 119mm, 110-120-V ac, 30-60 CFM, (EBM 4800Z or equiv)

R1 to R14 — Bleeder resistor, 100 k Ω , 3 W, Metal Oxide Film (MOF)

R15 — Power resistor, 50 Ω , 100 W

R16 — Power resistor, 3.9 k Ω , 25 W

R17 — Power resistor, 30 Ω , 25 W

R18 — Power resistor, 20 Ω , 50 W

S1 — Ceramic rotary, 2-pos. tap-select

switch (optional). Voltage rating between tap positions should be at least 2.5 kV. Mount switch on insulated or ungrounded material such as a metal plate on standoff insulators, or an insulating plate, and use only a *non-conductive* or otherwise *electrically-isolated* shaft through the front panel for safety

T1 — High-voltage plate transformer, 220/230-V primary, 2000/3500-V, 1.5-A CCS JK secondary. (Peter W. Dahl Company, Inc., Hipersil C-Core.) Primary 220-V tap fed with nominal 240-V ac line voltage to obtain modest increase in specified secondary voltage levels

T2 — Power transformer, 120-V Pri., 18-VCT, 2-A Sec. (Hi-Q Magnetics; Mouser 41FJ020)

Z1-Z2 — 130-V MOV (AVX VE24M00131K or equiv)

ity and excellent high-voltage isolation. The full-wave bridge consists of four commercial diode block assemblies.

POWER SUPPLY OPERATION

When the front-panel breaker is turned on, a single 50- Ω , 100-W power resistor

limits primary inrush current to a conservative value as the capacitor bank charges. After approximately two seconds, step-start relay K1 actuates, shorting the 50- Ω resistor and allowing full line voltage to be applied to the plate transformer. No-load output voltages under low- and high-tap settings

as configured and shown in Fig 17.49 are 3050 V and 5400 V, respectively. Full-load levels are somewhat lower, approximately 2800 V and 4900 V. If a tap-select switch is used as described in the schematic parts list, it should only be switched when the supply is off.

THE MICRO M+

The Micro M+ is an ideal photovoltaic (PV) controller for use at home or in the field. It's an easy-to-build, one-evening project even a beginner can master. This project was designed by Mike Bryce, WB8VGE. An earlier charge controller called the "Micro M" proved to be a very popular project.¹

Hams really do like to operate their rigs from solar power. Many have found solar power to be very addictive. I had dozens of requests for information on how to increase the current capacity of the original "Micro M" controller. The Micro M would handle up to 2 A of current. I wanted to improve the performance of the Micro M while I was at it. Because the Micro M switched the negative lead of the solar panel on and off, that lead had to be insulated from the system ground. While that's not a problem with portable use, it may cause trouble with a home station where all the grounds should be connected. Here's what I wanted to do:

- Reduce the standby current at night
- Increase current handling capacity to 4 A
- Change the charging scheme to high (positive) side switching
- Improve the charging algorithm
- Keep the size as small as possible, but large enough to easily construct.

I called the end result the Micro M+. You can assemble one in about an hour. Everything mounts on one double-sided PC board. It's small enough to mount inside your rig yet large enough so you won't misplace it! You can stuff four of them in your shirt pocket! And, you need not worry about RFI being generated by the Micro M+. It's completely silent and

makes absolutely no RFI!

The Micro M+ will handle up to 4 A of current from a solar panel. That's equal to a 75-W solar panel.² I've reduced the standby current to less than one milliamp. I've also introduced a new charging algorithm to the Micro M+. All the current switching is done on the positive side. Now, you can connect the photovoltaic array, battery and load grounds together.

A complete kit of parts is available as well as just the PC board.³ The Micro M+ is easy to build, making it a perfect first time project.

HOW IT WORKS

Fig 17.50 shows the complete Micro


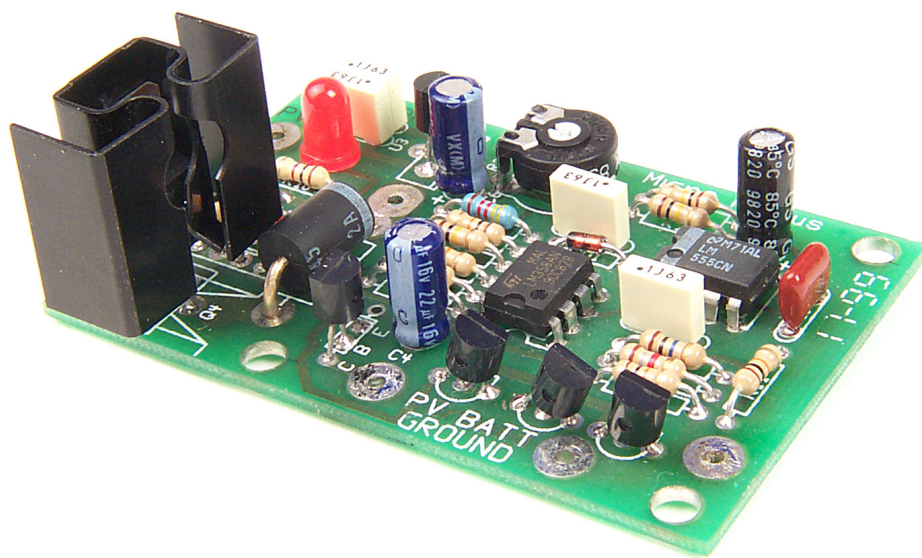


Fig 17.50 — This photo shows the Micro M+ charge controller circuit board. Leads solder to the board and connect to a solar panel and to the battery being charged.

M+. Fig 17.51 shows the schematic diagram. Let's begin with the current handling part of the Micro M+. Current from the solar panel is controlled by a power MOSFET. Instead of using a common N-channel MOSFET, however, the Micro M+ uses an STMicroelectronics STP80PF55 P-channel MOSFET. This P-channel FET has a current rating of 80 A with an $R_{DS(on)}$ of 0.016 Ω . It comes in a TO-220 case. Current from the solar panel is routed directly to the MOSFET source lead.

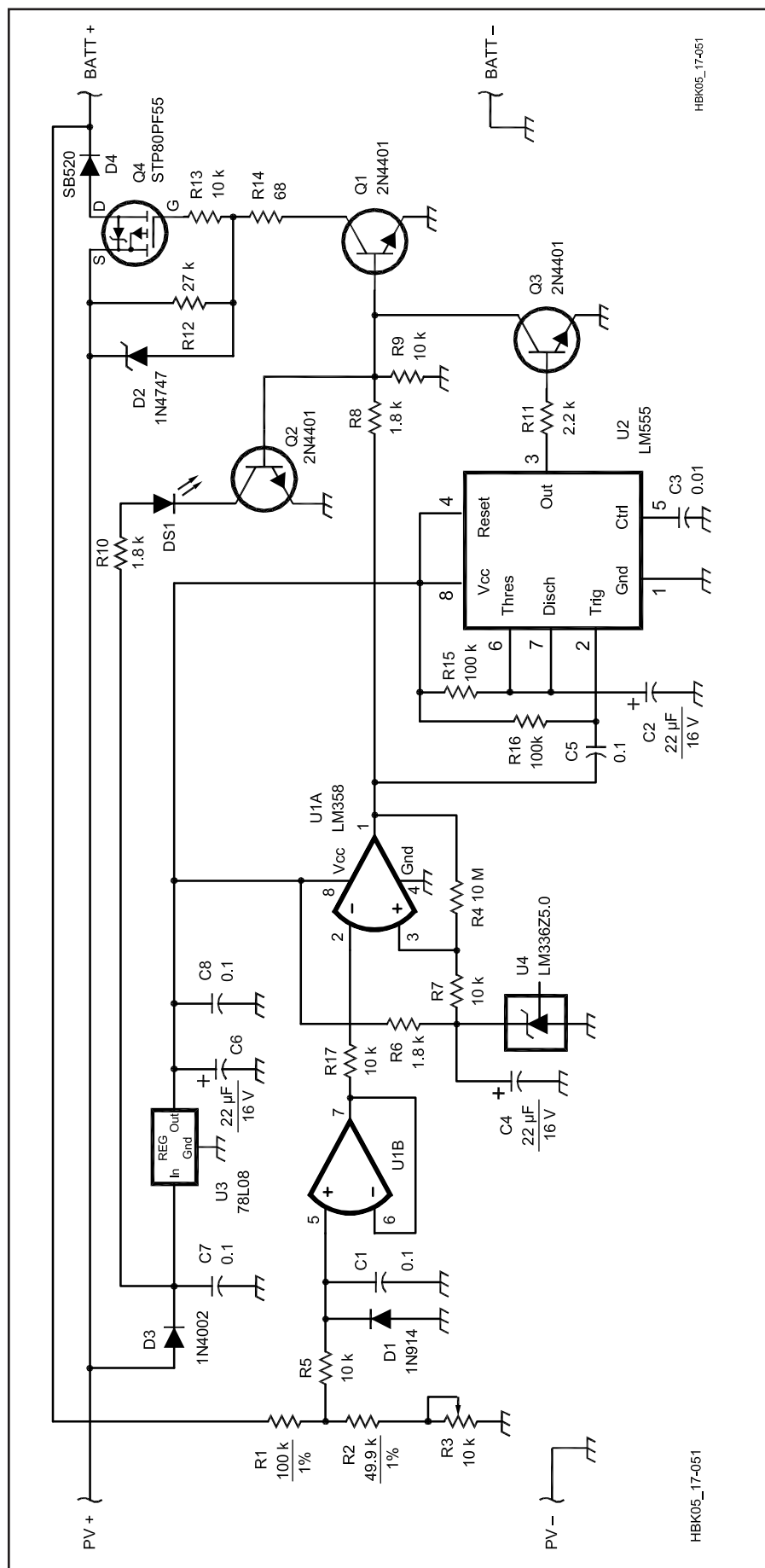N-channel power MOSFETs have very low $R_{DS(on)}$ and even lower prices. To switch current on and off in a high-side application, though, the gate of an N-channel MOSFET must be at least 10 V higher



than the rail it is switching. In a typical 12-V system, the gate voltage must be at least 22 V to ensure the MOSFET is turned completely on. If the gate voltage is less than that required to fully enhance the MOSFET, it will be almost on and somewhat off (the MOSFET is operating in its linear region). Hence, the device will likely be destroyed at high current levels.

Normally, to produce this higher gate voltage, some sort of oscillator is used to charge a capacitor via a voltage doubler. This charge pump generates harmonics that may ride on the dc flowing into the battery under charge. Normally, this would not cause any problem, and in most cases, a filter or two on the dc bus will eliminate most of the harmonics generated. Even the best filter won't get rid of all the harmonics, however. To compound the problem, long wire runs to and from the solar panels and batteries act like antennas.

The P-channel MOSFET eliminates the need for a charge pump altogether. To turn on a P-channel MOSFET, all we have to do is pull the gate lead to ground! Since the Micro M+ does not have a charge pump, it generates NO RFI!

Now, you may be wondering if the P-channel MOSFET is so great, why have you not seen them in applications like this before? The answer is twofold. First, the $R_{DS(on)}$ of a P-channel MOSFET has always been much higher than its N-channel cousin. Several years ago, a P-channel MOSFET with an $R_{DS(on)}$ of 0.12 Ω was

Fig 17.51 — The schematic diagram of the Micro M+ charge controller.

C1, C5, C7, C8 — 0.1 μ F

C2, C4, C6 — 22 μ F, 16 V electrolytic

C3 — 0.01 μ F

D1 — 1N914, small signal silicon switching diode

D2 — 1N4747, 20-V, 1-W Zener

D3 — 1N4002, silicon rectifier diode

D4 — SB520 20V, 5A Schottky diode (Mouser 512-SB520)

DS1 — LED, junkbox variety

Q1, Q2, Q3 — 2N4401 NPN small-signal transistor (2N2222 or 2N3904 will also work.)

Q4 — STP80PF55 P-channel MOSFET in TO-220 case (Mouser 511-STP80PF55).

You will also need a small clip-on heat sink for this case.

R1 — 100 k Ω , 1%

R2 — 49.9 k Ω , 1%

R3 — 10 k Ω trimmer

U1 — LM358AN, Dual op-amp

U2 — LM555AN timer

U3 — LM78L08, 8-V regulator

U4 — LM336Z-5.0, 5.0-V Zener diode in TO-92 case. The adjust terminal allows control of the temperature coefficient and voltage over a range. The adjust terminal is not used for the Micro M+.

considered very low. At that time an N channel MOSFET had an $R_{DS(on)}$ of 0.009 Ω . Suppose you want to control 10 A of current from your solar panel. Using the N-channel MOSFET above we find the MOSFET will dissipate less than a watt of power. On the other hand, the P-channel MOSFET will dissipate 12 W of power! Current generated by our solar panels is way too precious (and expensive) to have 12 W go up as heat from the charge controller.

The second factor was price. The P-channel MOSFET I described above would have easily sold for \$19 each. The N-channel device would have been a few dollars.

More recently, the $R_{DS(on)}$ of a typical P-channel MOSFET has fallen to 0.028 Ω . The price, while still a bit expensive, has dropped to about \$8 each.

With the P channel MOSFET controlling the current, diode D4—an SB520 Schottky—prevents battery current from flowing into the solar panel at night. This diode also provides reverse polarity protection to the battery in the event you connect the solar panel backwards. This protects the expensive P channel MOSFET.

Zener diode D2, a 1N4747, protects the gate from damage due to spikes on the solar panel line. Resistor R12 pulls the gate up, ensuring the power MOSFET is off when it is supposed to be.

THE MICRO M+ LIKES TO SLEEP

The Micro M+ never draws current from the battery. The solar panel provides all the power the Micro M+ needs, which means the Micro M+ goes to sleep at night. When the sun rises, the Micro M+ will start up again. As soon as the solar panel is producing enough current and voltage to start charging the battery, the Micro M+ will pass current into the battery.

To reduce the amount of stand-by current, diode D3 passes current from the solar panel to U3, the voltage regulator. U3, an LM78L08 regulator, provides a steady +8 V to the Micro M+ controller. Bypass capacitors, C6, C7 and C8 are used to keep everything happy. As long as there is power being produced by the solar panel, the Micro M+ will be awake. At sun down, the Micro M+ will go to sleep. Sleep current is on the order of less than 1 mA!

BATTERY SENSING

The battery terminal voltage is divided down to a more usable level by resistors, R1, R2 and R3. Resistor R3, a 10 k Ω trimmer, sets the state-of-charge for the Micro M+. A filter consisting of R5 and C1 helps keep the input clean from noise picked up by the wires to and from the solar panel.

Diode D1 protects the op-amp input in case the battery sense line was connected backwards.

An LM358 dual op-amp is used in the Micro M+. One section (U1B) buffers the divided battery voltage before passing it along to the voltage comparator, U1A. Here the battery sense voltage is compared to the reference voltage supplied by U4. U4 is an LM336Z-5.0 precision diode. To prevent U1A from oscillating, a 10-M Ω resistor is used to eliminate any hysteresis.

As long as the voltage of the battery under charge is below the reference point, the output of U1A will be high. This saturates transistors Q1 and Q2. Q2 conducts and lights LED DS1, the CHARGING LED. Q1, also fully saturated, pulls the gate of the P channel MOSFET to ground. This effectively turns on the FET, and current flows from the solar panel into the battery via D4.

As the battery begins to take up the charge, its terminal voltage will increase. When the battery reaches the state-of-charge set point, the output of U1A goes low. With Q1 and Q2 now off, the P channel MOSFET is turned off, stopping all current into the battery. With Q2 off, the CHARGING LED goes dark.

Since we have eliminated any hysteresis in U1A, as soon as the current stops, the output of U1A pops back up high again. Why? Because the battery terminal voltage will fall back down as the charging current is removed. If left like this, the Micro M+ would sit and oscillate at the state-of-charge set point.

To prevent that from happening, the output of U1A is monitored by U2, an LM555 timer chip. As soon as the output of U1A goes low, this low trips U2. The output of U2 goes high, fully saturating transistor Q3. With Q3 turned on, it pulls the base of Q1 and Q2 low. Since both Q1 and Q2 are now deprived of base current, they remain off.

With the values shown for R15 and C2, charging current is stopped for about four seconds after the state-of-charge has been reached.

After the four second delay, Q1 and Q2 are allowed to have base drive from U1A. This lights up the charging LED and allows Q4 to pass current once more to the battery.

As soon as the battery hits the state-of-charge once more, the process is repeated. As the battery becomes fully charged, the “on” time will shorten up while the “off” time will always remain the same four seconds. In effect, a pulse of current will be sent to the battery that will shorten over time. I call this charging algorithm “Pulse Time Modulation.”

As a side benefit of the pulse time modulation, the Micro M+ won’t go nuts if you put a large solar panel onto a small battery. The charging algorithm will always keep the off time at four seconds allowing the battery time to rest before being hit by higher current than normal for its capacity.

BUILDING YOUR OWN MICRO M+

There’s nothing special about the circuit. The use of a PC board makes the assembly of the Micro M+ quick and easy. It also makes it much easier if you need to troubleshoot the circuit. The entire circuit can be built on a piece of perf board.

The power MOSFET must be protected against static discharges. A dash of common sense and standard MOSFET handling procedures will work best. Don’t handle the MOSFET until you need to install it in the circuit. A wrist strap is a good idea to prevent static damage. Once installed in the PC board, the device is quite robust.

A small clip-on heat sink is used for the power MOSFET. If you desire, the MOSFET could be mounted to a metal chassis. If you do this, make sure you electrically insulate the MOSFET tab from the chassis.

If you plan to use the Micro M+ outside, then consider soldering the IC directly onto the board. I’ve found that cheap solder-plated IC sockets corrode. If you want to use an IC socket, use one with gold plated contacts.

Feel free to substitute part values. There’s nothing really critical. I do suggest you stick with 1% resistors for both R1 and R2. This isn’t so important for their closer tolerance but for the 50-PPM temperature compensation they have. You can use standard off-the-shelf parts for either or both R1 and R2, but the entire circuit should then be located in an environment with a stable temperature.

ADJUSTMENTS

You’ll need a good digital voltmeter and a variable power supply. Set the power supply to 14.3 V. Connect the Micro M+ battery negative lead to the power supply negative lead. Connect the Micro M+ PV positive and battery positive leads to the power supply positive lead. The charging LED should be on. If not, adjust trimmer R3 until it comes on. Check for +8 V at the VCC pins of the LM358 and the LM555. You should also see +5 V from the LM336Z5.0 diode.

Quickly move the trimmer from one end of its travel to the other. At one point the LED will go dark. This is the switch point. To verify that the “off pulse” is working, as soon as the LED goes dark quickly

reverse the direction of the trimmer. The LED should remain off for several seconds and then come back on. If everything seems to be working, it's time to set the state-of-charge trimmer.

Now, slowly adjust the trimmer until the LED goes dark. You might want to try this adjustment more than once as the closer you get the comparator to switch at exactly 14.3 V, the more accurate the Micro M+ will be. Here's a hint I've learned after adjusting hundreds of Micro M+ controllers. Set the power supply to slightly above the cut-off voltage that you want. If you want 14.3 V, then set the supply to 14.5 V. I've found that in the time it takes to react to the LED going dark, you overshoot the cut-off point. Setting the supply higher takes this into account and usually you can get the trimmer set to exactly what you need in one try. That's all you need to do. Disconnect the supply from the Micro M+ and you're ready for the solar panel.

ODDS AND ENDS

The 14.3-V terminal voltage will be correct for just about all sealed and flooded-cell lead-acid batteries. You can change

the state-of-charge set point if you want to recharge NiCds or captive sealed lead-acid batteries.

Keep the current from the solar panel within reason for the size of the battery you're going to be using. If you have a 7-amp hour battery, then don't use a 75-W solar panel. You'll get much better results and smoother operation with a smaller panel.

The tab of the power MOSFET is electrically hot. If you plan on using the Micro M+ without a protective case, make sure you insulate the tab from the heatsink. A misplaced wire touching the heatsink could cause real damage to both the Micro M+ and your equipment. A small plastic box from RadioShack works great.

MORE CURRENT?

Well yes, you can get the Micro M+ to handle more current. You must increase the capacity of the blocking diode and mount the power MOSFET on a larger heat sink. I've used an MBR2025 diode and a large heatsink for the MOSFET and can easily control 12 A of current.

BATTERY CHARGING WITHOUT A SOLAR PANEL?

Yes, it's possible. The trick is to use a power supply for which you can limit the output current. A discharged lead-acid battery will draw all the current it can from the charging source. In a solar panel setup, if the panel produces 3 A, that's all it will do. With an ac-powered supply, the current can be excessive. To use the Micro M+ with an ac-powered supply, set the voltage to 15.5 V. Then limit the current to 2 or 3 A.

No matter if you're camping in the out-back, or storing photons just in case of an emergency, the Micro M+ will provide your battery with the fullest charge. The Micro M+ is simple to use and completely silent. Just like the sun!

Notes

¹The Micro M, September 1996 *QST*, p 41.

²A 75-W module produces 4.4 A at 17 V. The Micro M+ can easily handle the extra 400 ma.

³PC boards, partial kits and full kits are available from Sunlight Energy Systems, www.seslogic.com.

THE UPS — A UNIVERSAL POWER SUPPLY

If you have spent much time around personal computers, you have probably heard of the uninterruptible power supply (UPS). This supply is designed to provide a continuous source of power for a computer in the event of an ac power-line failure. The UPS plugs into the ac house current and the computer plugs into the UPS. Under normal operating conditions, the UPS passes the 120-V house current to the computer. Surge protection and ac power conditioning circuitry is included in the UPS, protecting your computer from voltage spikes and other electrical conditions that could cause damage.

A UPS contains a battery and dc-to-ac inverter circuitry. The battery-charging circuitry in the UPS will maintain the battery at a full charge during normal operation. If the ac power goes off for any reason, the inverter automatically turns on to maintain the 120-V ac supply. You can continue working on the computer, either until the UPS battery discharges or until the ac power comes back on. At the very least, this will give you time to save files and shut down your computer normally.

This project is adapted from the January 1999 *QST* Technical Correspondence column, page 64, by Robert Whitaker, K15PG.

It describes how you can modify a UPS to supply 120 V ac and 12 V dc for a wide variety of ham-shack applications.

WHAT TO LOOK FOR, WHERE TO FIND IT

Computer salvage dealers, computer shows and hamfests are good places to

shop for a used UPS. Try calling the service department of some computer dealers and computer-repair services to find out what they have on hand.¹ You may pick up one or more older supplies that were taken in trade or with failed batteries, for much less than you would pay for a new UPS. Computer users often throw these

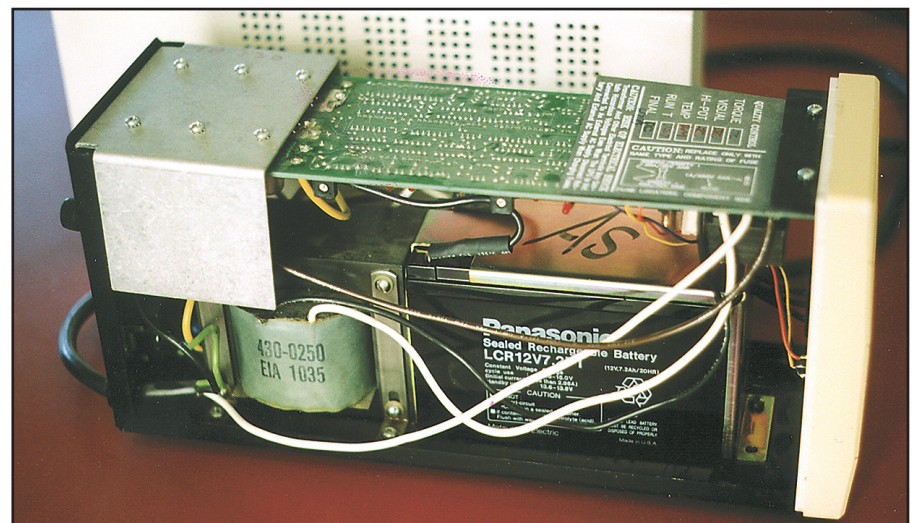


Fig 17.52 — UPS with cover removed to show internal layout. All UPS's have ac-line conditioning components, a battery, and a dc-to-ac inverter.

supplies away when the battery fails, even though many of the supplies have user-replaceable batteries!

Look for a UPS that can be forced into the inverting mode without the need to disconnect it from an active ac line. Most medium-sized units have an on/off switch and a test/alarm disable switch. Some American Power Conversion (APC)² UPS's have secondary DIP switches labeled TEST and ALARM DISABLE. On these models, the unit switches to the inverter mode while connected to ac power when you switch the unit on and press the ALARM DISABLE button.

Higher grade UPS's, such as the APC Back-UPS Pro series have a single on/off power pushbutton. These models can usually be forced into the inverter mode by pressing and holding the pushbutton for a few seconds.

Most medium or small UPS's use a single 12-V gel cell. Larger supplies may use two 6-V batteries in series. Some use two 12-V batteries to form a 24-V system. You will want a UPS with a 12-V system for maximum utility. A 12-V system can be easily configured to work with an external deep-discharge or marine battery. **Fig 17.52** shows a small UPS with the cover removed.

MODIFYING A UPS

If you have a UPS with a battery that will no longer hold a charge, you can either replace the battery or simply use your Universal Power Supply with an external battery. Remember that used batteries are considered hazardous materials, and must be taken to a recycling center or otherwise disposed of properly. Used or new batteries for these supplies are usually not too expensive. Check with battery suppliers like E. H. Yost & Company, W & W Manufacturing and B. G. Micro.

With the battery removed, test the charging circuit by plugging the UPS into a 120-V ac outlet and checking the voltage at the battery leads. With a 12-V system, the charging voltage should be around 13.85 V.

To attach an external battery to the UPS, simply bring the battery-lead connections outside the case. **Fig 17.53** shows how you can add a set of terminal posts on the back panel. You should also install



Fig 17.53 — This rear-panel view of a converted UPS shows a pair of binding posts for the 12 V dc connections and a fuse holder for the 12 V output. **Carefully position and drill the mounting holes for the binding posts and fuse holder, so that you don't damage existing parts. Ensure that the placement of these parts will not interfere with any existing components. A Unibit or KWIK STEPPER is ideal for cutting through the 1/8-inch thick steel rear panel. (See "Tool Tips," Technical Correspondence, QST, Dec 1998, p 63.)**

a chassis-mounted fuse holder in series with the positive terminal post. A 15- or 20-A fuse should be sufficient to provide adequate current with a margin of safety against short circuiting the output.

Many UPS's have a DIP switch, one section of which disables the power-failure alarm. If your supply doesn't have such a switch, you may want to permanently disable the alarm by unsoldering the alarm lead or cutting a PC board trace.

Keep extra fuses handy by taping spares to the inside or outside of the case. Be sure to include extra fuses for the 120-V, ac-input and 12-V, dc-output lines. Don't let a careless mistake and a blown fuse deprive you of power when you need it most!

USING YOUR UPS

An uninterruptible power supply converted to a universal power supply has many uses:

- Portable 120-V, ac-power source using the internal battery.
- Portable 12-V, dc-power source using the internal battery.
- 120-V, ac-power source with dc for the inverter taken from an external 12-V, dc-automotive or deep-cycle battery.
- Base station 12-V, dc-power supply and 120-V, ac-backup supply.
- Battery charger (12 V) using 120-V, ac-line input.

The UPS is intended for medium power output for short-term use. Don't expect the internal battery-driven inverter or the battery alone to power your 100-W HF rig for a week. You can expect to power a VHF/UHF-mobile radio at medium power for a day or more during an emergency. If you are using an HT, you can probably operate it on high power for a week or more.

Adding a heavy gel-cell or deep-cycle marine battery in parallel with — or independently from — the internal back-up battery will prolong the power-delivery cycle. Be sure that you don't draw more power than your UPS's rated output. If you must draw power at or near the rated power output, use a fan to force air inside the case to help get rid of the heat.

HOW LONG WILL IT LAST?

A test may help you estimate how long you can expect to use the UPS's battery-driven inverter with a given load. Connect a lamp with a 60-W light bulb, which will draw 0.5 A at 120 V. Two lamps in parallel will draw 1 A. (Just plug in two lamps to the ac output of your supply.) Use a voltmeter to record the battery voltage at the beginning of the test and every 5 to 15 minutes. Plot your data on a graph, with time along the horizontal (X) axis and the battery voltage along the vertical (Y) axis.

Notes

¹ATCI Consultants is one possible source for used uninterruptible power supplies.

www.dallas.net/~atci

²American Power Conversion manufactures a variety of supplies and also offers repair and battery-replacement services.

www.apcc.com

A PORTABLE POWER SUPPLY

This project was developed and the text written by Tony Jarvis, G6TTL. It originally appeared in the May, 1997 issue of *RadCom*, the monthly publication of the Radio Society of Great Britain (RSGB).

When time permits, I enjoy participating in the Backpacker series of RSGB contests,¹ operating in the 3-W category. The power supply I use for these outings is described here and shown in **Fig 17.54**. It is ideal for the purpose and can also be used as a simple, uninterruptible power supply (UPS) for the shack.

DESIGN CRITERIA

- A weight maximum of 10 lb (4.5 kg)
- Able to be carried in a small backpack
- Able to be plugged into the nearest power outlet to be recharged
- When at home, to run in 'float-charge mode' to operate low-current equipment
- To be of reasonable cost
- To use readily available components

At a Rainham Rally, I found several sealed, lead-acid cells rated at a nominal 12 V and 7-Ah capacity. They weighed in at a little over 2.2 kg (5 lb) — just what I needed! To prevent gassing, care must be exercised to not overcharge sealed cells, which requires a charge voltage limit of 13.8 V at the terminals. Thus, a stabilized supply is essential.

THE CIRCUIT

The float charger is hardly original; it was adapted from an excellent series of articles by John Case.² One major consideration was the need to over-engineer it, as I would leave it plugged in and switched on almost continuously.

Fig 17.55 shows the circuit diagram. Many of the components were salvaged from redundant equipment or the junk

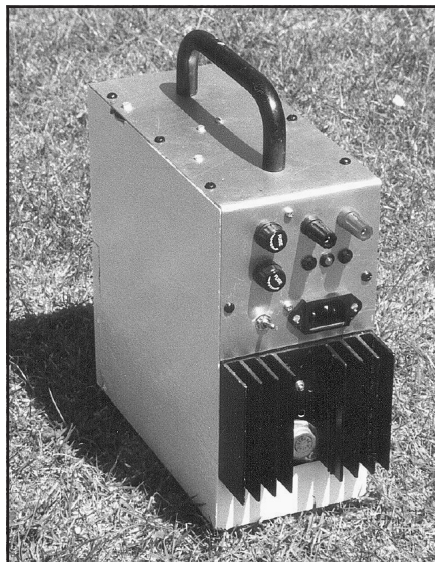


Fig 17.54 — The completed power supply.

Table 17.1

Components List

Resistors

R1	1.2 k Ω
R2	1.5 k Ω
R3	2.7 k Ω
R4	0.5 Ω , 2W
R5	8.2 k Ω
R6	7.5 k Ω
R7	820 Ω
R8	500 Ω linear preset potentiometer
R9	1 k Ω linear preset potentiometer
VDR1	V275LA40A

All resistors 1/2-W, metal film, 5% tolerance, unless otherwise specified.

Capacitors

C1	10,000 μ F, 40 V electrolytic
C2	4.7 μ F, 40 V electrolytic
C3	500 pf ceramic

Semiconductors

D1	Red LED
D2	Yellow LED
D3	Green LED
D4	MR752 (or similar)
D5	50 PIV, 25A
U1	LM723
Q1	2N3055

Additional items

F1	1A fuse and holder
F2	3A fuse and holder
S1	DPST toggle
T1	Power transformer with 2 ea, 15V @ 0.75A secondaries
	7Ah sealed lead-acid battery
	IEC socket
	Matrix board
	Screw terminals, insulated
	Case to suit

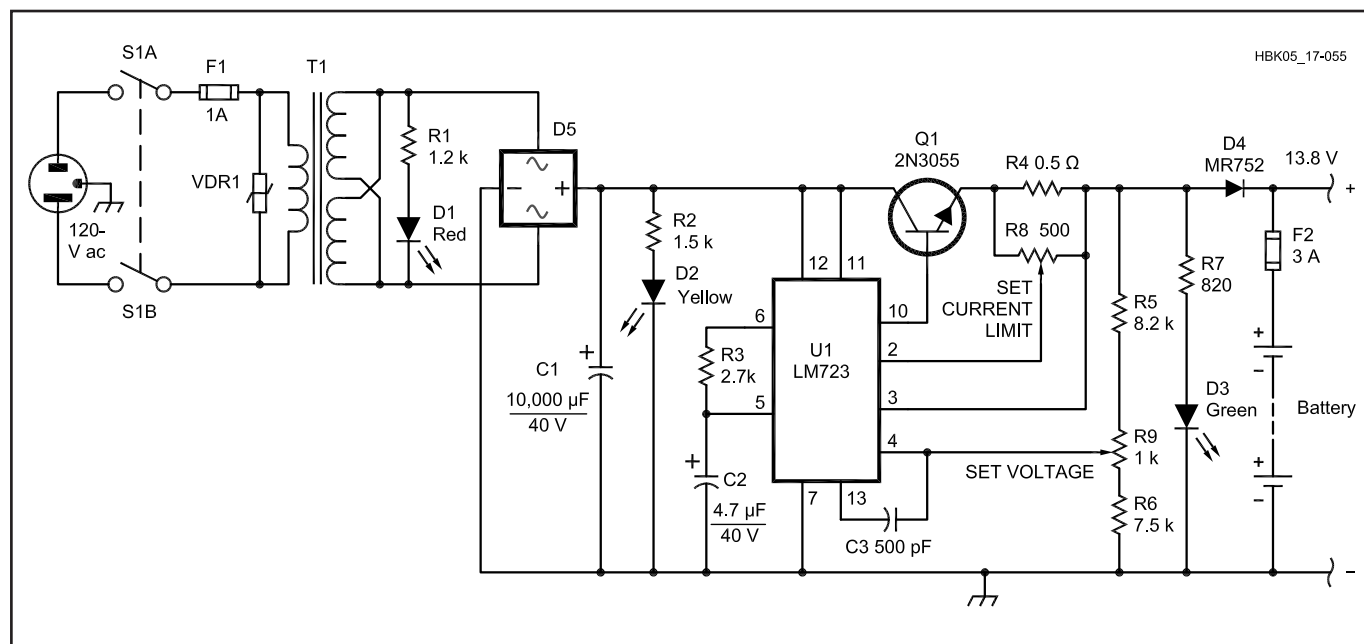


Fig 17.55 — Schematic diagram. The portable power supply works by float-charging a sealed lead-acid battery to provide an uninterruptible supply.

box; however, the critical components — transformer, pass transistor, reservoir capacitor and regulator chip — were all purchased new.

There are many options available for layout; mine were dictated by the size and shape of the heatsink. In my case, the box that holds it all is made from half-inch plywood, with the major components mounted on an L-shaped aluminum plate that forms the front and part of one side. A voltage-dependent resistor (varistor) is located across the primary of the transformer, and an over-current control is provided to limit the current to 1.5A.

A heavy-duty diode, D4, is incorporated in the feed to the battery, and LEDs are

placed at strategic points as a confidence feature and for ease of fault-finding. The voltage controller, an LM723, is mounted, along with its components, on a small piece of matrix board, the remaining components being wired point-to-point using substantial cable for the heavy-current paths. Setup is quite straightforward — connect everything together to a fully charged battery, connect a voltmeter to the battery's terminals, turn-on and adjust the output to 13.8V as measured at the battery terminals. Set the current limit to 1.5A, which in practice is rarely exceeded.

RESULTS

Does it meet the criteria set forth previ-

ously? That is for you to decide:

- Weight — 11 lb.
- Size — approximately 10 × 10 × 4 inches, including heatsink and handle.
- Cost — about \$40.
- Capacity — enough for a full backpacking session.

Even when left on continuously, the temperature of the portable power pack hardly rises above room temperature.

Notes

¹Backpacking — Summertime Delights, G6TTL, *RadCom*, May, 1997.

²Power Supplies on a Shoestring, GW4HWR, *RadCom*, July and August 1986.

